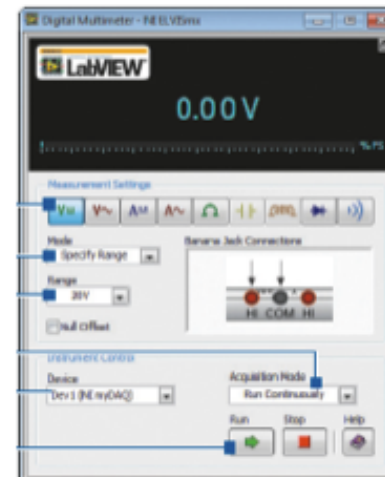


Uncertainty Analysis

- Given the relationship between the known resistors and the unknown resistors, find the uncertainty in your measurement that is due to the uncertainty in the values of R_1 and R_2 ($100\Omega, \pm 1\%$).
- **Assume that the precision error in decade resistor/Elenco Box is very small.** ... However their setting resolution is only *1 Ohm*. **Account for this value in the total error budget.**
- How do you account for the fact that the “Elvis” voltmeter only has two digits of precision in voltage?...
- Compare this calculated value to the standard deviation you computed

based on your 20 resistors

based on all 80 resistors



- Comment on the manufacturer’s claim as to the accuracy of these resistors.

Uncertainty Analysis (2)

- Precision Uncertainty ... Due to Bridge Resistors ...

$$R_x = f(R_1, R_2, R_3) = \frac{R_2 R_3}{R_1}$$

$$U_{R_x} = \sqrt{\left[\frac{\partial}{\partial R_1} \left(\frac{R_2 \cdot R_3}{R_1} \right) \right]^2 \cdot U_{R_1}^2 + \left[\frac{\partial}{\partial R_2} \left(\frac{R_2 \cdot R_3}{R_1} \right) \right]^2 \cdot U_{R_2}^2 + \left[\frac{\partial}{\partial R_3} \left(\frac{R_2 \cdot R_3}{R_1} \right) \right]^2 \cdot U_{R_3}^2}$$

$$\left[\begin{array}{l} \frac{\partial f}{\partial R_1} = -\frac{R_2 R_3}{R_1^2} \\ \frac{\partial f}{\partial R_2} = \frac{R_3}{R_1} \\ \frac{\partial f}{\partial R_3} = \frac{R_2}{R_1} \end{array} \right] \rightarrow U_{R_x} = \sqrt{\left[\frac{R_2 \cdot R_3}{R_1^2} \right]^2 \cdot U_{R_1}^2 + \left[\frac{R_3}{R_1} \right]^2 \cdot U_{R_2}^2 + \left[\frac{R_2}{R_1} \right]^2 \cdot U_{R_3}^2}$$

Uncertainty Analysis (3)

- Precision Uncertainty ... Due to Bridge Resistors ...

$$R_x = f(R_1, R_2, R_3) = \frac{R_2 R_3}{R_1}$$

$$\text{Normalize} \rightarrow \frac{U_{R_x}}{R_x} = \sqrt{\left(\frac{R_1}{R_2 \cdot R_3}\right)^2 \left(\left[\frac{R_2 \cdot R_3}{R_1^2}\right]^2 \cdot U_{R_1}^2 + \left[\frac{R_3}{R_1}\right]^2 \cdot U_{R_2}^2 + \left[\frac{R_2}{R_1}\right]^2 \cdot U_{R_3}^2 \right)} = \sqrt{\left(\frac{U_{R_1}}{R_1}\right)^2 + \left(\frac{U_{R_2}}{R_2}\right)^2 + \left(\frac{U_{R_3}}{R_3}\right)^2}$$

Assume Precision Uncertainty of Elenco Box ~ 0

Elenco Resolution Error $\rightarrow$

$$R_x = \frac{R_2 \cdot R_3}{R_1} \rightarrow R_1 \approx R_2 \rightarrow \frac{1}{n} \sum_{i=1}^n R_x \approx \frac{1}{n} \sum_{i=1}^n R_3 \rightarrow \boxed{\left(\frac{U_{R_3}}{R_3}\right) \approx \frac{1_{\Omega}}{\bar{R}_x}}$$

$$\bar{R}_x \equiv \frac{1}{n} \sum_{i=1}^n R_x$$

$$R_x = \left(\frac{R_2 R_3}{R_1}\right) \rightarrow \frac{R_3}{R_x} = \frac{R_1}{R_2} \approx \frac{100\Omega}{100\Omega} \sim 1$$

Uncertainty Analysis (4)

... *Uncertainty Due to Bridge Resistors* ...

$$\frac{U_{R_x}}{R_x} = \sqrt{\left(\frac{U_{R_1}}{R_1}\right)^2 + \left(\frac{U_{R_2}}{R_2}\right)^2 + \left(\frac{U_{R_3}}{R_3}\right)^2} = \sqrt{\left(\frac{U_{R_1}}{R_1}\right)^2 + \left(\frac{U_{R_2}}{R_2}\right)^2 + \left(1_{\Omega} / \frac{1}{n} \sum_{i=1}^n R_x\right)^2}$$


- How do you account for the fact that the meter only has two digits of precision

Voltmeter Resolution Error →

$$U_{R_x V_M} \approx \frac{U_{V_M}}{\partial V_M / \partial R_x} \rightarrow V_M = \frac{R_1 \cdot R_x - R_2 \cdot R_3}{(R_1 + R_2) \cdot (R_x + R_3)} V_{ex}$$

U_{V_M} → *Resolution Error in Voltmeter Reading*

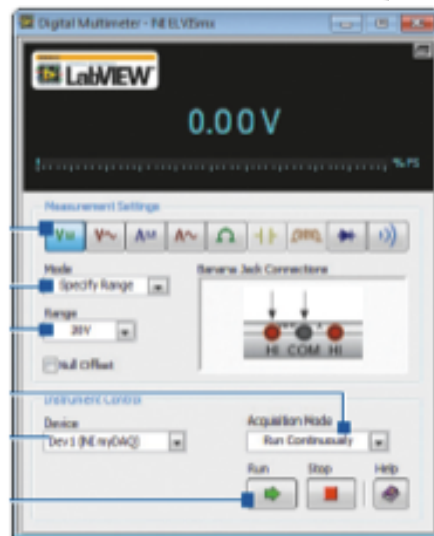$U_{R_x V_M}$ → *Error in R_x Due to Voltmeter Resolution Error*




Uncertainty Analysis (5)

... *Uncertainty Due to Voltmeter Resolution...*

$$V_M = V_{ex} \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)} \rightarrow$$

$$\frac{\partial V_M}{\partial R_x} = V_{ex} \left[\frac{R_1}{(R_1 + R_2)(R_3 + R_x)} - \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{R_1(R_3 + R_x) - R_1 R_x + R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] =$$
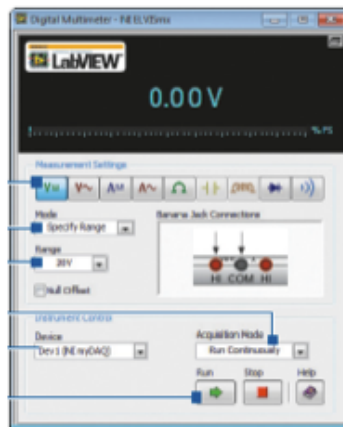
$$V_{ex} \left[\frac{R_1 R_3 + R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{(R_1 + R_2) \cdot R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{R_3}{(R_3 + R_x)^2} \right]$$



$U_{V_M} \rightarrow$ Resolution Error in Voltmeter Reading

$U_{R_x V_M} \rightarrow$ Error in R_x Due to Voltmeter Resolution Error

Uncertainty Analysis (6)

Voltmeter Resolution Error →

$$U_{R_x V_M} \approx \frac{U_{V_M}}{\partial V_M / \partial R_x} = \frac{U_{V_M}}{V_{ex} \frac{R_3}{(R_x + R_3)^2}} = \frac{(R_x + R_3)^2}{V_{ex} \cdot R_3} U_{V_M}$$

Normalize Error →

$$\frac{U_{R_x V_M}}{R_x} = \frac{1}{R_x} \frac{(R_x + R_3)^2}{R_3} \frac{U_{V_M}}{V_{ex}} = \frac{1}{\frac{R_2 \cdot R_3}{R_1}} \frac{(R_x + R_3)^2}{R_3} \frac{U_{V_M}}{V_{ex}} = \frac{R_1}{R_3} \frac{(R_x + R_3)^2}{R_2 \cdot R_3} \frac{U_{V_M}}{V_{ex}}$$

Since → $R_1 \approx R_2 \rightarrow R_x \approx R_3 \rightarrow \frac{U_{R_x V_M}}{R_x} = \frac{(2 \cdot R_x)^2}{R_3 \cdot R_3} \frac{U_{V_M}}{V_{ex}} = 4 \cdot \frac{U_{V_M}}{V_{ex}}$ For Balanced Bridge

$U_{V_M} \rightarrow$ Resolution Error in Voltmeter Reading

$U_{R_x V_M} \rightarrow$ Error in R_x Due to Voltmeter Resolution Error

Uncertainty Analysis (7)

$$\frac{U_{R_x}}{R_x} = \sqrt{\left(\frac{U_{R_1}}{R_1}\right)^2 + \left(\frac{U_{R_2}}{R_2}\right)^2 + \left(1_{\Omega} / \frac{1}{n} \sum_{i=1}^n R_x\right)^2 + \left(\frac{U_{R_x V_M}}{R_x}\right)^2} =$$

$$\sqrt{\underbrace{\left(\frac{U_{R_1}}{R_1}\right)^2 + \left(\frac{U_{R_2}}{R_2}\right)^2}_{\text{Resistor Precision Error}} + \underbrace{\left(1_{\Omega} / \frac{1}{n} \sum_{i=1}^n R_x\right)^2}_{\text{Elenco Resolution Error}} + \underbrace{\left(4 \cdot \frac{U_{V_M}}{V_{ex}}\right)^2}_{\text{Voltmeter Resolution Error}}}$$