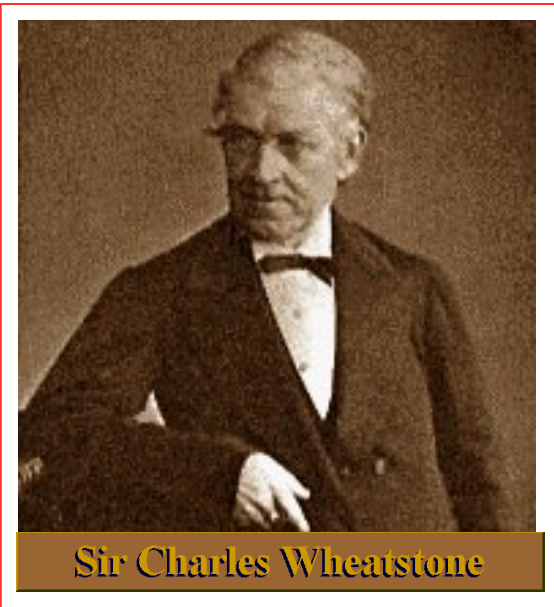


Laboratory 5: Wheatstone Bridge and Measurement Uncertainty

- ***Lab Objectives:***

- Understand Wheatstone Bridge Properties
- Power Dissipation in Resistor
- Reading the Resistor Labeling Code
- Balancing a Resistance Bridge
- Using a resistance bridge to measure and unknown resistance
- Understand how to Calculate statistics levels for a random population


Chapters 7, 3, Beckwith



You will build this bridge ...

*Known
Precision
100 Ω resistors*


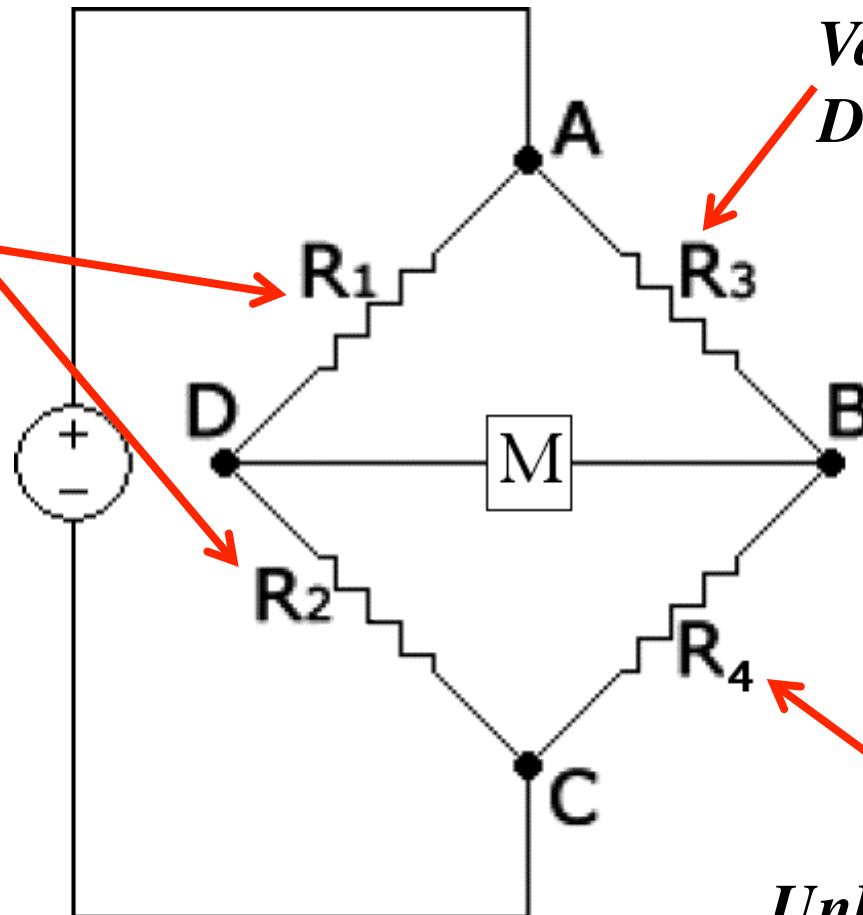
- You will
Balance this
bridge ...
Using R_3
To determine
 R_4




Unknown Resistor

Wheatstone Bridge (1)

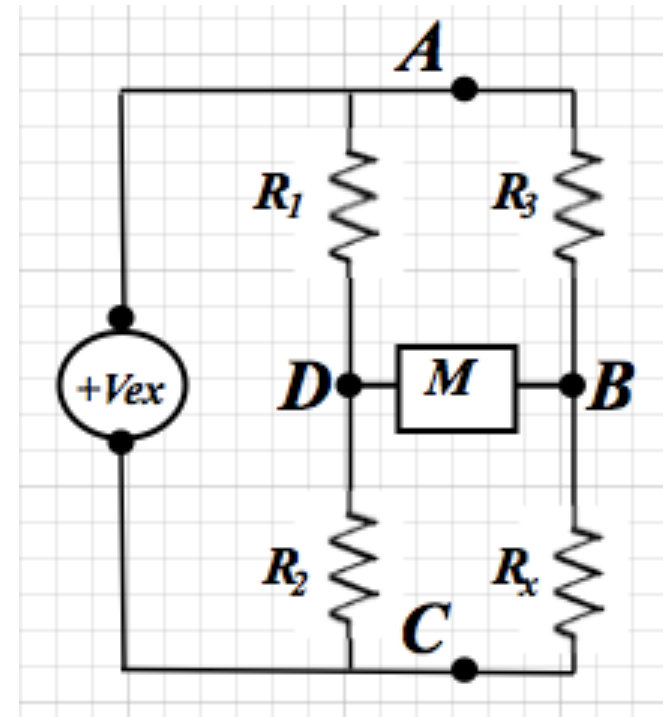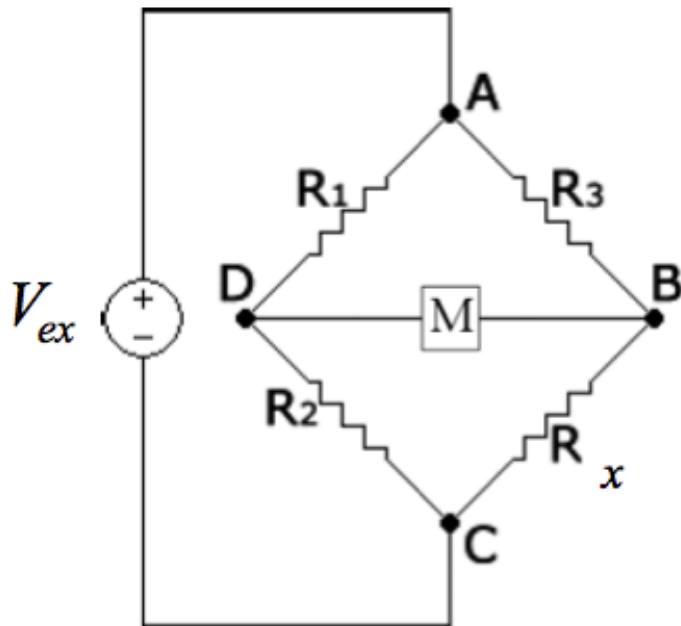- A Circuit that amplifies small changes in an unknown resistance R_x
 - Consider the circuit
- REDRAW CIRCUIT AS PAIR OF VOLTAGE DIVIDERS




Wheatstone Bridge (2)

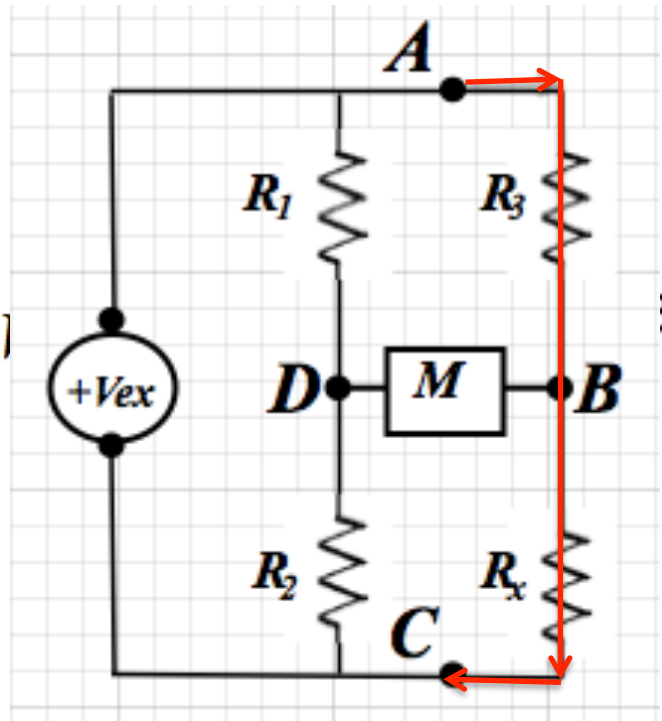

- What is Voltage Drop from *B* to *C*?

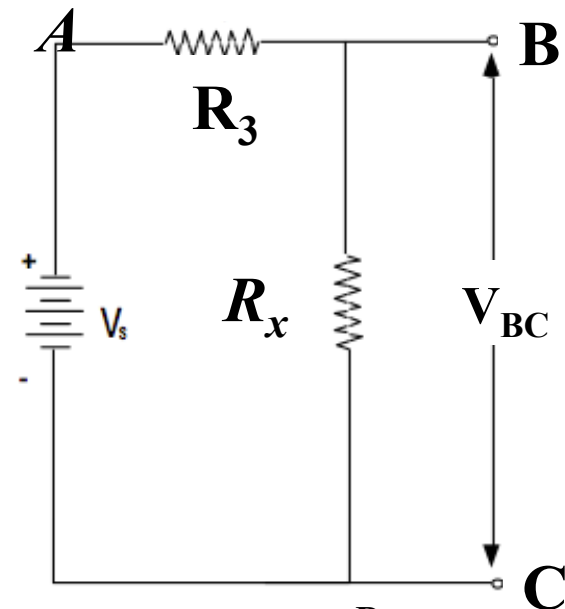...
*Looks like
Voltage
Divide Circuit*
...




$$V_{BC} = V_{ex} \frac{R_x}{R_3 + R_x}$$

$$I_3 = \frac{V_{ex}}{(R_3 + R_x)}$$

$$I_x = \frac{V_{ex}}{(R_3 + R_x)}$$

$$V_{BC} = V_{ex} \cdot \frac{R_x}{R_3 + R_x}$$

Wheatstone Bridge (3)

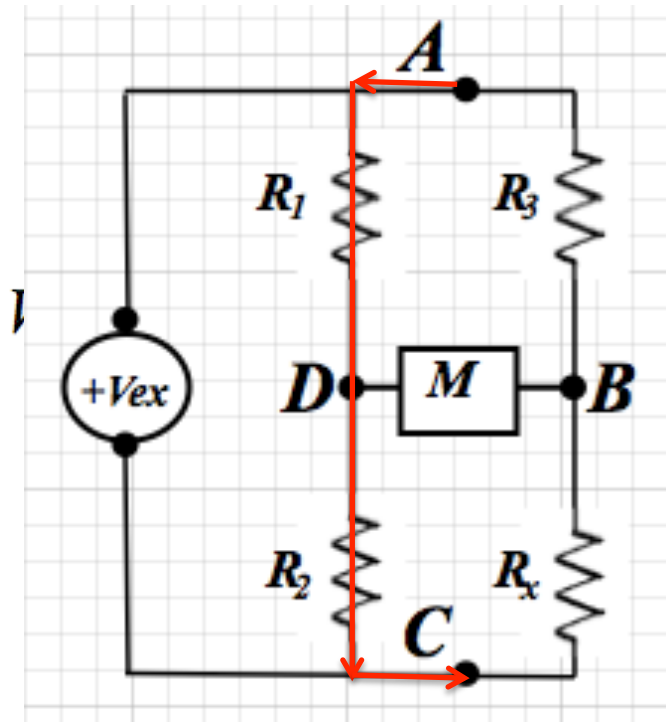


$$V_{DC} = V_{ex} \frac{R_2}{R_1 + R_2}$$

- What is Voltage Drop from *D* to *C*?



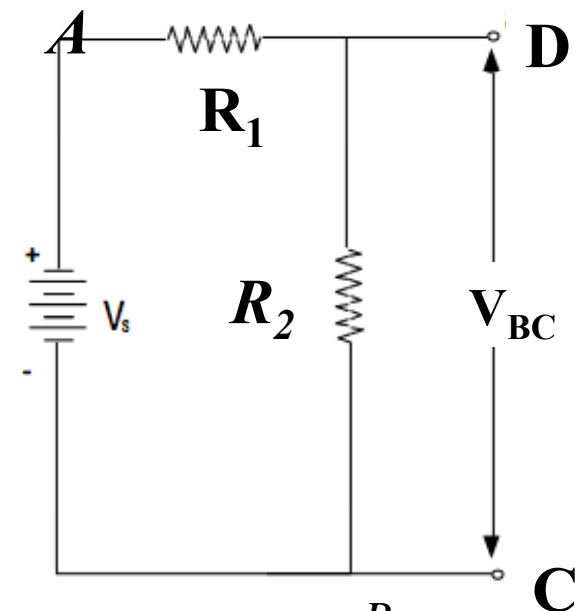...
Looks like
Voltage
Divide Circuit
...




$$V_{DC} = V_{ex} \cdot \frac{R_2}{R_1 + R_2}$$

$$I_1 = \frac{V_{ex}}{(R_1 + R_2)}$$

$$I_2 = \frac{V_{ex}}{(R_1 + R_2)}$$

Wheatstone Bridge (4)

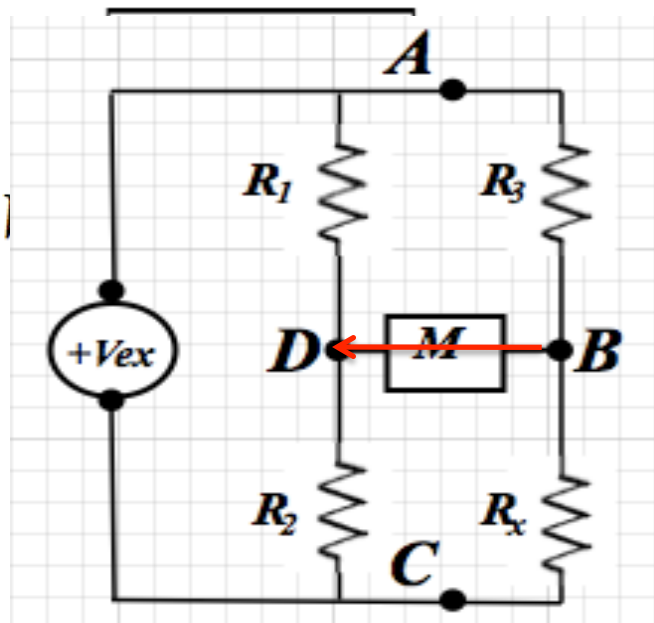

- What is Voltage Drop from *B* to *D*? (across meter)
- Assume Impedance of *M* is Very Large
> $M\Omega$, thus negligible current flows
across meter


$$V_{BD} = V_{BC} + V_{CD} = V_{BC} - V_{DC} =$$

$$V_{ex} \left(\frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2} \right) = V_{ex} \left(\frac{R_x(R_1 + R_2) - R_2(R_3 + R_x)}{(R_1 + R_2)(R_3 + R_x)} \right) =$$


$$V_{ex} \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)}$$

Resistance Bridge Summary (see Appendix I)

- *.. Infinite Meter Impedance*

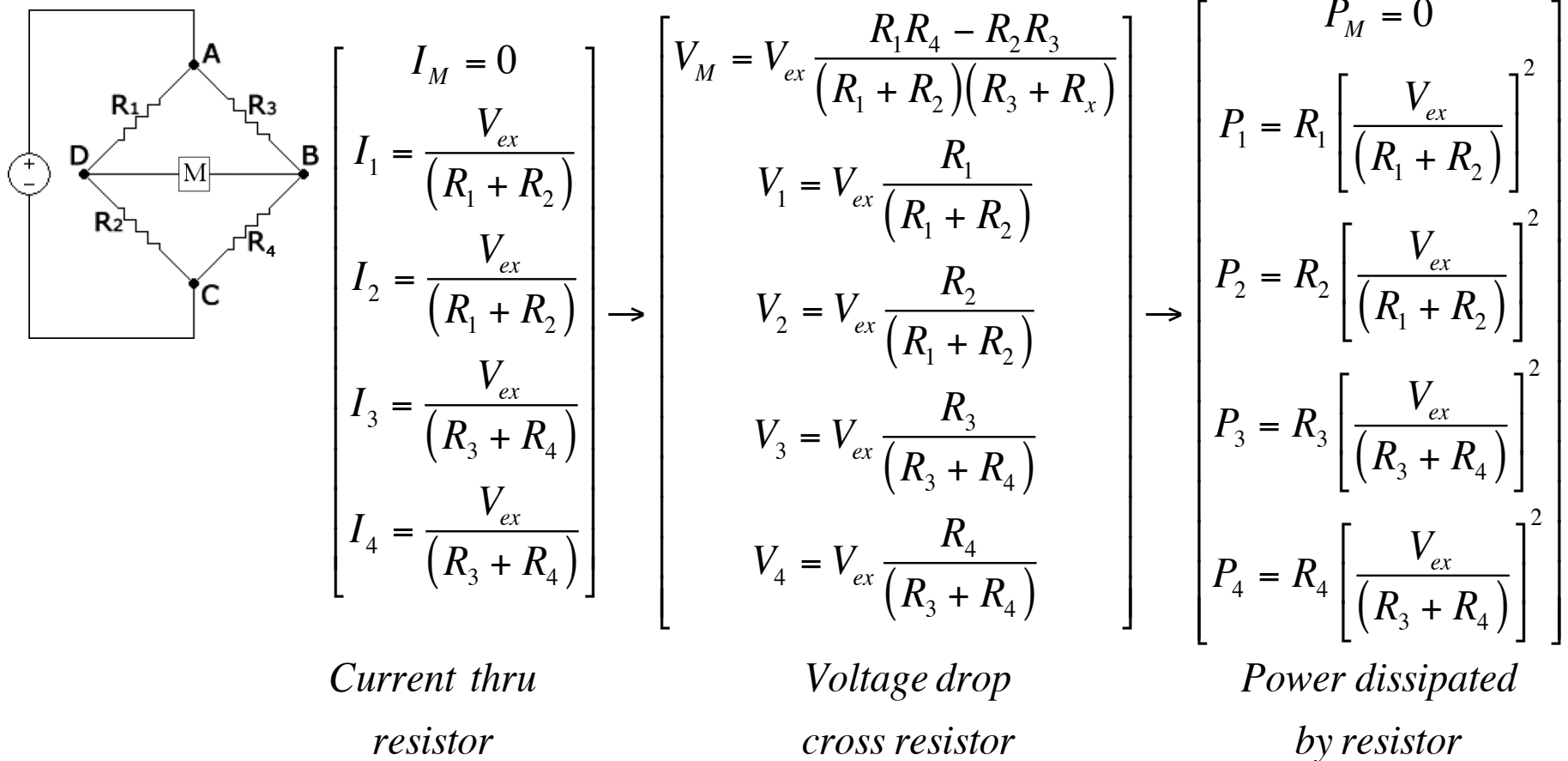

“Balanced” Bridge

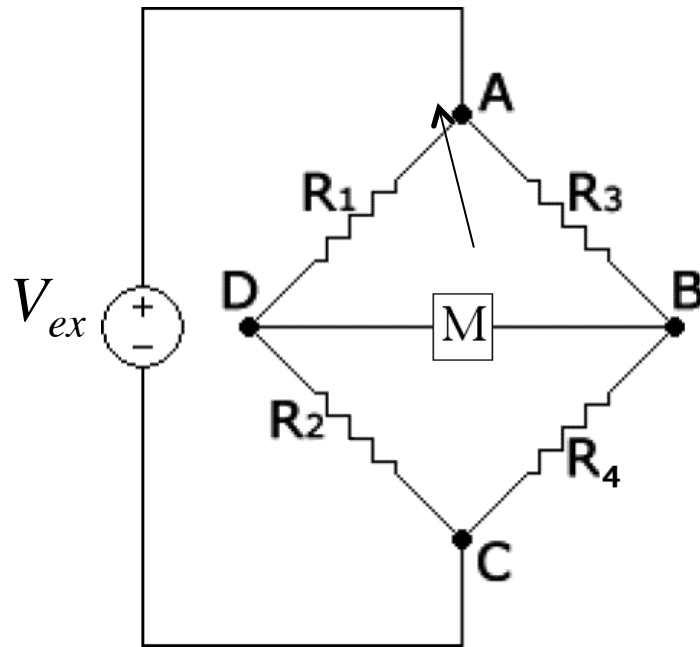

$$V_{Meter} = V_{ex} \frac{R_1 \cdot R_x - R_2 \cdot R_3}{(R_1 + R_2) \cdot (R_3 + R_x)}$$

- $R_1 \cdot R_x = R_2 \cdot R_3 \rightarrow V_{Meter} = 0$


- Condition for Balance, $V_M = 0$

$$\rightarrow \boxed{V_{meter} = 0 \rightarrow R_x = R_3 \frac{R_2}{R_1}}$$

- Good way to sense *unknown resistance*
- Adjust R_3 until $V_M = 0$


Your Lab Circuit

Figure 7.10 Simple Wheatstone bridge circuit

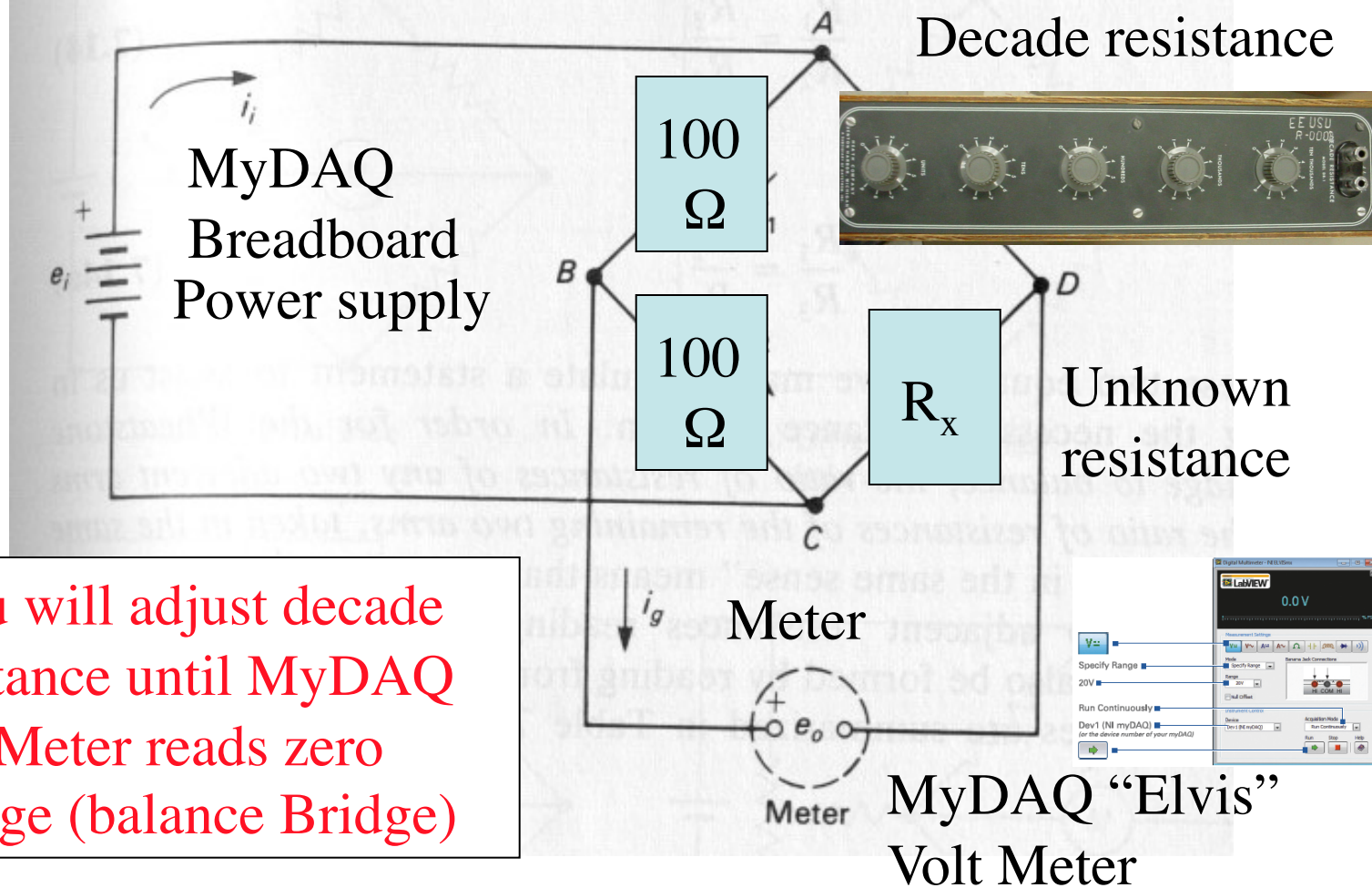

- You will adjust decade resistance until MyDAQ Volt Meter reads zero voltage (balance Bridge)

+ 5V Power Supply Using MyDAQ

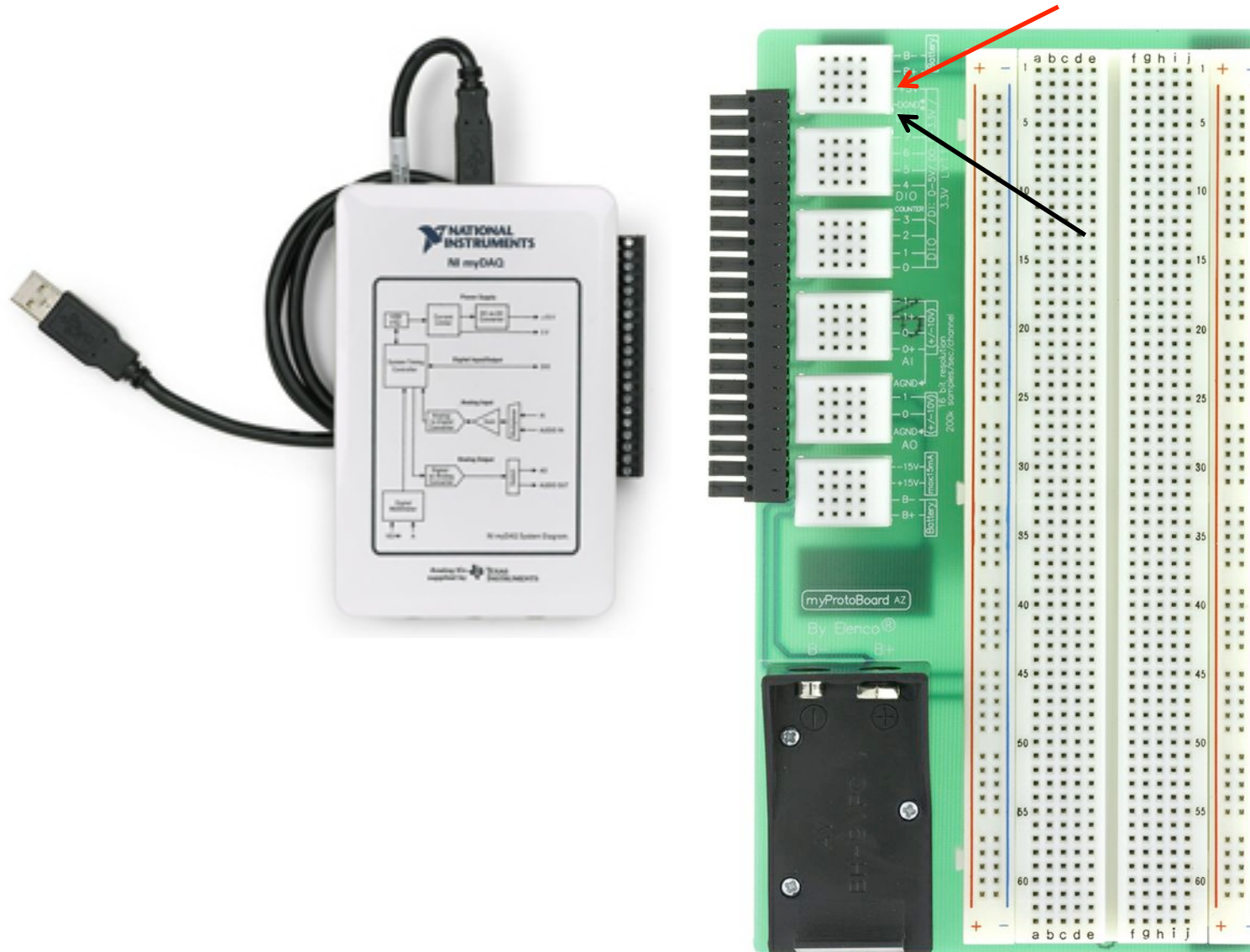

Decade Variable Resistor Box



There are 3 decade resistors that measure higher resistances, and 2 that measure lower resistances. They will be marked “High Resistance” or “Low Resistance”. These can create a resistance anywhere between 0.01 and 900 ohms in 0.01-ohm increments (Low Resistance), or 1 to 99,000 Ohms in 1-Ohm increments (High Resistance).

***Use the “High Resistance” Boxes for this Lab
1-Ohm resolution***

Elenco 1-Watt Resistor Substitution Box

You will also be using
Elenco 1-Watt Boxes for
half of your resistors
instead of decade
resistors



1-Ohm resolution



Elenco 1-Watt Resistor Substitution Box (2)


INTRODUCTION

The RS-500 Resistance Substitution Box is a convenient instrument for determining the desired resistance values in circuits under design or test. The resistance obtainable is from 0Ω to $11,111,110\Omega$ in 1 ohm steps. All resistors are precision 1% resistors.

OPERATION

All of the resistors are wired in series. A switch on the front panel shorts each resistor. Putting the switch in the ON (up) position removes the short and places the resistor across the output terminals. The two green binding posts serve as the output terminals. The black binding post is tied to the front panel. To place any resistance across the output terminals turn ON those switches that add up to the desired resistance. For example, for $5,071\Omega$, turn on the $3k\Omega$, $2k\Omega$, 40Ω , 30Ω and 1Ω switches.

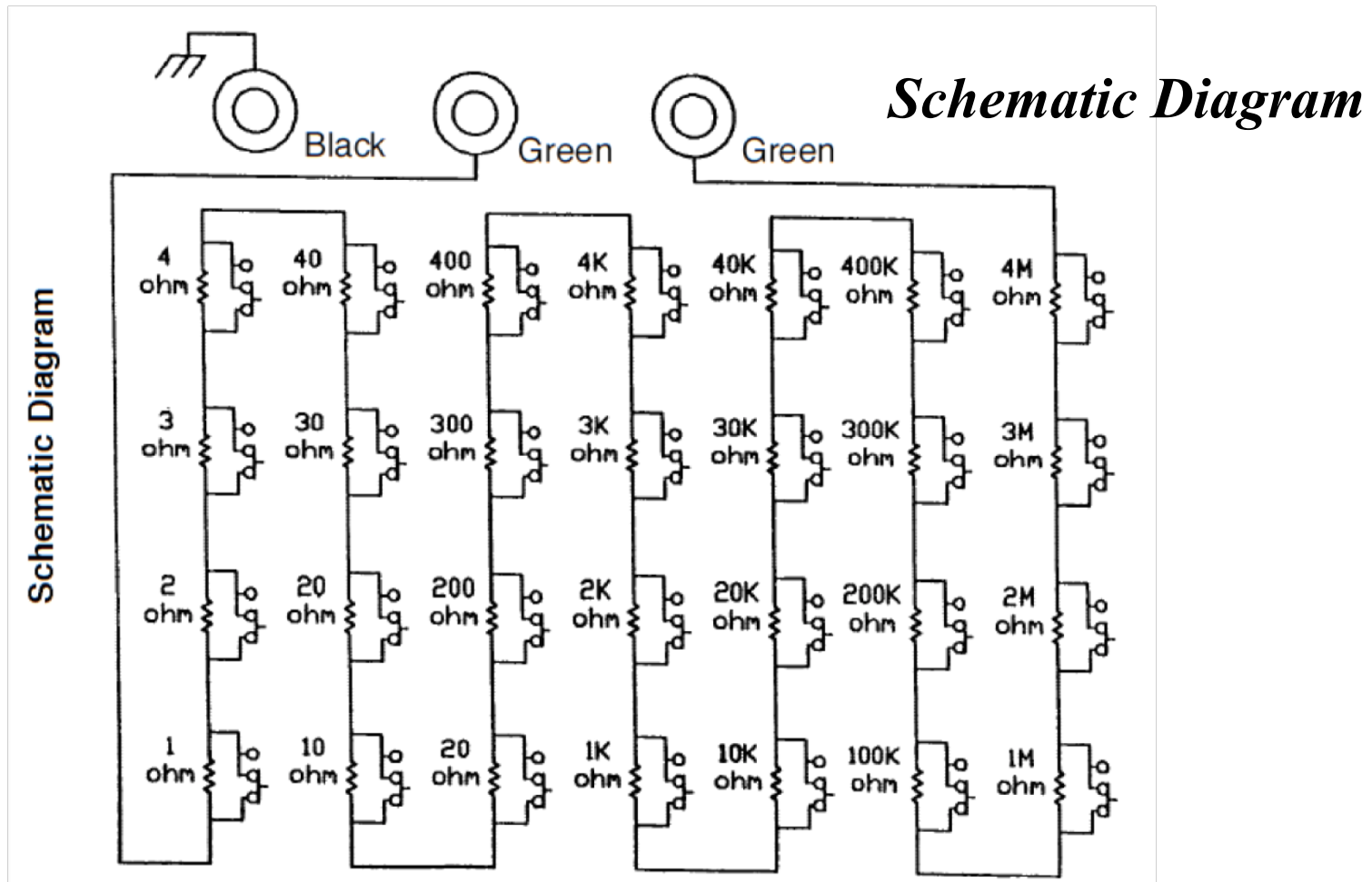Elenco 1-Watt Resistor Substitution Box (3)




Excitation Voltage ...

The Precision 100 Ω resistors (R_1, R_2) ($\pm 1\%$) Have a 1/4th watt capability



*... but to be safe ... we want
To limit power dissipated
To 1/16th watt safety factor 4*

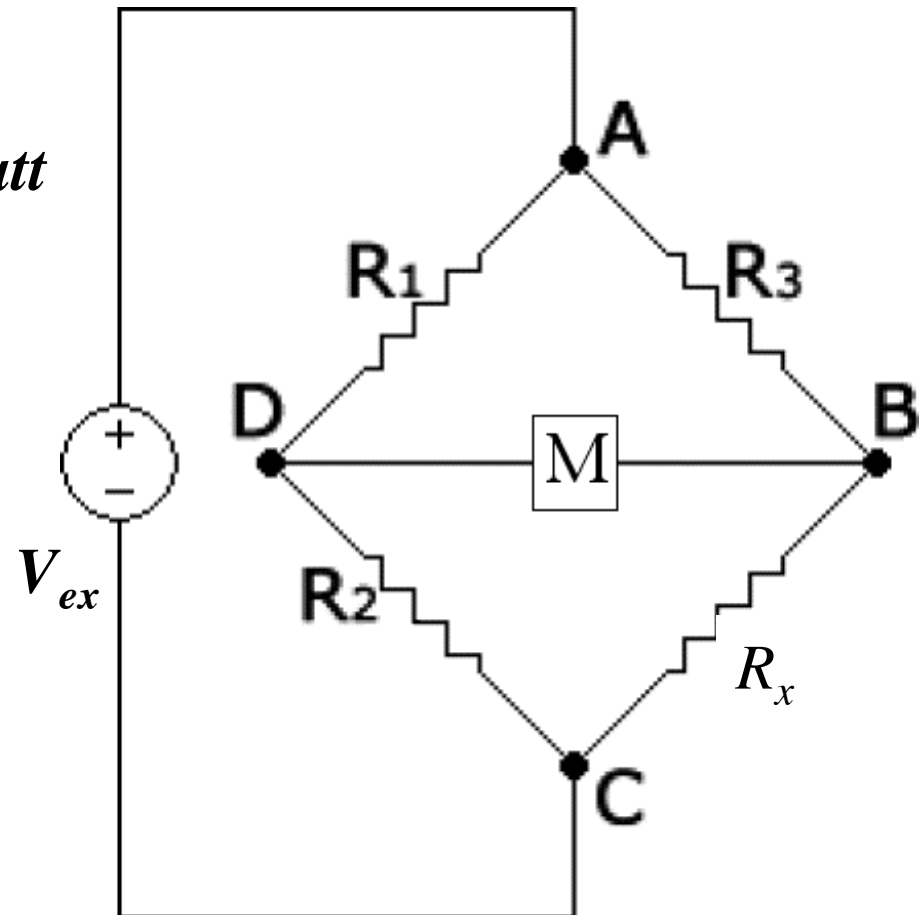*... Verify that $V_{ex} = 5\text{VDC}$
Will dissipate 1/16th watt in
 R_1, R_2*



Do the analysis before lab, and show it to the lab instructor before lab, staple it to this report.

Example Wheatstone Bridge on Breadboard

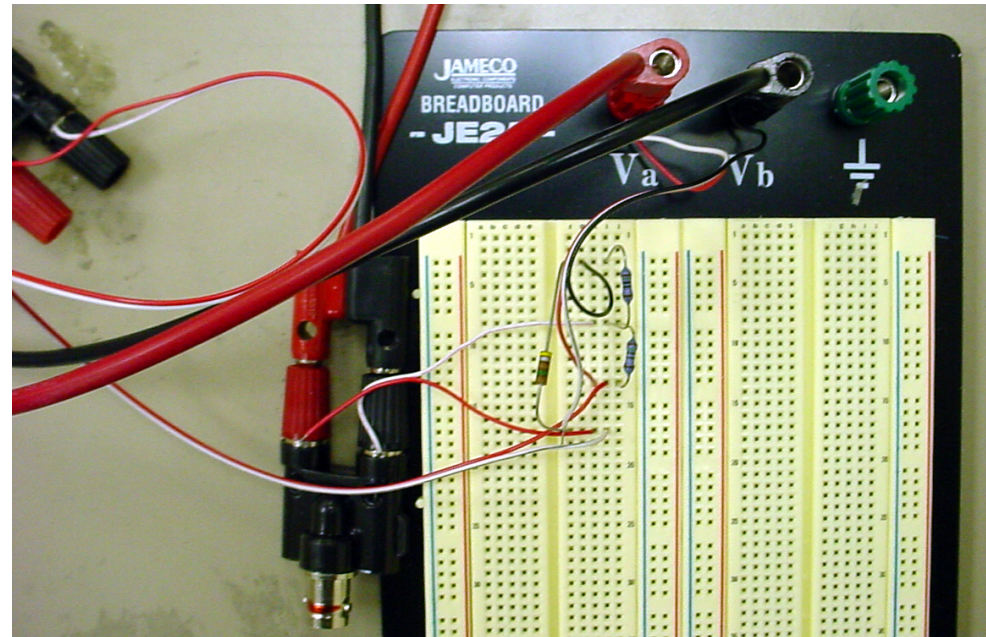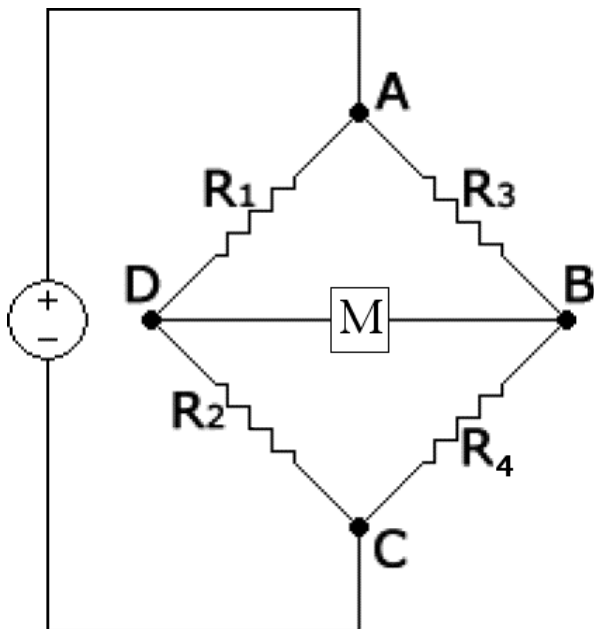

Resistance Table

Table I: Resistance Values

20 resistors
selected at
random ...

You will fill out
this table

.. Also
populate .xlsx
spreadsheet
(download
example from
Lab 5 section of
Web page)

Resistor Number	Nominal resistance (Ohms) (color code)	Spec Accuracy (%) (color code)	Actual resistance (Ohms)	R_i/R_{nom}

Also save data in Text.CSV format
(“comma, separated, values”)

Sample Statistics

- Sample Mean, Standard Deviation Estimates

“sample mean”

$$\bar{x} = \sum_{i=1}^n \frac{\left(\frac{R_i}{R_{nom}} \right)_i}{n}$$

$R_{nom} \rightarrow$ Value
from Resistor
Color Code

- Sample Standard Deviation Estimates

*“sample Std.
Dev.”*

$$S_x = \sqrt{\sum_{i=1}^n \frac{\left(\frac{R_{x_i}}{R_{nom}} - \bar{x} \right)^2}{n-1}}$$

$$\{x_n\} = \left\{ \begin{array}{c} \left(\frac{R}{R_{nom}} \right)_1 \\ \left(\frac{R}{R_{nom}} \right)_2 \\ \left(\frac{R}{R_{nom}} \right)_3 \\ \cdot \\ \cdot \\ \cdot \\ \left(\frac{R}{R_{nom}} \right)_{n-1} \\ \left(\frac{R}{R_{nom}} \right)_n \end{array} \right\}$$

Lab Report Summary (1)

- When you are finished, get together with the other 4 groups in your section and make a text file containing all 80 samples. . . .
- Using all the data, compute an estimate of the normalized mean and the standard deviation for *your 20 resistors*, and *the the pool of 80 resistors from your lab section*.
- Exchange spreadsheets and cut/paste to get all 80 resistors.
- Using only your 20 resistors, estimate the normalized mean, standard deviation, and the precision uncertainty of the mean to 95% confidence, ***assuming student-t distribution***
- Repeat Calculations using all 80 resistors for your section (95% confidence, ***assume Gauss distribution***)?
- Which set would you expect to have the smallest confidence interval??

- Down Load and Open Histogram Code ... See Link on Section 4 of web page


Section_4/Histogram_Folder.zip

**This VI will read your spreadsheet file ...
if saved on *Text.CSV* format**



- *Make a histogram of the data with all your 20 samples and 80 samples for you're a section and and attach it to this lab (screenshot)*

Lab Report Summary (3)

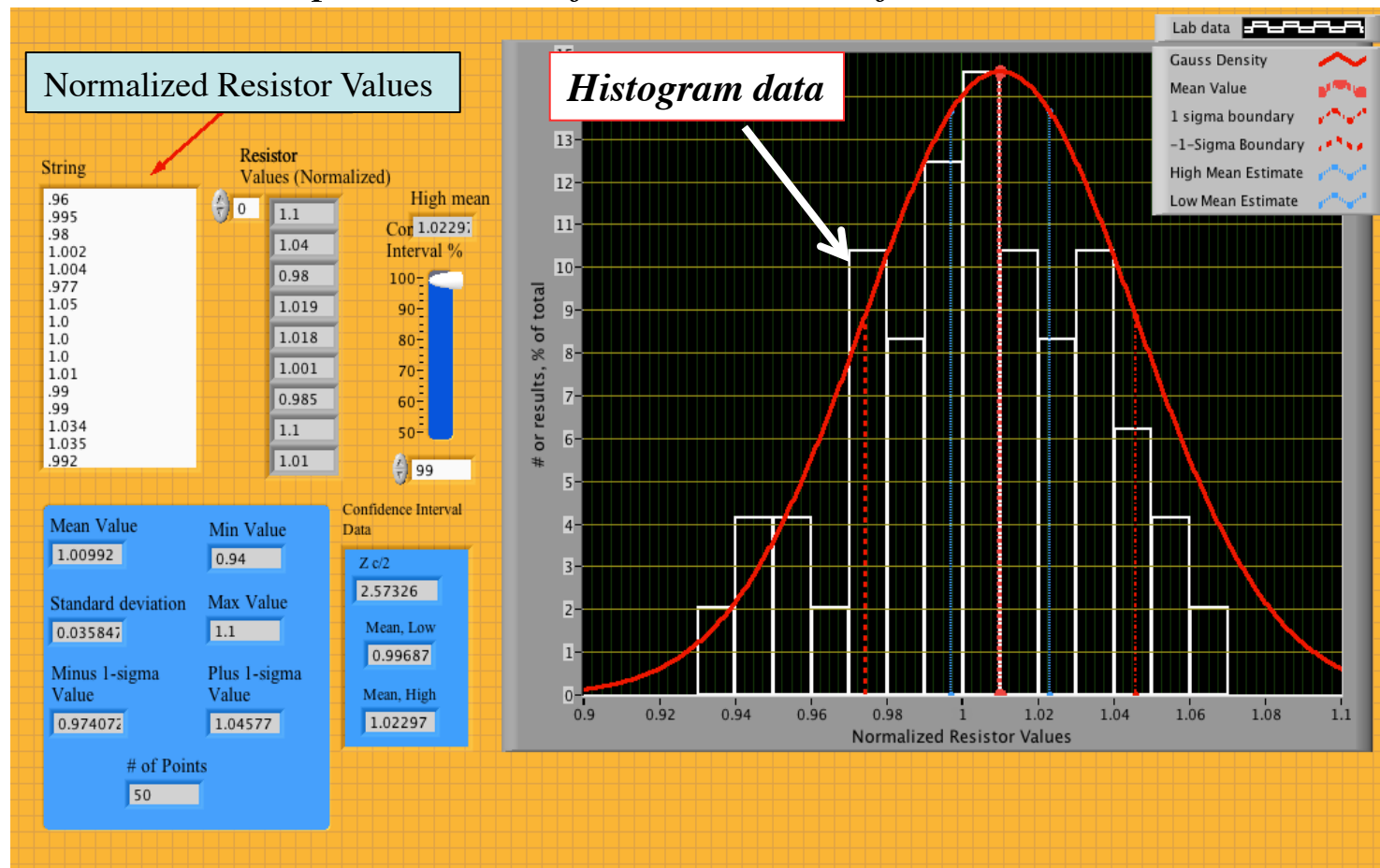- A histogram divides the range of possible values up into “bins” and plots the % of occurrences of values within that bin




Example Histograms

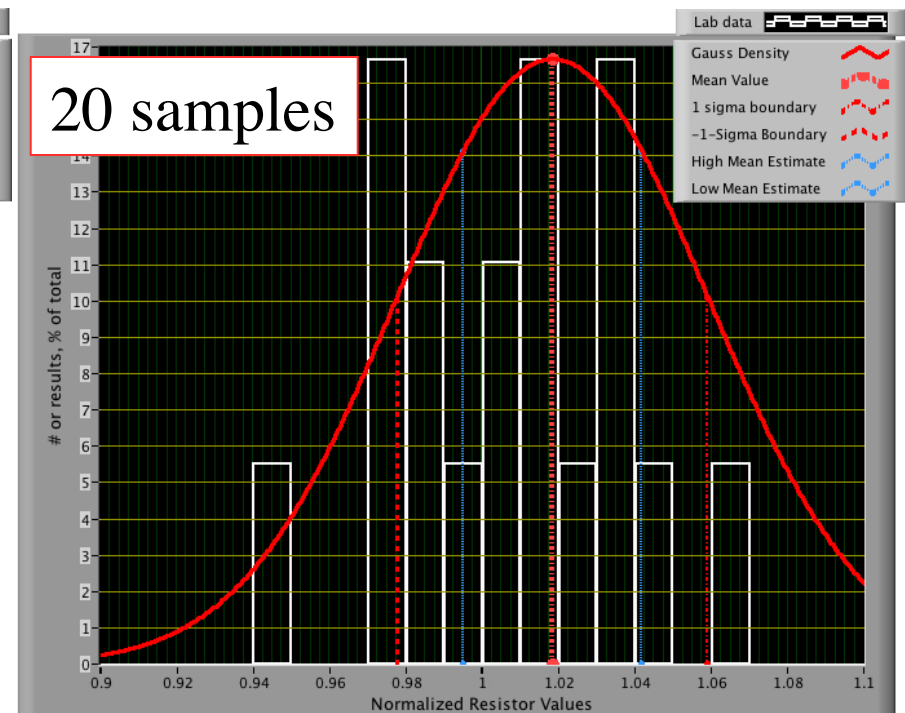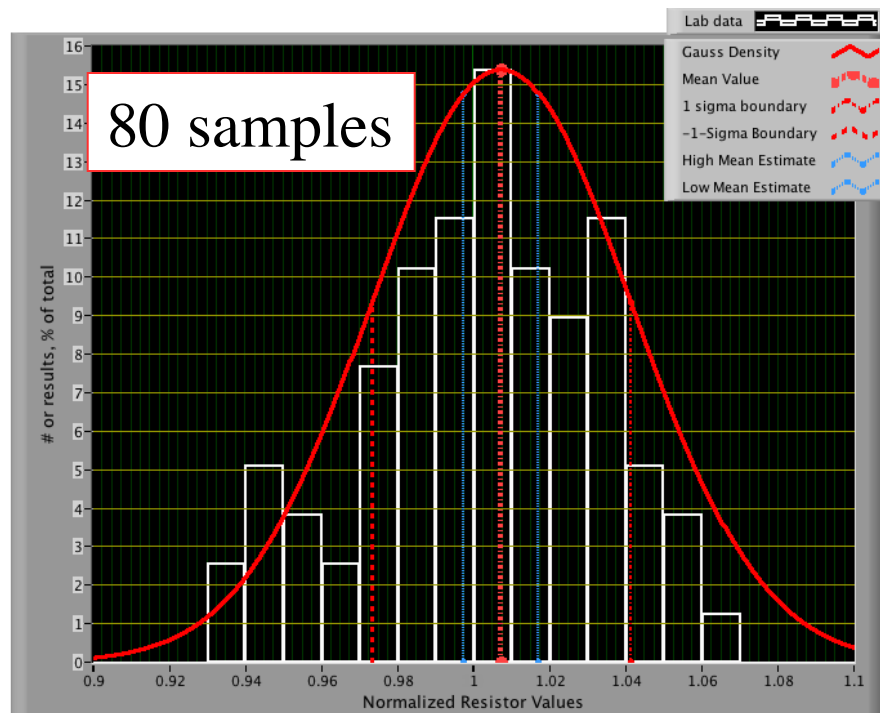

Error Analysis (1)

- Given the relationship between the known resistors and the unknown resistors, find the uncertainty in your measurement that is due to the uncertainty in the values of R_1 and R_2 (100Ω , $\pm 1\%$).
- **Assume that the precision error in decade resistor/Elenco Box is very small.** ... However their setting resolution is only *1 Ohm*. **Account for this value in the total error budget.**
- How do you account for the fact that the “Elvis” voltmeter only has two digits of precision in voltage?... *see next page*
- Compare this calculated value to the standard deviation you computed
based on your 20 resistors
based on all 80 resistors
- Comment on the manufacturer’s claim as to the accuracy of these resistors.

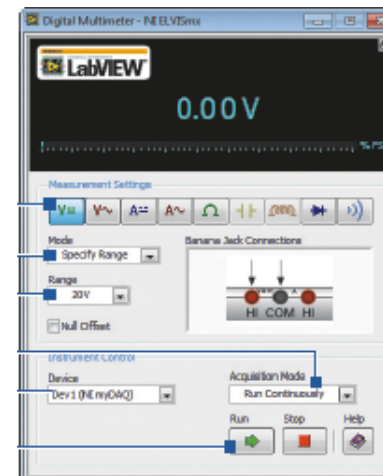

Uncertainty Analysis (6)

- How do you account for the fact that the meter only has two digits of precision

$$\delta V_M \approx \frac{\partial V_M}{\partial R_x} \cdot \delta R_x \rightarrow \boxed{\delta R_x \approx \frac{\delta V_M}{\partial V_M / \partial R_x}}$$

$$V_M = V_{ex} \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)} \rightarrow$$

$$\frac{\partial V_M}{\partial R_x} = V_{ex} \left[\frac{R_1}{(R_1 + R_2)(R_3 + R_x)} - \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{R_1(R_3 + R_x) - R_1 R_x + R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] =$$

$$V_{ex} \left[\frac{R_1 R_3 + R_2 R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{(R_1 + R_2) \cdot R_3}{(R_1 + R_2)(R_3 + R_x)^2} \right] = V_{ex} \left[\frac{R_3}{(R_3 + R_x)^2} \right]$$

Uncertainty Analysis (7)


- How do you account for the fact that the meter only has two digits of precision

$$\delta R_x \approx \frac{\delta V_M}{\partial V_M / \partial R_x} \rightarrow \frac{\partial V_M}{\partial R_x} = V_{ex} \left[\frac{R_3}{(R_3 + R_x)^2} \right] \rightarrow R_x \approx \frac{\delta V_M}{V_{ex} \left[\frac{R_3}{(R_3 + R_x)^2} \right]} =$$

$$\frac{(R_3 + R_x)^2}{R_3} \left[\frac{\delta V_M}{V_{ex}} \right] = R_3 \cdot \left(1 + \frac{R_x}{R_3} \right)^2 \left[\frac{\delta V_M}{V_{ex}} \right] \rightarrow \left[\frac{\delta R_x}{R_x} \right]_{\text{Meter}} = \left(\frac{R_3}{R_x} \right) \cdot \left(1 + \frac{R_x}{R_3} \right)^2 \left[\frac{\delta V_M}{V_{ex}} \right]$$

- But For a balanced bridge
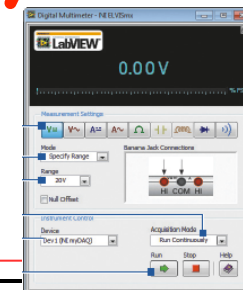
$$R_x = \left(\frac{R_2 R_3}{R_1} \right) \rightarrow \frac{R_3}{R_x} = \frac{R_1}{R_2} \approx \frac{100\Omega}{100\Omega} = 1$$



$$\left[\frac{\delta R_x}{R_x} \right]_{\text{Meter}} \approx 4 \frac{\delta V_M}{V_{ex}}$$

Uncertainty Analysis (8)

- Precision Uncertainty

$$R_x = f(R_1, R_2, R_3) = \frac{R_2 R_3}{R_1}$$

$$\delta R_x = \sqrt{\left(\frac{\partial f}{\partial R_1}\right)^2 \cdot \delta R_1^2 + \left(\frac{\partial f}{\partial R_2}\right)^2 \cdot \delta R_2^2 + \left(\frac{\partial f}{\partial R_3}\right)^2 \cdot \delta R_3^2}$$

$$\left[\begin{array}{l} \frac{\partial f}{\partial R_1} = -\frac{R_2 R_3}{R_1^2} \\ \frac{\partial f}{\partial R_2} = \frac{R_3}{R_1} \\ \frac{\partial f}{\partial R_3} = \frac{R_2}{R_1} \end{array} \right] \rightarrow \delta R_x = \sqrt{\left(\frac{R_2 R_3}{R_1^2}\right)^2 \cdot \delta R_1^2 + \left(\frac{R_3}{R_1}\right)^2 \cdot \delta R_2^2 + \left(\frac{R_2}{R_1}\right)^2 \cdot \delta R_3^2}$$

Uncertainty Analysis (8)

- Precision Uncertainty

$$\text{Normalize} \rightarrow \frac{\delta R_x}{R_x} = \frac{1}{\frac{R_2 R_3}{R_1}} \cdot \sqrt{\left(\frac{R_2 R_3}{R_1^2}\right)^2 \cdot \delta R_1^2 + \left(\frac{R_3}{R_1}\right)^2 \cdot \delta R_2^2 + \left(\frac{R_2}{R_1}\right)^2 \cdot \delta R_3^2} = \sqrt{\left(\frac{\delta R_1}{R_1}\right)^2 + \left(\frac{\delta R_2}{R_2}\right)^2 + \left(\frac{\delta R_3}{R_3}\right)^2}$$

- **Total Uncertainty** ... Root Sum Square Precision and Resolution Uncertainty


$$\rightarrow \frac{\delta R_x}{R_x} = \sqrt{\underbrace{\left(\frac{\delta R_1}{R_1}\right)^2 + \left(\frac{\delta R_2}{R_2}\right)^2 + \left(\frac{\delta R_3}{R_3}\right)^2}_{\text{Precision Uncertainty}} + \underbrace{\left(\frac{\delta R_x}{R_x}\right)^2}_{\text{Meter Resolution}}}$$

Precision Uncertainty

***How do you account for Resolution
Of only 1 Ohm on Decade Resistor/Elenco Box?***

Appendix

Histogram Plots Using Labview

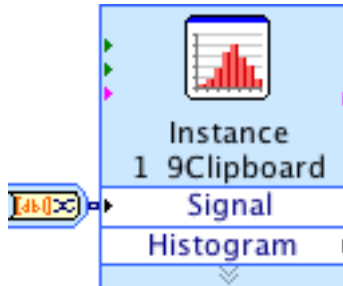

Using Labview for Histogram Plot (2)


Waveform Graphs:

Wire data directly to waveform graph:



Y Array	Resulting Graph
1D	Single Plot
WDT	Single Plot
2D	Multiplot

WDT (Waveform Data Type) includes timing info.
Others default to 0 for x_0 and 1 for Δx .

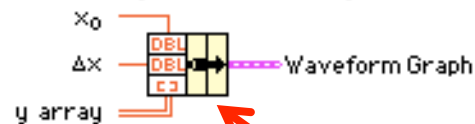Combine timing information using a bundle node:




See the example: Waveform Graph.vi

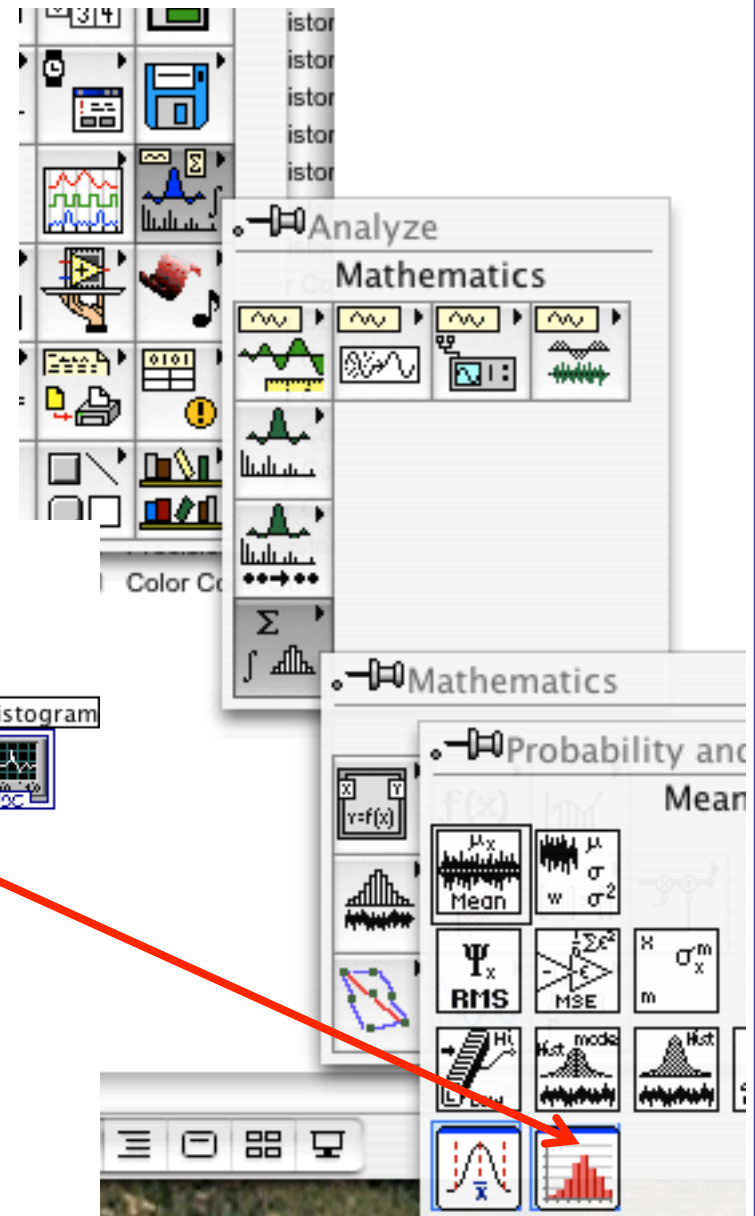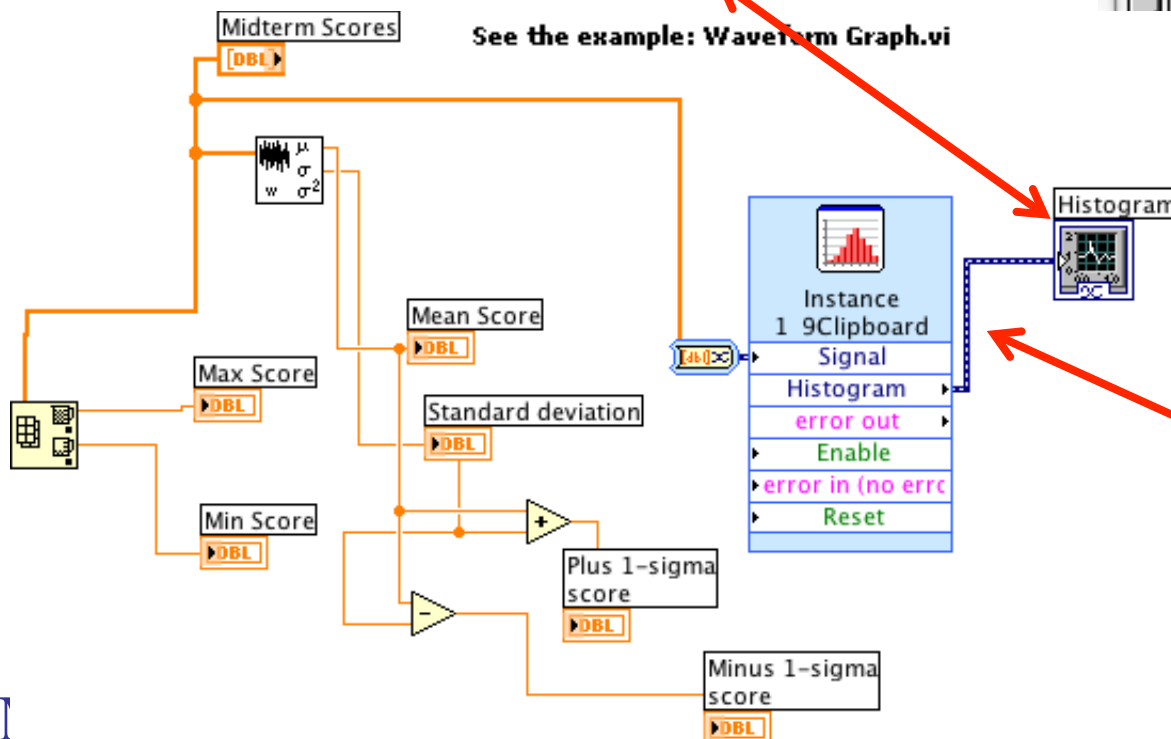


Using Labview for Histogram Plot (3)

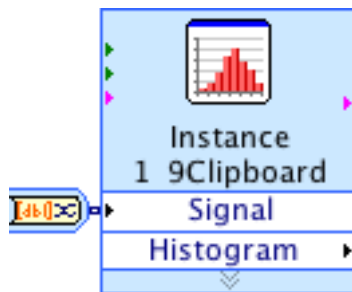
Set bin intervals
And min/max
On front panel



“double click”

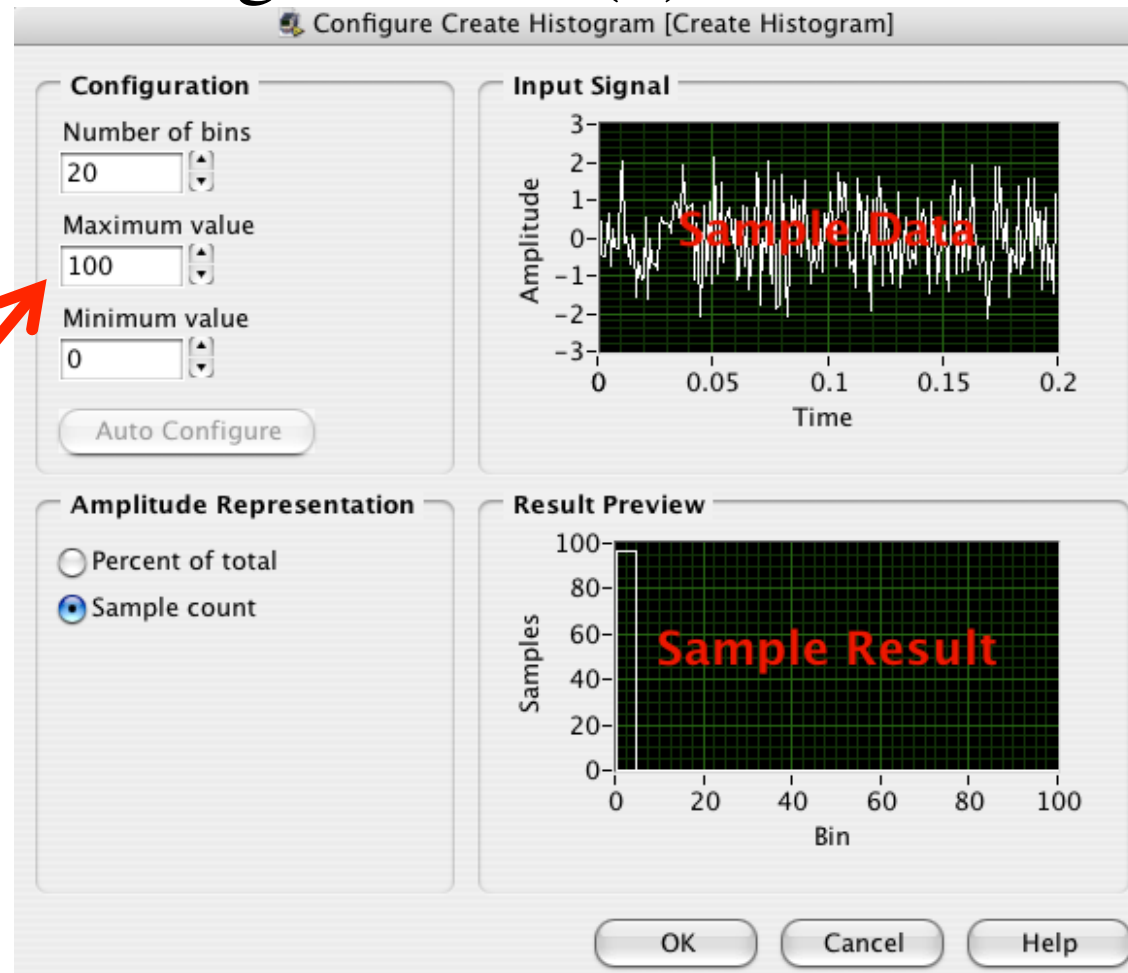

Wheatstone Bridge (3)

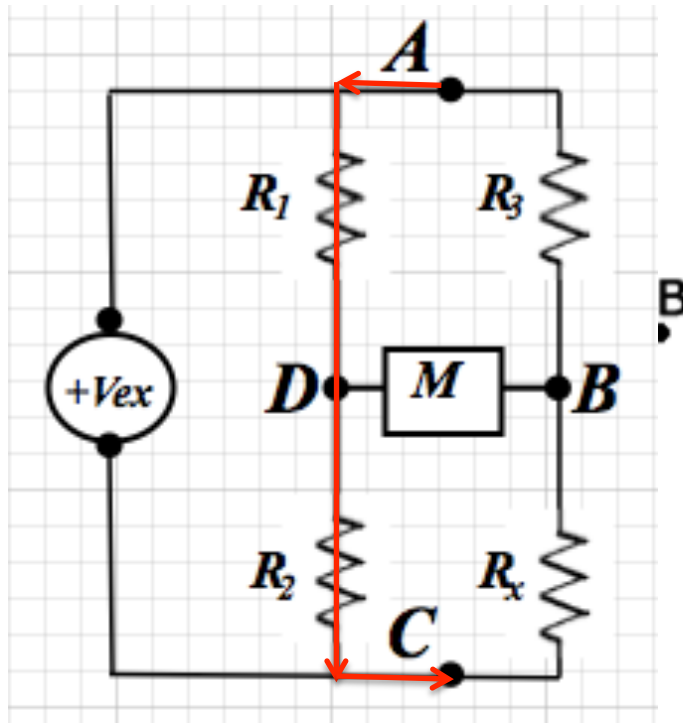

Watts Dissipated in First Leg of Bridge

$$I_{R_1, R_2} = \frac{V_{ex}}{R_1 + R_2} = \frac{5_V}{200_{\Omega}} = 0.025_{Amps}$$

$$P_{R_1} = (I_{R_1, R_2})^2 \cdot R_1 = (0.025_{Amps})^2 \cdot 100_{\Omega} = 0.0625_{Watts}$$

$$P_{R_2} = (I_{R_1, R_2})^2 \cdot R_2 = (0.025_{Amps})^2 \cdot 100_{\Omega} = 0.0625_{Watts}$$

$$V_{DC} = V_{ex} \frac{R_2}{R_1 + R_2}$$

Precision Uncertainty Analysis (2)

Standard Error of
the Sample Mean

$$S_{\bar{x}} = \frac{S_x}{\sqrt{n}}$$

• Confidence Interval
for Sample Mean Estimate

$$\bar{x} - z_{c/2} \frac{S_x}{\sqrt{n}} < \mu < \bar{x} + z_{c/2} \frac{S_x}{\sqrt{n}}$$


95% Confidence Interval --->

$$0.95 = P_{(\bar{x})} = \frac{1}{\sqrt{2\pi} \cdot \sigma_{\bar{x}}} \int_{z=-\frac{(\bar{x}-\mu_{\bar{x}})^2}{\sigma_{\bar{x}}^2}}^{z=\frac{(\bar{x}-\mu_{\bar{x}})^2}{\sigma_{\bar{x}}^2}} \left(e^{-\frac{(x-\mu)^2}{2\sigma^2}} \right) dx$$

“Gauss Distribution”

MAE 3340 INSTRUMENTATION SYSTEMS

Confidence Interval

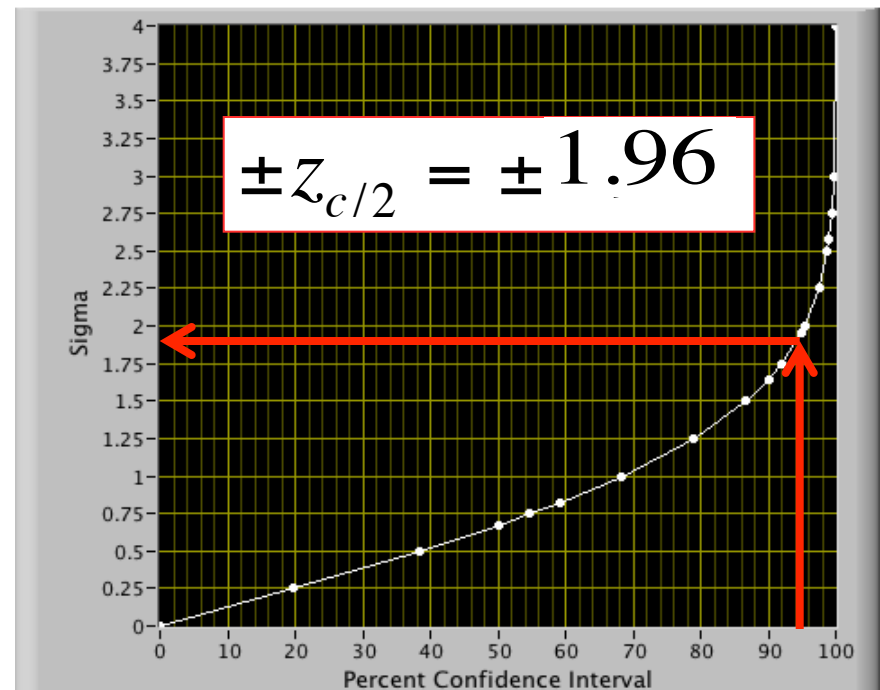

Precision Uncertainty Analysis (3)

$$\rightarrow \text{let } \dots z = \frac{\bar{x} - \mu_{\bar{x}}}{\sigma_{\bar{x}}} \rightarrow$$

$$0.95 = P_{(x)} = \frac{1}{\sqrt{2\pi} \cdot \sigma_{\bar{x}}} \cdot \int_{z_{c/2}}^{z_{c/2}} (e^{-z^2/2}) dz$$

Integral data

Xmin (standard deviations)

$\frac{z}{\sigma}$ -1.958


Xmax (standard deviations)

$\frac{z}{\sigma}$ 1.958

Points in Integrator

$\frac{z}{\sigma}$ 1000

Probability density

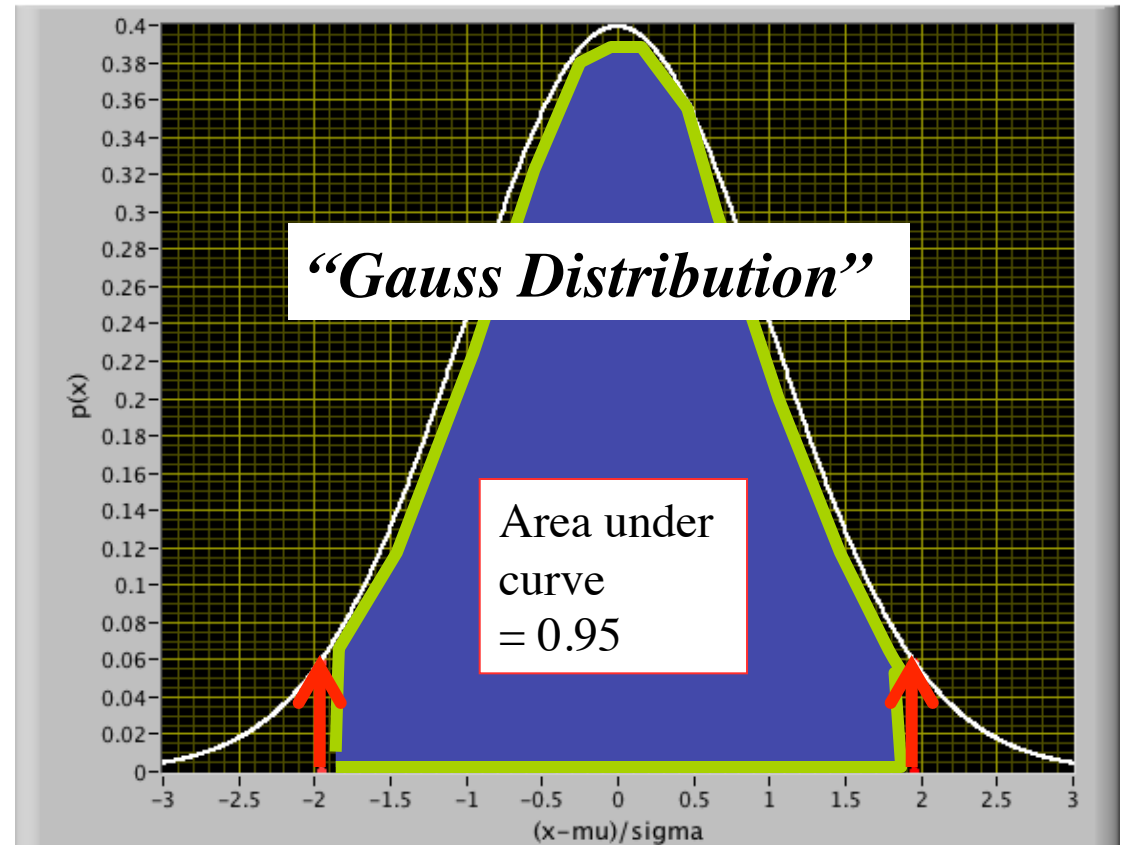

$$\pm z_{c/2} = \pm 1.96$$

Precision Uncertainty Analysis (4)

$$\pm Z_{c/2} = \pm 1.96$$

$$\bar{x} - \left(1.96 \cdot \frac{S_x}{\sqrt{n}} \right) < \mu_{\bar{x}} < \bar{x} + \left(1.96 \cdot \frac{S_x}{\sqrt{n}} \right) \dots$$

or... $\mu_{\bar{x}} = \bar{x} \pm \left(1.96 \frac{S_x}{\sqrt{n}} \right)$

- precision uncertainty
...in mean estimate

*Assuming Gauss
Distribution*

Probability density

