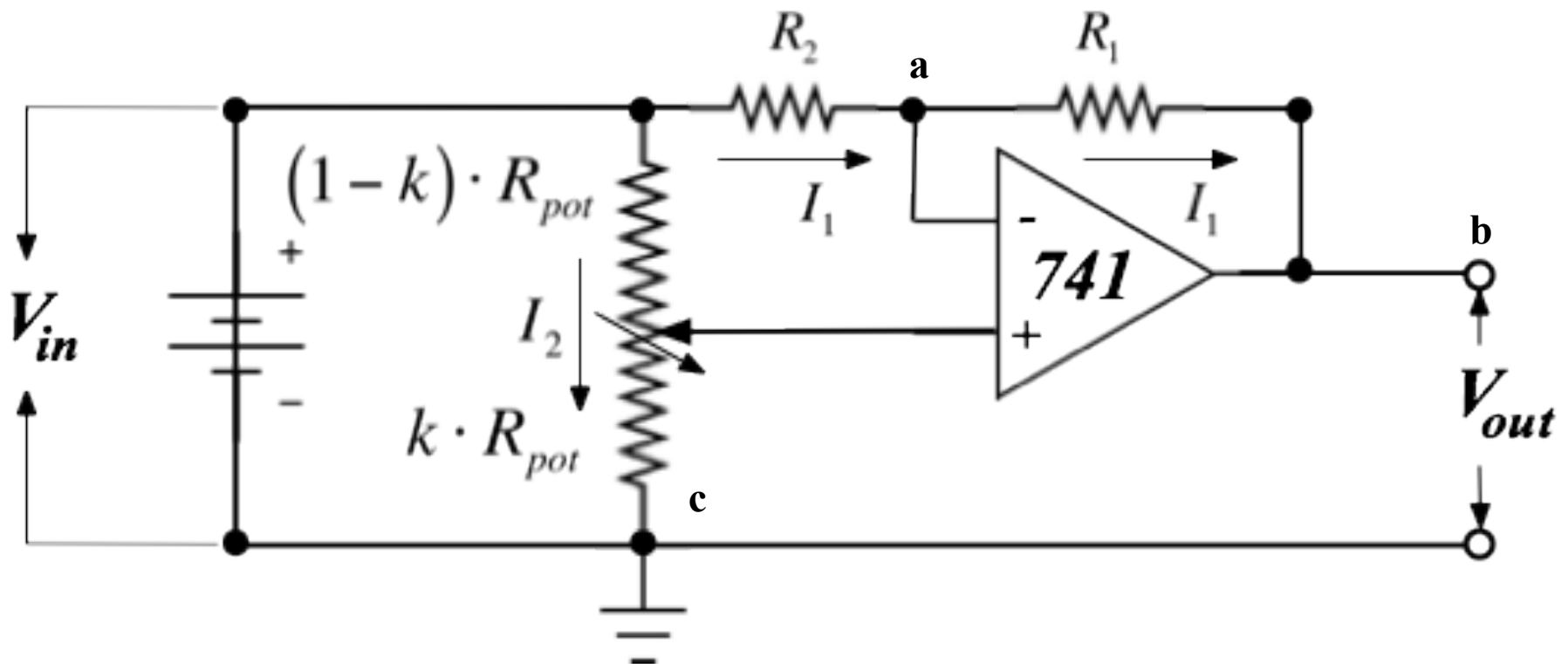


Laboratory 7: Introduction to Op-Amps and High Impedance Amplifier Circuits

- *Lab Objectives:*

- Understand Op-Amp Properties
- Understand Potentiometers and Variable Resistances
- Build a Variable Gain Inverting Amplifier
- Understand “Virtual Ground” Concept ... and Associated Grounding Issues

You Will Build This Amplifier Circuit



National Semiconductor 741 Op-Amp ⁽¹⁾

- The 741 is the godfather of all Op-Amps.
- Although many other designs beat it for speed, low noise, etc, it works well as a general purpose device.
- One of its advantages is that it is *compensated* to ensure that under most circumstances it won't produce unwanted spurious oscillations.
- This property makes 741 easy to use, but the down-side is the poor speed/gain performance compared to more modern op-amps.


NS Operational Amplifier (3)

Very common, available as a chip and has the following characteristics:

- 1) High input impedance (won't draw current)
- 2) Low output impedance (will deliver current w/o affecting voltage)
- 3) High internal gain ($A > 10^5$)

$$V_{out} = A[V_+ - V_-] \dots A \rightarrow \infty$$

$$\rightarrow V_+ = V_-$$

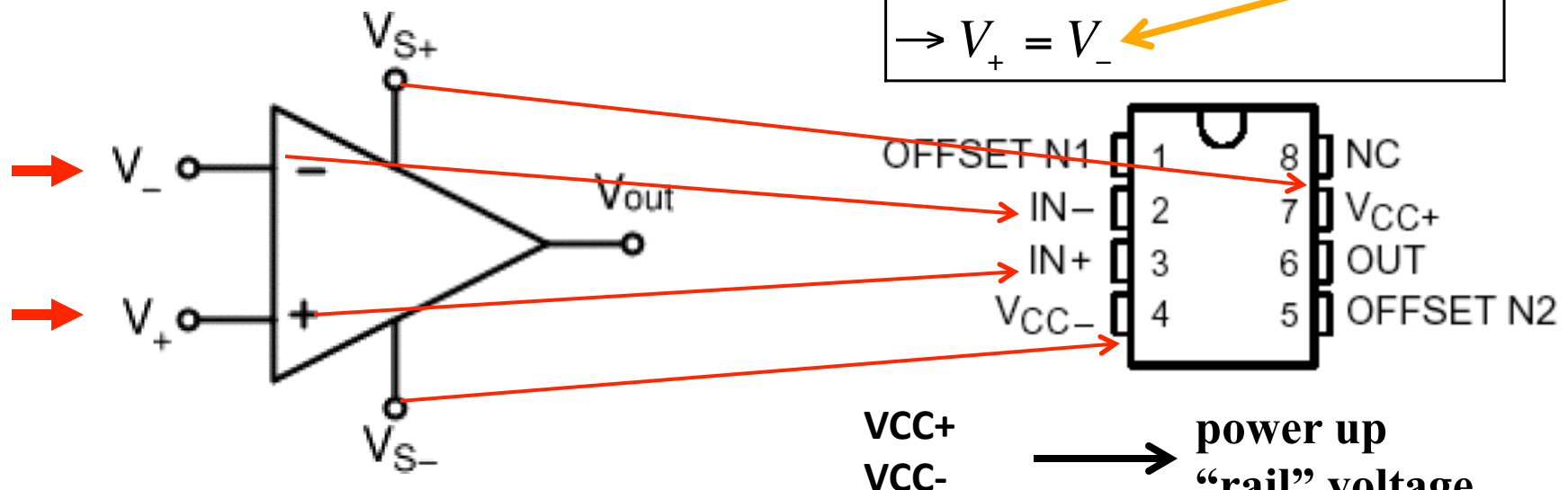

VCC+
VCC-


power up
"rail" voltage

Circuit Analysis (1)

Idealized OpAmp

$$V_{out} = A \cdot (V^+ - V^-)$$
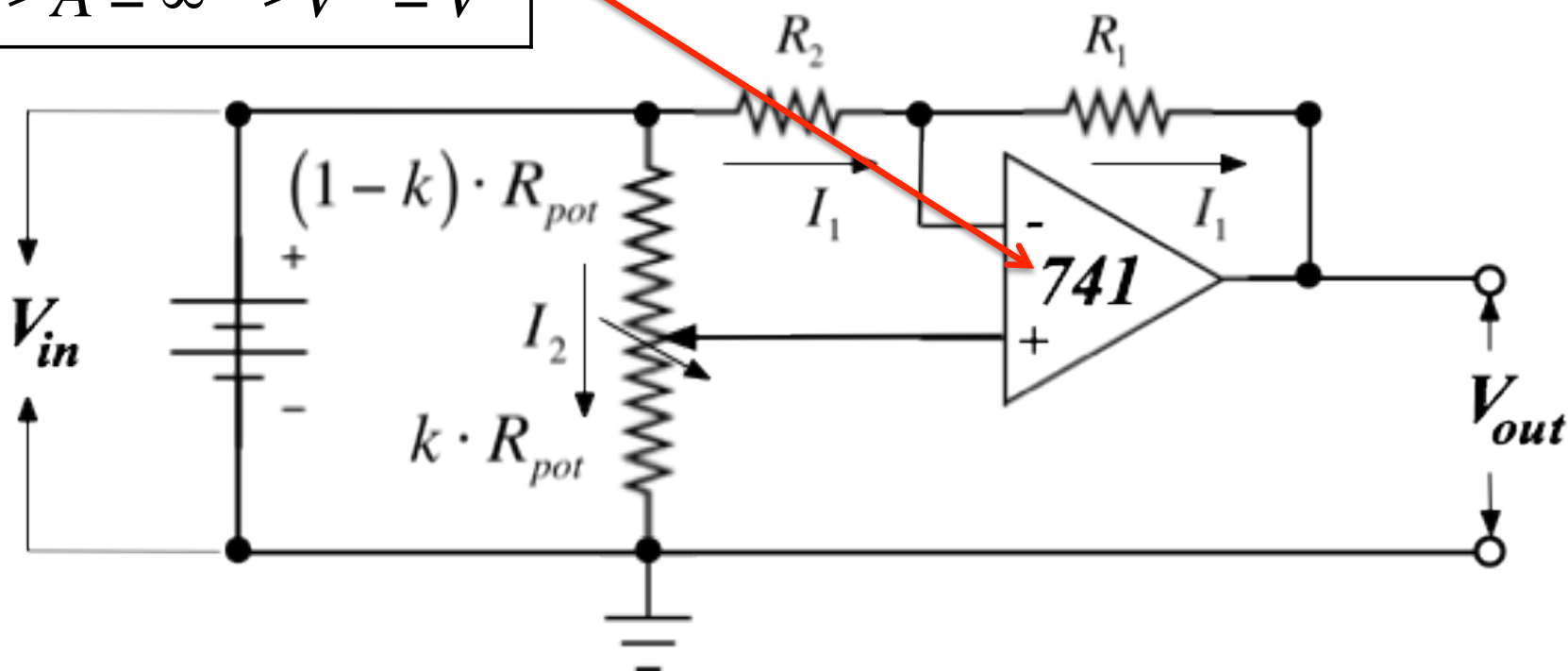
$$\rightarrow A = \infty \rightarrow V^+ = V^-$$




Circuit Analysis (2)

Across OpAmp Terminals :

$$V^{-} - V_{out} = R_1 I_1$$

$$V_{in} - V^{+} = (1 - k) \cdot R_{pot} \cdot I_2 \rightarrow V_{out} + R_1 I_1 = V_{in} - (1 - k) \cdot R_{pot} \cdot I_2$$


$$V^{-} = V^{+}$$

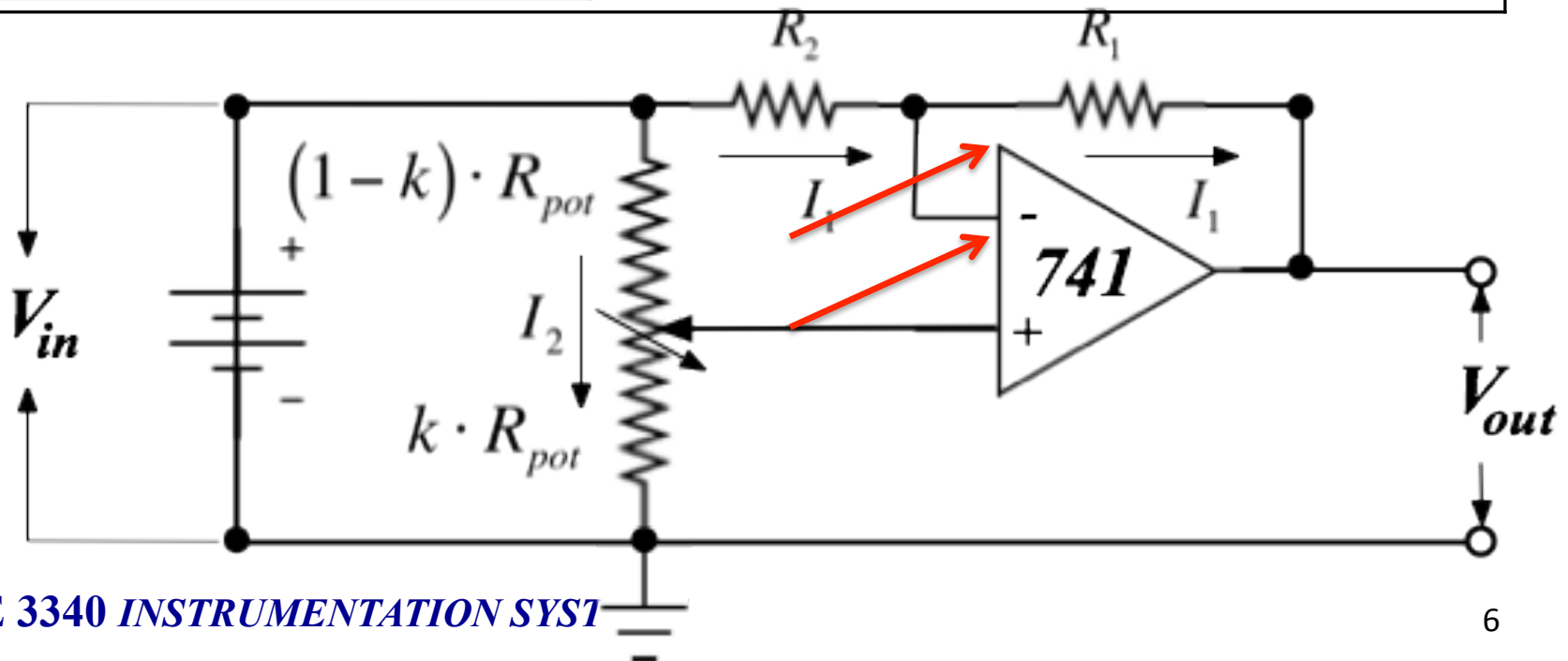

Circuit Analysis (3)

Across Potentiometer :
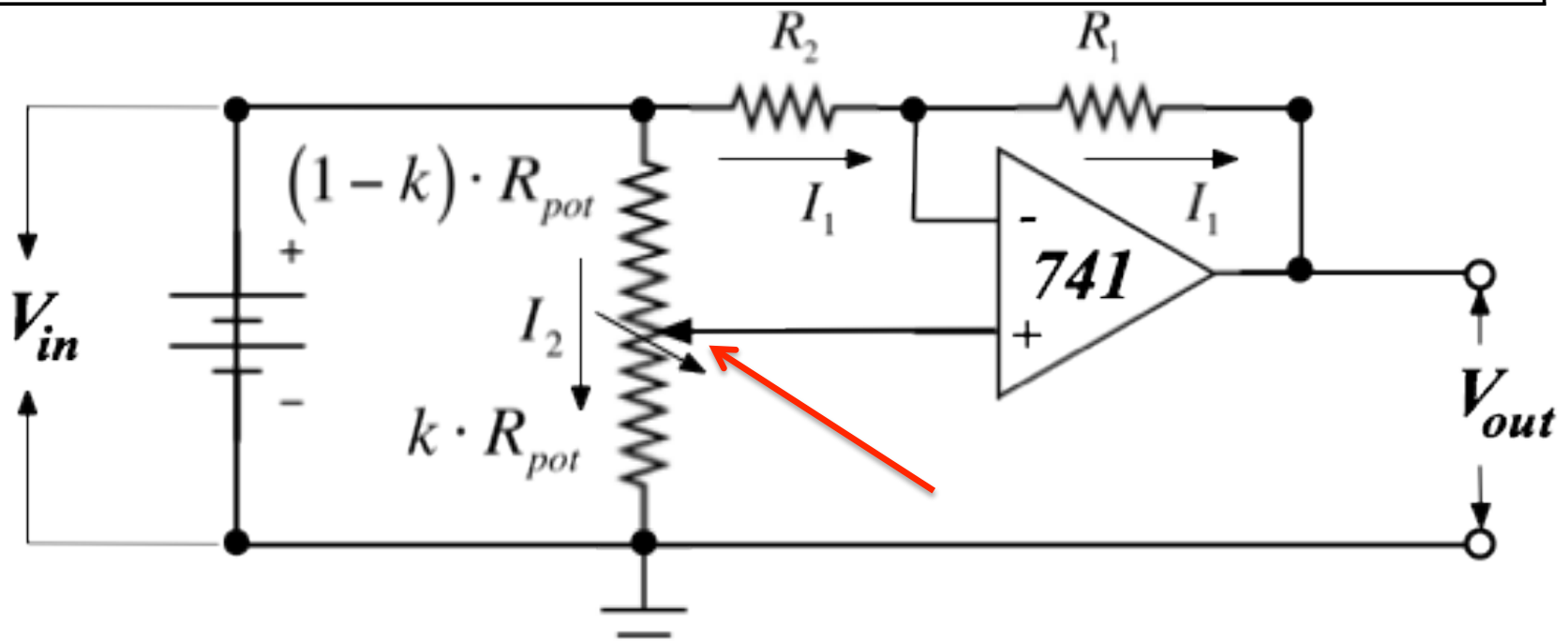
$$V_{in} = (1 - k) \cdot R_{pot} \cdot I_1 + k \cdot R_{pot} \cdot I_2 = R_{pot} \cdot I_2 \rightarrow I_2 = \frac{V_{in}}{R_{pot}}$$




Circuit Analysis (4)

$$\text{Substitute : } V_{in} = \underline{R_{pot} \cdot I_2} \rightarrow V_{out} + I_1 \cdot R_1 = V_{in} - (1 - k) \cdot \underline{R_{pot} \cdot I_2}$$

$$V_{out} + I_1 \cdot R_1 = V_{in} - (1 - k) \cdot V_{in}$$

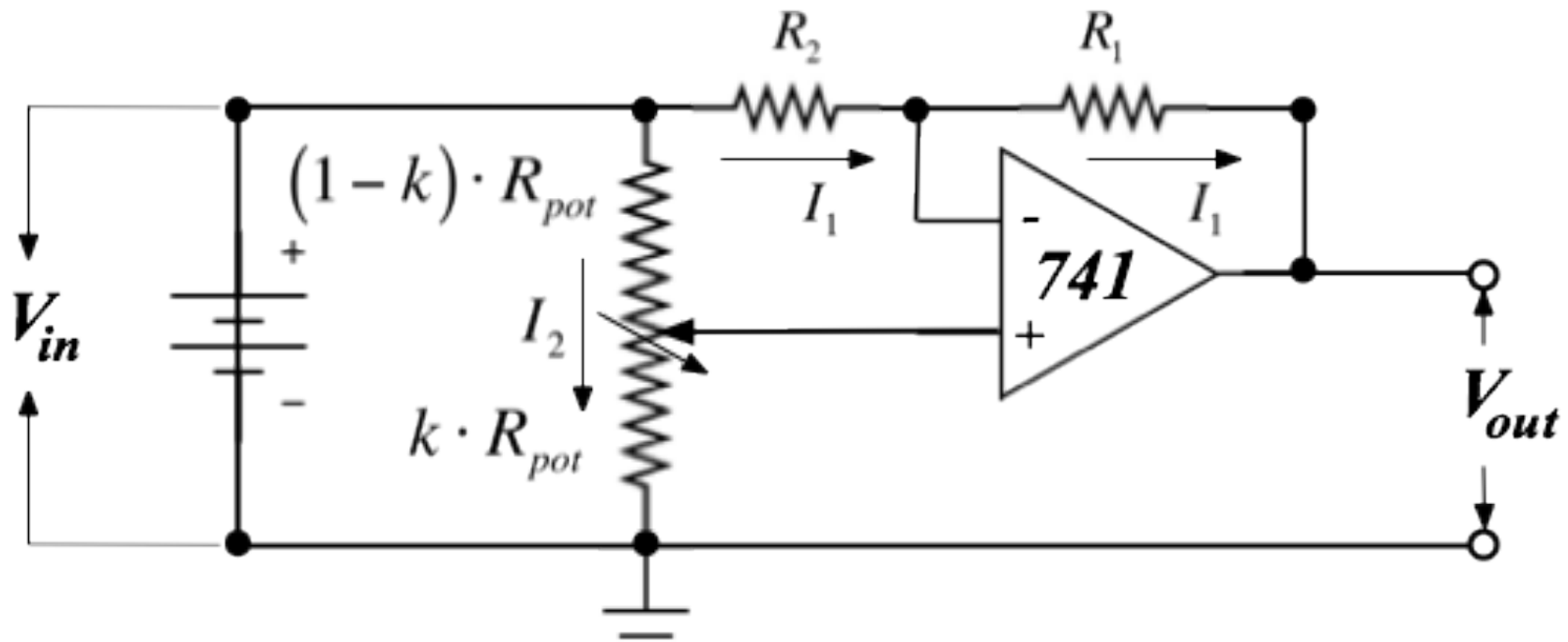
$$V_{out} = k \cdot V_{in} - I_1 \cdot R_1$$



Circuit Analysis (5)

From Input to Output Across Top Loop :
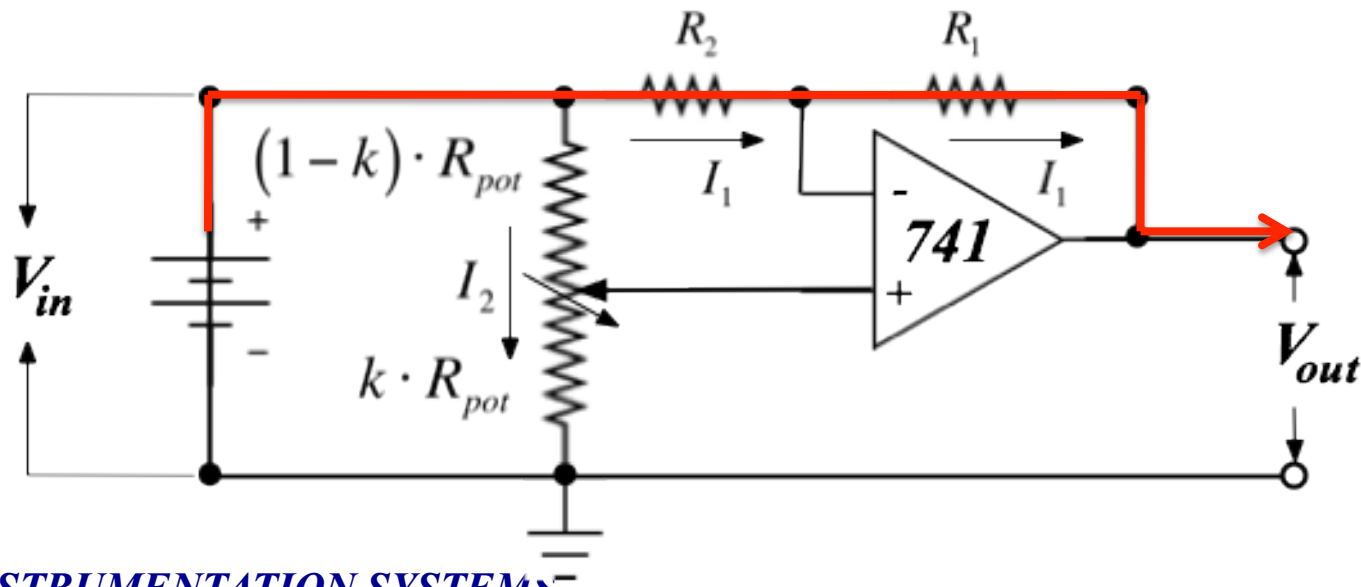
$$\boxed{V_{in} - V_{out} = (R_2 + R_1) \cdot I_1} \rightarrow I_1 = \frac{V_{in} - V_{out}}{(R_2 + R_1)}$$



Circuit Analysis (6)

Collected Equations :

$$\begin{aligned} V_{out} &= V_{in} - (R_2 + R_1) \cdot I_1 \\ V_{out} &= k \cdot V_{in} - R_1 \cdot I_1 \end{aligned} \rightarrow \frac{V_{out} - V_{in}}{(R_2 + R_1)} = I_1$$

Eliminate I_1

$$\begin{aligned} (R_2 + R_1) \cdot V_{out} &= (R_2 + R_1) \cdot k \cdot V_{in} - R_1 \cdot (R_2 + R_1) I_1 \\ - R_1 \cdot V_{out} &= - R_1 \cdot V_{in} + R_1 \cdot (R_1 + R_2) \cdot I_1 \end{aligned}$$


$$R_2 \cdot V_{out} = [(R_1 + R_2) \cdot k - R_1] \cdot V_{in}$$

Circuit Analysis (7)

→ Simplify

→
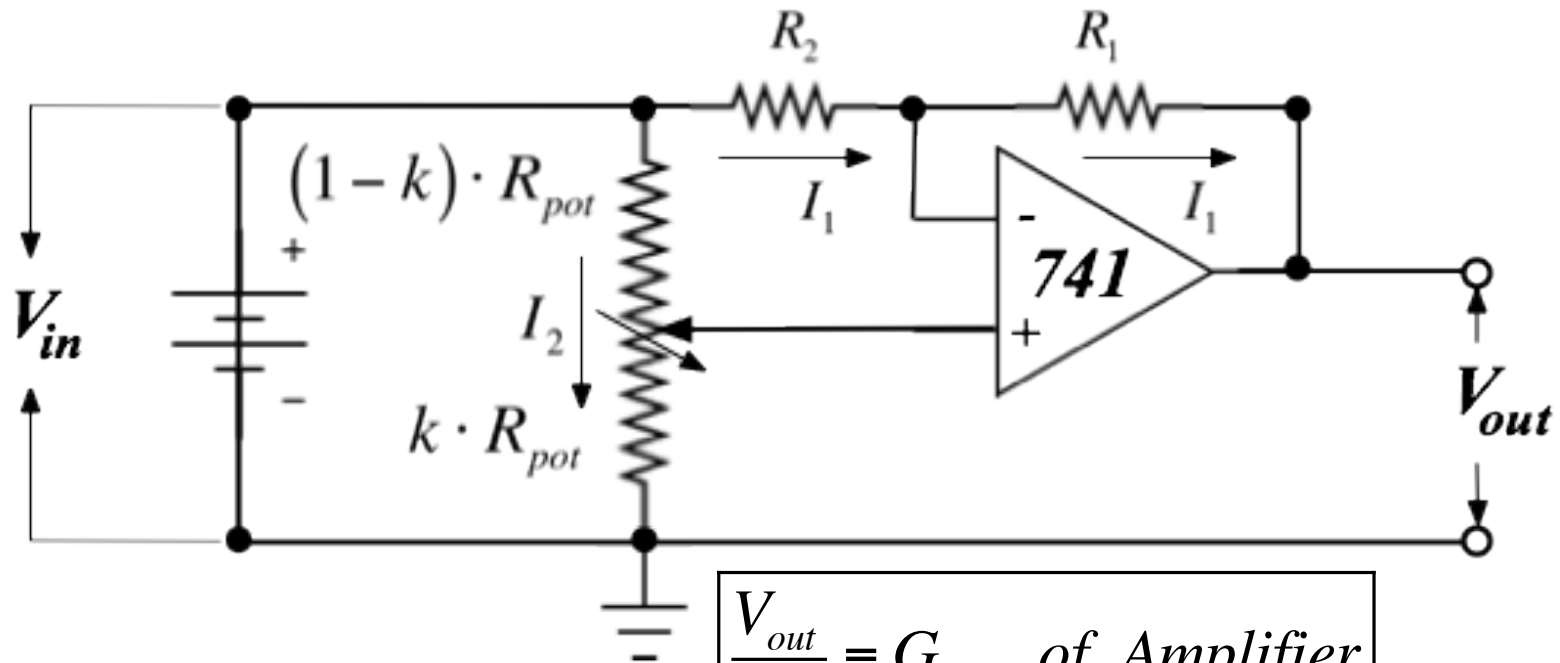
$$V_{out} = \left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} \right] \cdot V_{in}$$




$$\frac{V_{out}}{V_{in}} \equiv G_{ain} \dots \text{of Amplifier}$$

Circuit Power Dissipation (1)

Potentiometer:
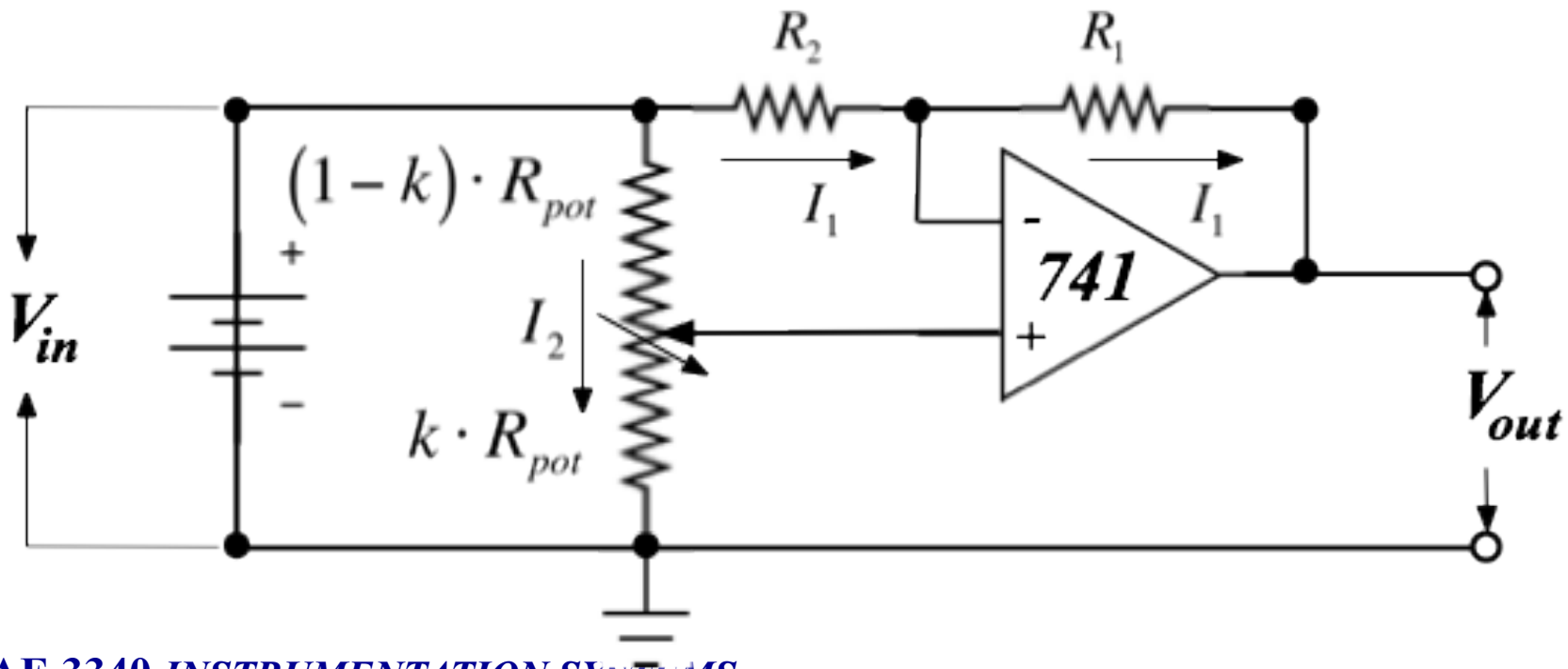
$$I_2 = \frac{V_{in}}{R_{pot}} \rightarrow \boxed{P_{R_{pot}} = I_2 \cdot V_{in} = \frac{V_{in}^2}{R_{pot}}} \dots (\text{Slide 7})$$



Circuit Power Dissipation (2)

*Current
Through R_1 , R_2 :*

$$\begin{aligned} \text{from Slide 9} \rightarrow I_1 &= \frac{V_{out} - V_{in}}{(R_2 + R_1)} = \frac{\left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} \right] V_{in} - V_{in}}{(R_2 + R_1)} = \\ &= \frac{\left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} - 1 \right] \cdot V_{in}}{(R_2 + R_1)} = \frac{\left[(k - 1) \cdot \frac{(R_2 + R_1)}{R_2} \right] \cdot V_{in}}{(R_2 + R_1)} = \frac{(k - 1)}{R_2} V_{in} \end{aligned}$$

Circuit Power Dissipation (3)

*Power
Dissipated by
 R_1, R_2 :*

$$P_{R_2} = I_1^2 \cdot R_2 = \left(\frac{(k-1)}{R_2} V_{in} \right)^2 \cdot R_2 = \frac{[(k-1)V_{in}]^2}{R_2}$$

$$P_{R_1} = I_1^2 \cdot R_1 = \left(\frac{(k-1)}{R_2} V_{in} \right)^2 \cdot R_1 = \left(\frac{R_1}{R_2} \right) \cdot \frac{[(k-1)V_{in}]^2}{R_2}$$

R_1 is the critical resistor we have to watch for power dissipation

Circuit Properties (1)

Let $\rightarrow k = 0$


across OpAmp Terminals $\rightarrow V^+ = V^-$

$\rightarrow \boxed{V^- = 0 = V^+} \rightarrow \text{"virtual ground"}$

$$V_{in} = R_2 \cdot I_1 \rightarrow V_{out} = -R_1 \cdot I_1$$

$$\boxed{V_{out} = -\frac{R_1}{R_2} \cdot V_{in}}$$

• Original Circuit

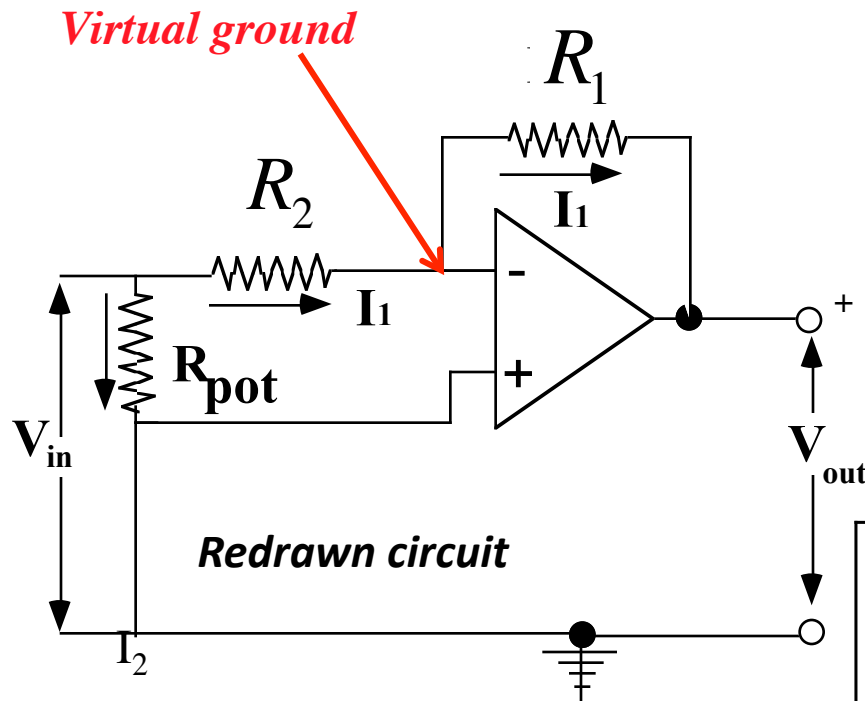


$$\boxed{V_{out} = \left[\left(1 + \frac{R_1}{R_2} \right) \cdot 0 - \frac{R_1}{R_2} \right] V_{in} = -\frac{R_1}{R_2} \cdot V_{in}}$$

Check! • Voltage Polarity Inverter!

Circuit Properties (2)

Let $\rightarrow k = 1$

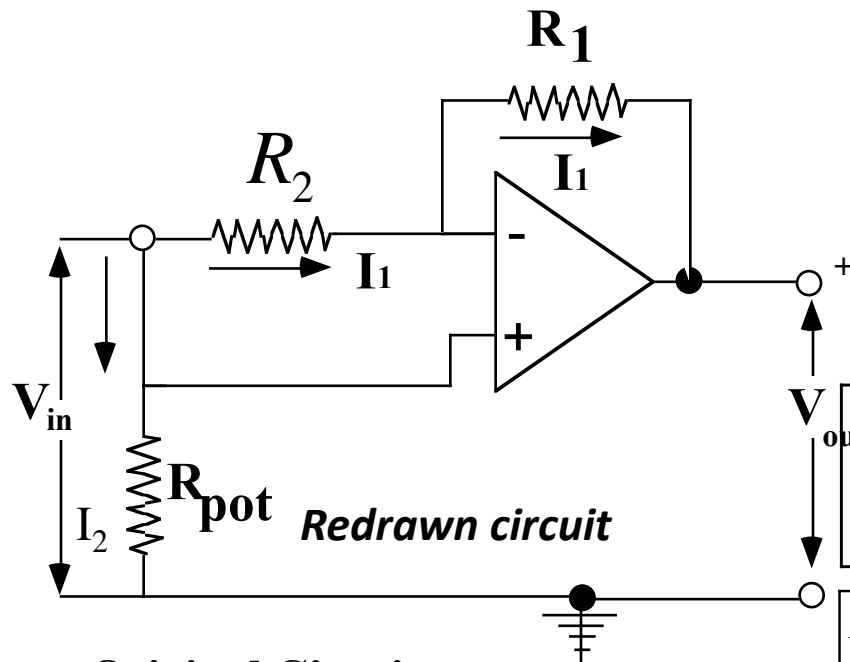

• Original Circuit

$$V_{out} = \left[\left(1 + \frac{R_1}{R_2} \right) \cdot 1 - \frac{R_1}{R_2} \right] V_{in} = V_{in}$$

• Voltage Follower!

Check 2!

• Check ... let $k=1$

across OpAmp Terminals :

$$V_{in} = V^+ \rightarrow V^- = V_{out} + R_1 \cdot I_1$$

$$V^+ = V \rightarrow V_{in} = V_{out} + R_1 \cdot I_1$$

across Top Loop from Input to Output :

$$V_{in} = V_{out} + (R_1 + R_2) \cdot I_1$$

Eliminate I_1 :


$$(R_1 + R_2) \cdot V_{in} = (R_1 + R_2) \cdot V_{out} + (R_1 + R_2) \cdot R_1 \cdot I_1$$

$$- R_1 \cdot V_{in} = - R_1 \cdot V_{out} - R_1 \cdot (R_1 + R_2) \cdot I_1$$


$$R_2 \cdot V_{in} = R_2 \cdot V_{out}$$

$$\rightarrow V_{in} = V_{out}$$


Circuit Properties (3)

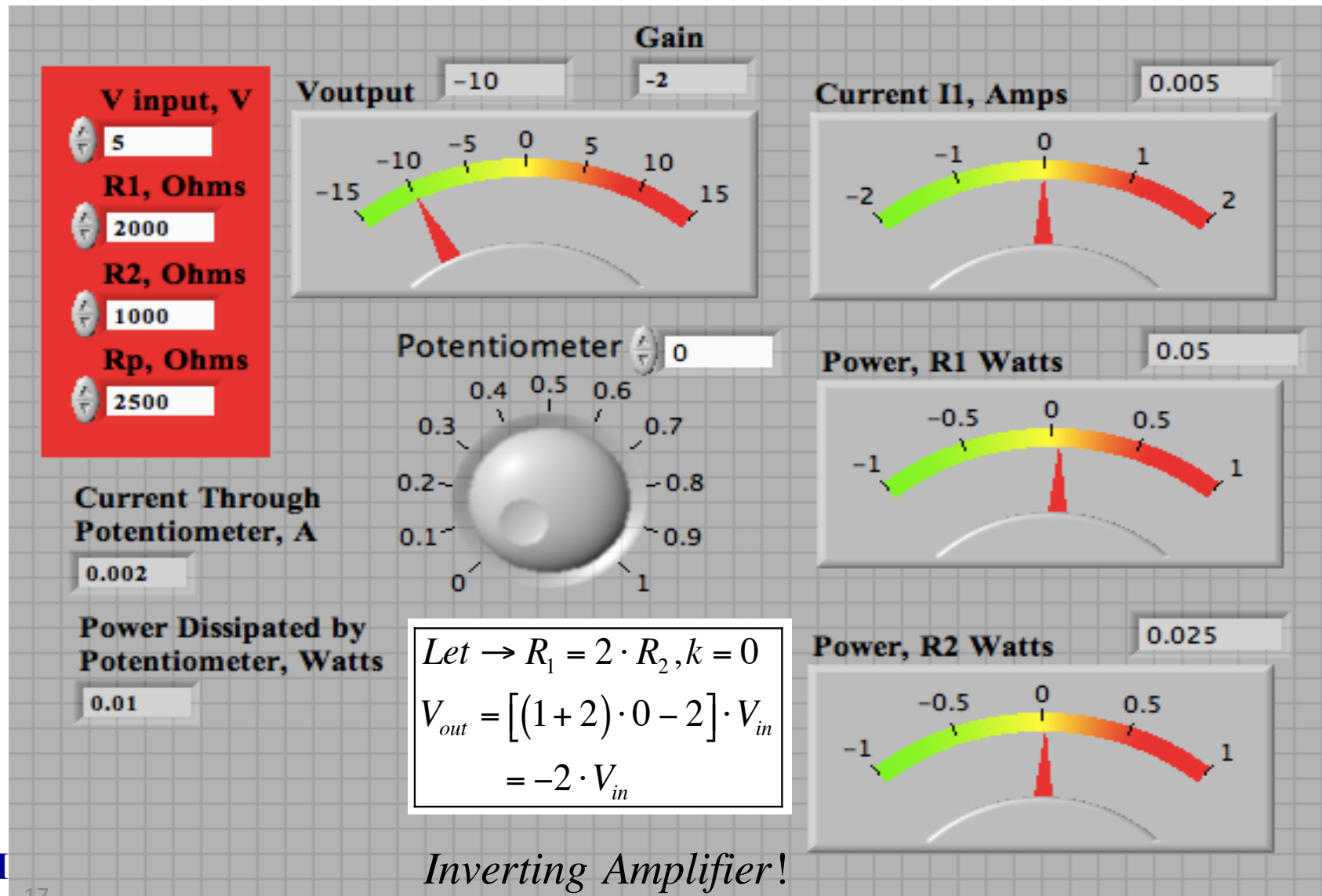

Circuit Properties (4)

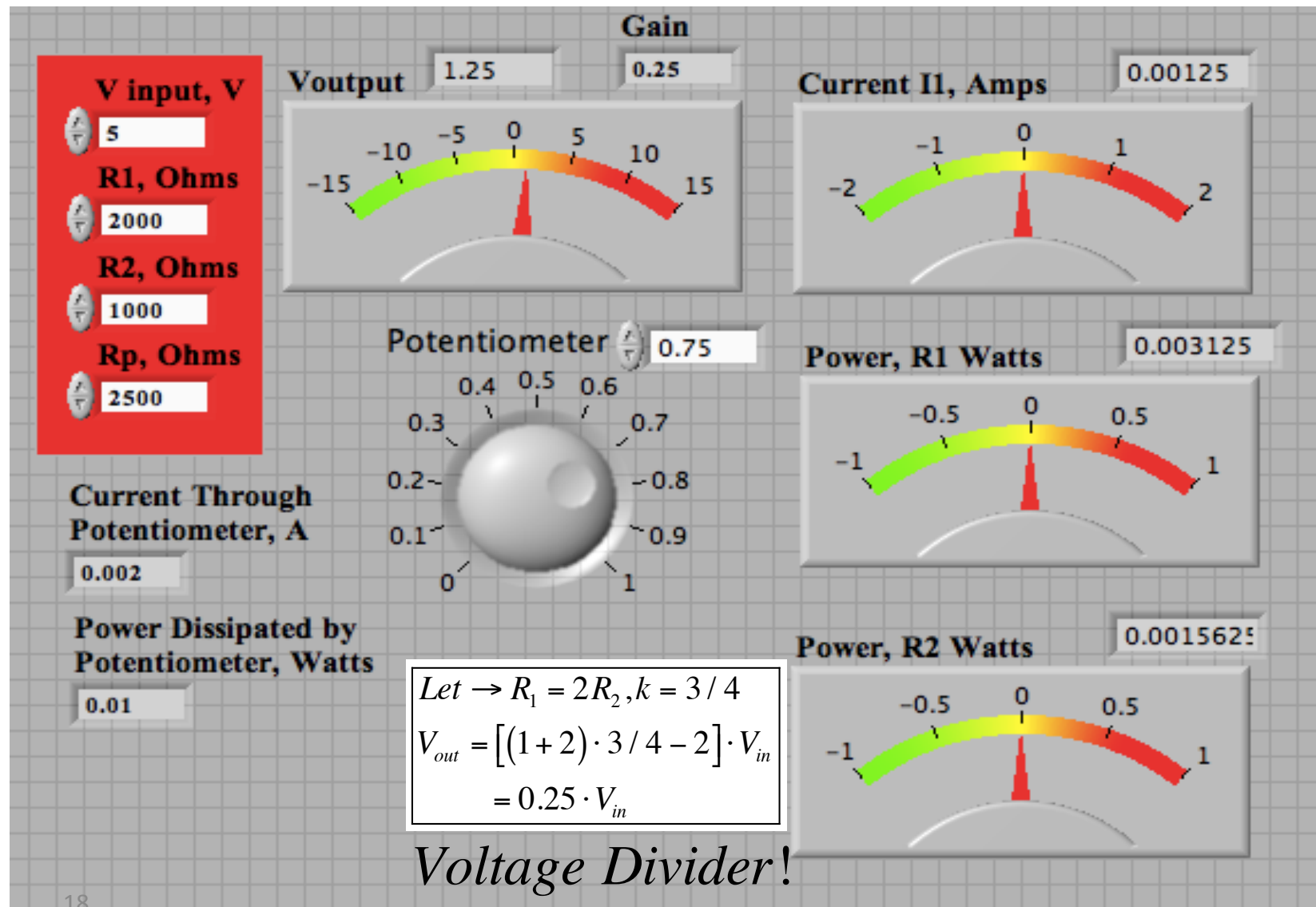


Circuit Properties ⁽⁵⁾

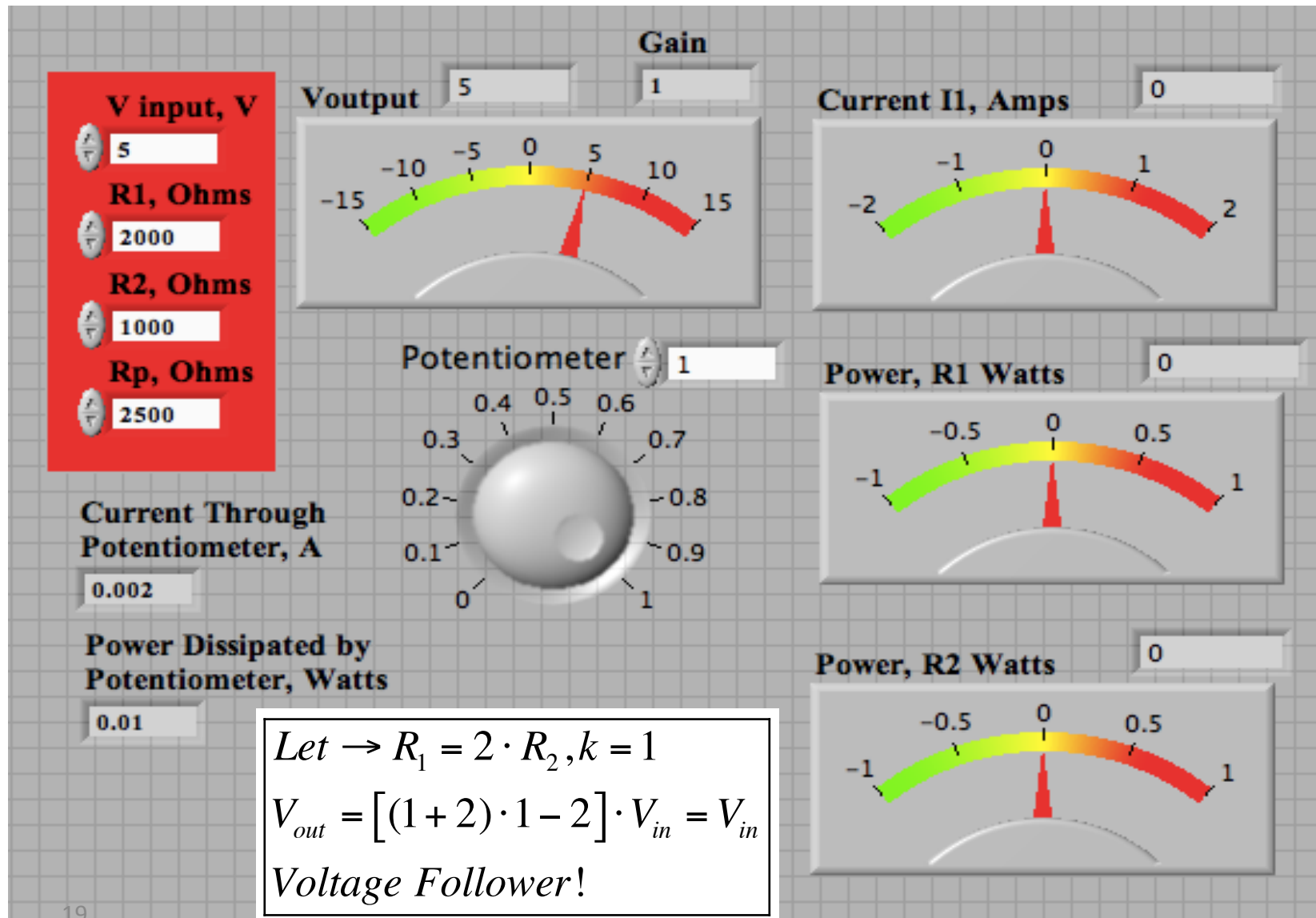

Lab Equipment

1. My DAQ Chassis and USB Cable
2. MyDAQ Red and Black Voltage Probes
3. MyDAQ BreadBoard
4. Honeywell 2.5 k Ω , 2 Watt Potentiometer
5. Breadboard Jumper Wires
6. 10 Assorted Resistors from *1000 Ω to 5000 k Ω*
7. *NS-742 OpAmp*

Hardware Configuration

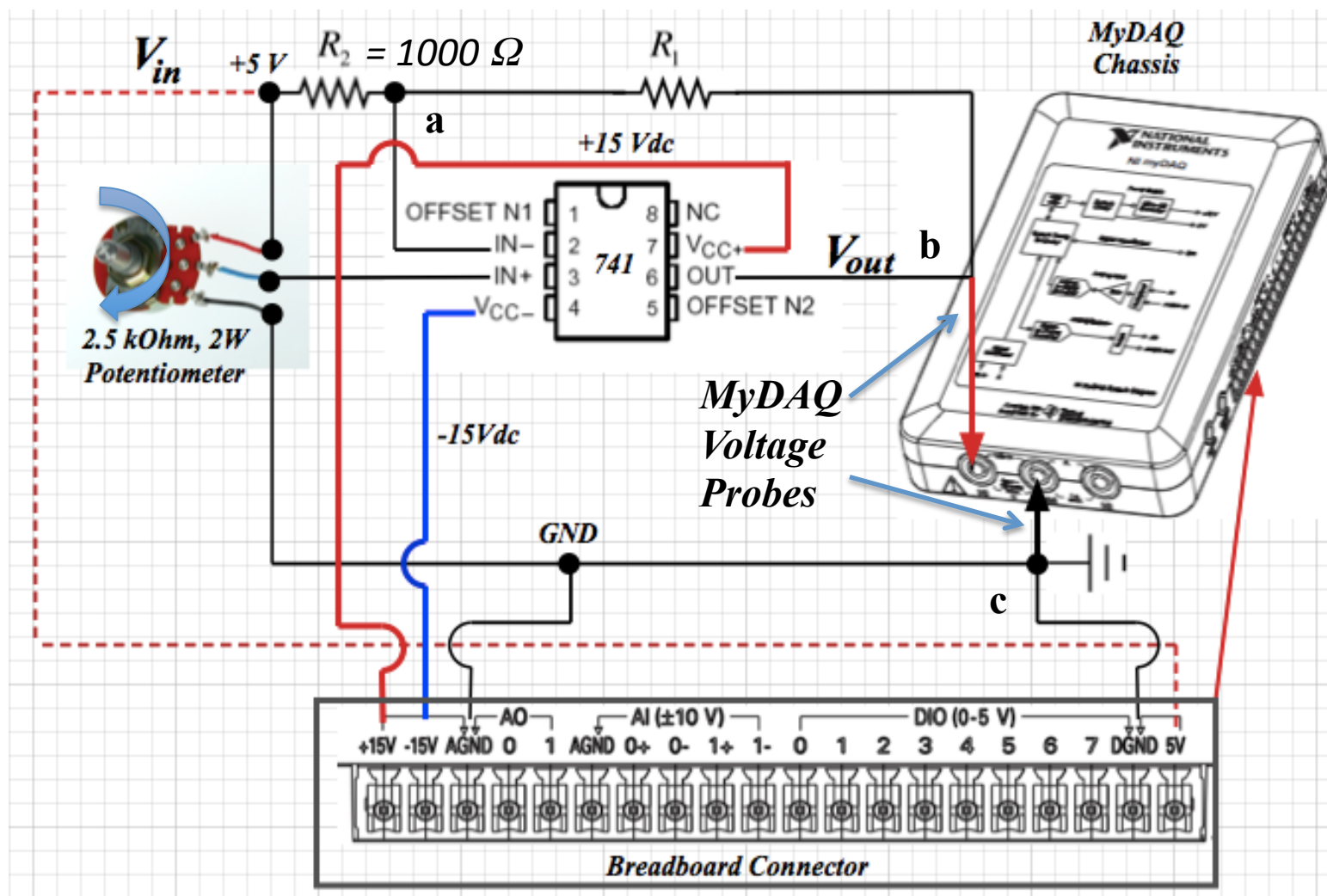

Potentiometer Spec Sheet ⁽¹⁾

Potentiometer Type	Industrial
Element Type	Conductive Plastic
Terminal	Solder lug
Power Rating	2 W
Resistance Value	2.5 kOhm
Resistance Tolerance	$\pm 10 \%$
Linearity	$\pm 5 \%$
Bushing Thread	9,53 mm [0.375 in] x 32 NEF-2A
Bushing Length	9,53 mm [0.375 in]
Bushing Type	Standard
Shaft Diameter	6,35 mm [0.25 in]
Shaft Length	50,80 mm [2.0 in]

Honeywell



Potentiometer Spec Sheet ⁽²⁾


Shaft Ending	Plain round
Body	27.8 mm [1.094 in] diameter max.
Electrical Taper	Linear
Operating Temperature	-55 °C to 120 °C [-67 °F to 248 °F]
Working Voltage (Max.)	500 V
Rotational Life	25000 cycles
Mechanical Rotation	312°
Availability	Global
Series Name	53
UNSPSC Code	4111363300
UNSPSC Commodity	4111363300 Potentiometers

Honeywell




Potentiometer Spec Sheet ⁽³⁾

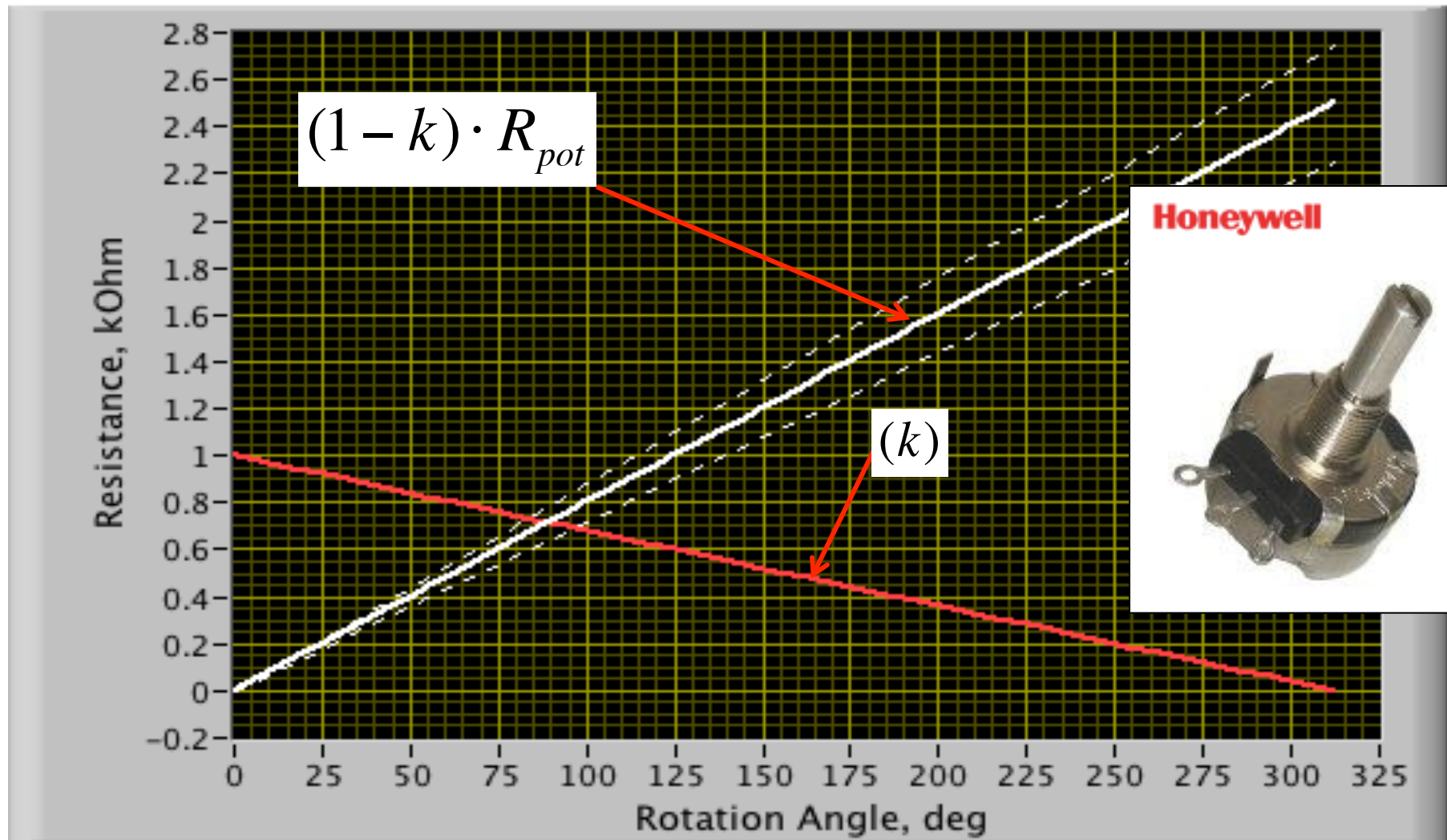Potentiometer Resistance, $(1-k) \cdot R_{max}$
Rotation Angle, deg.



Potentiometer Spec Sheet ⁽³⁾

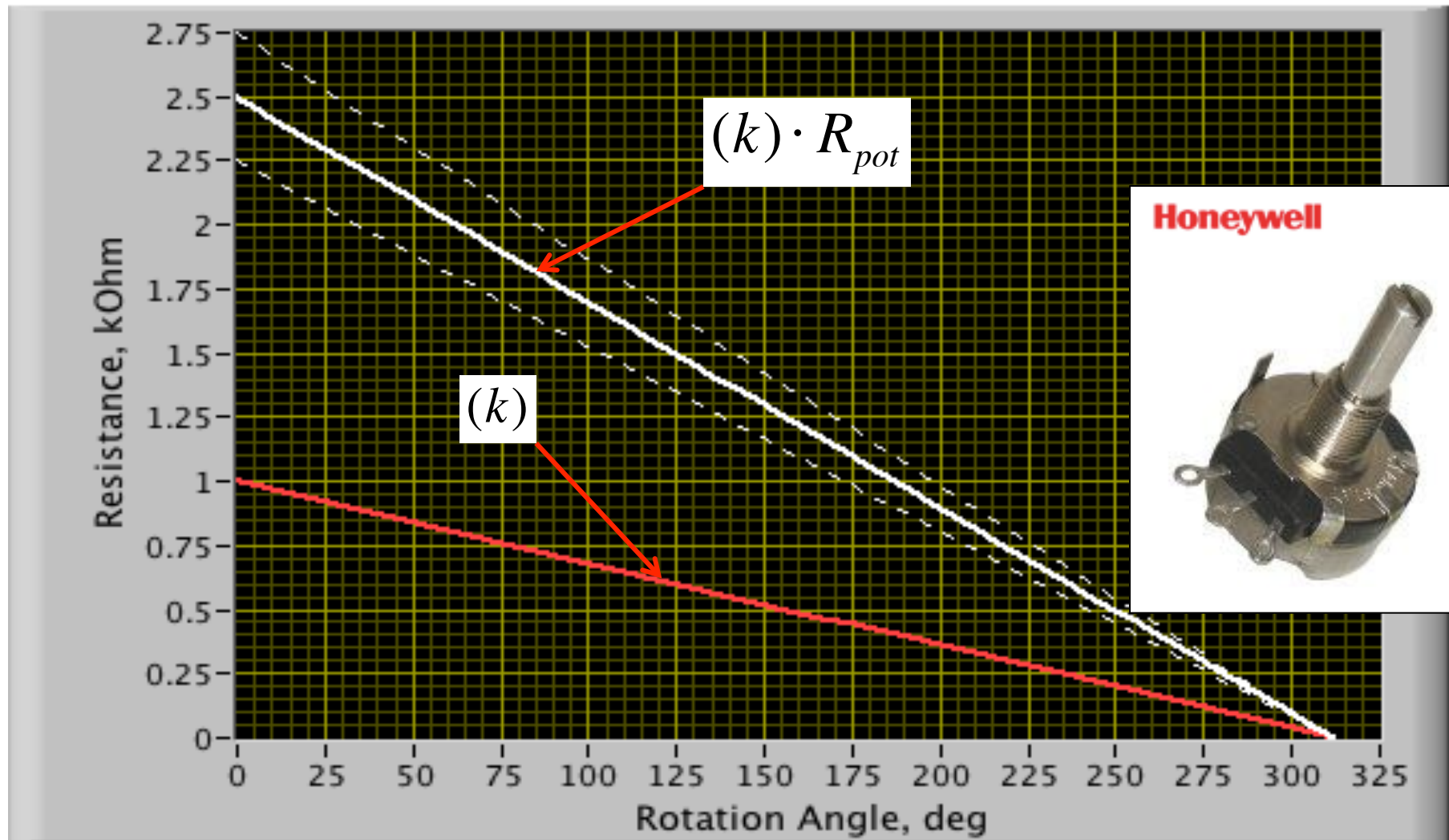Potentiometer Resistance, $(k) \cdot R_{max}$
Rotation Angle, deg.



PreLab Calculations/Measurements

- Verify that All Resistances lie Between $1\text{ k}\Omega$ and $5\text{ k}\Omega$
- Ensure that Two Resistors $\sim 1000\ \Omega$
- Power Dissipated by Potentiometer @ $5\text{Vdc } V_{in}$: _____
- Maximum Power Dissipated in $R_1 R_2$ @ $5\text{Vdc } V_{in}$: _____
- Expected Range of Output Voltages: _____

Based on Resistor Range from $1\text{ K}\Omega$ to $2\text{ K}\Omega$

- Actual Potentiometer Resistance ($k=1$): _____ %Deviation _____
- Actual Potentiometer Resistance ($k=0$): _____ %Deviation _____
- Find Rotation Point on Potentiometer where $k=0.5$, Mark with “Sharpie” Felt Tip Pen

-- Perform Calculation to Ensure that $\frac{1}{4}$ Watt Limit is not Exceeded for any Resistor with Any Potentiometer Setting at $5\text{Vdc } V_{in}$

PreLab Uncertainty Analysis

- Calculate the Expected Uncertainty in the Amplifier Gain

$$\text{Gain} = V_{out}/V_{in}$$

- Based on the Manufacturer's Specs for R_{pot} , R_1 , and R_2
For $k = \{0, 1/2, 1\}$ Potentiometer Settings
- Use Chain Rule for Error Propagation
- Assume $\sigma_k/k \sim$ linearity tolerance (See Slide 18)
- Plot Expected Gain Error as a function of R_1/R_2
- Assume V_{in} V_{out} measurements are exact

PreLab Uncertainty Analysis ⁽²⁾

$$\frac{V_{out}}{V_{in}} \equiv G_{ain} \dots U^2_{Gain} = \left(\frac{\partial G_{ain}}{\partial R_1} \right)^2 \cdot U^2_{R_1} + \left(\frac{\partial G_{ain}}{\partial R_2} \right)^2 \cdot U^2_{R_2} + \left(\frac{\partial G_{ain}}{\partial k} \right)^2 \cdot U^2_k$$

• Calculate Partial Derivatives

$$\frac{\partial G_{ain}}{\partial R_1} = \frac{\partial}{\partial R_1} \left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} \right] = \frac{1}{R_2} \cdot k - \frac{1}{R_2} = \frac{1}{R_2} \cdot (k - 1)$$

$$\frac{\partial G_{ain}}{\partial R_2} = \frac{\partial}{\partial R_2} \left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} \right] = \frac{\partial}{\partial R_2} \left[\frac{R_1}{R_2} \cdot (k - 1) + k \right] = -\frac{R_1}{R_2^2} \cdot (k - 1)$$

$$\frac{\partial G_{ain}}{\partial k} = \frac{\partial}{\partial k} \left[\left(1 + \frac{R_1}{R_2} \right) \cdot k - \frac{R_1}{R_2} \right] = \left(1 + \frac{R_1}{R_2} \right)$$

PreLab Uncertainty Analysis ⁽³⁾

Substitute Partial Derivatives

$$U^2_{Gain} = \left[\frac{1}{R_2} \cdot (k - 1) \right]^2 U^2_{R_1} + \left[\frac{R_1}{R_2^2} \cdot (k - 1) \right]^2 U^2_{R_2} + \left(1 + \frac{R_1}{R_2} \right)^2 \cdot U^2_k$$

Normalize Independent Errors ...

$$U^2_{Gain} = \left[\frac{R_1}{R_2} \cdot (k - 1) \right]^2 \left(\frac{U_{R_1}}{R_1} \right)^2 + \left[\frac{R_1}{R_2} \cdot (k - 1) \right]^2 \left(\frac{U_{R_2}}{R_2} \right)^2 + \left[k \left(1 + \frac{R_1}{R_2} \right) \right]^2 \cdot \left(\frac{U_k}{k} \right)^2$$

$$\left\{ \frac{U_{R_1}}{R_1}, \frac{U_{R_2}}{R_2} \right\} \approx 5\% \text{ tolerance}$$

$$\left(\frac{U_k}{k} \right) \approx 5\% \text{ linearity}$$

PreLab Uncertainty Analysis (4)

Resistance
Tolerance, %

5

R1/R2

1

2

3

4

5

0

Pot Linearity, %

5

k


1

0.5

0

0

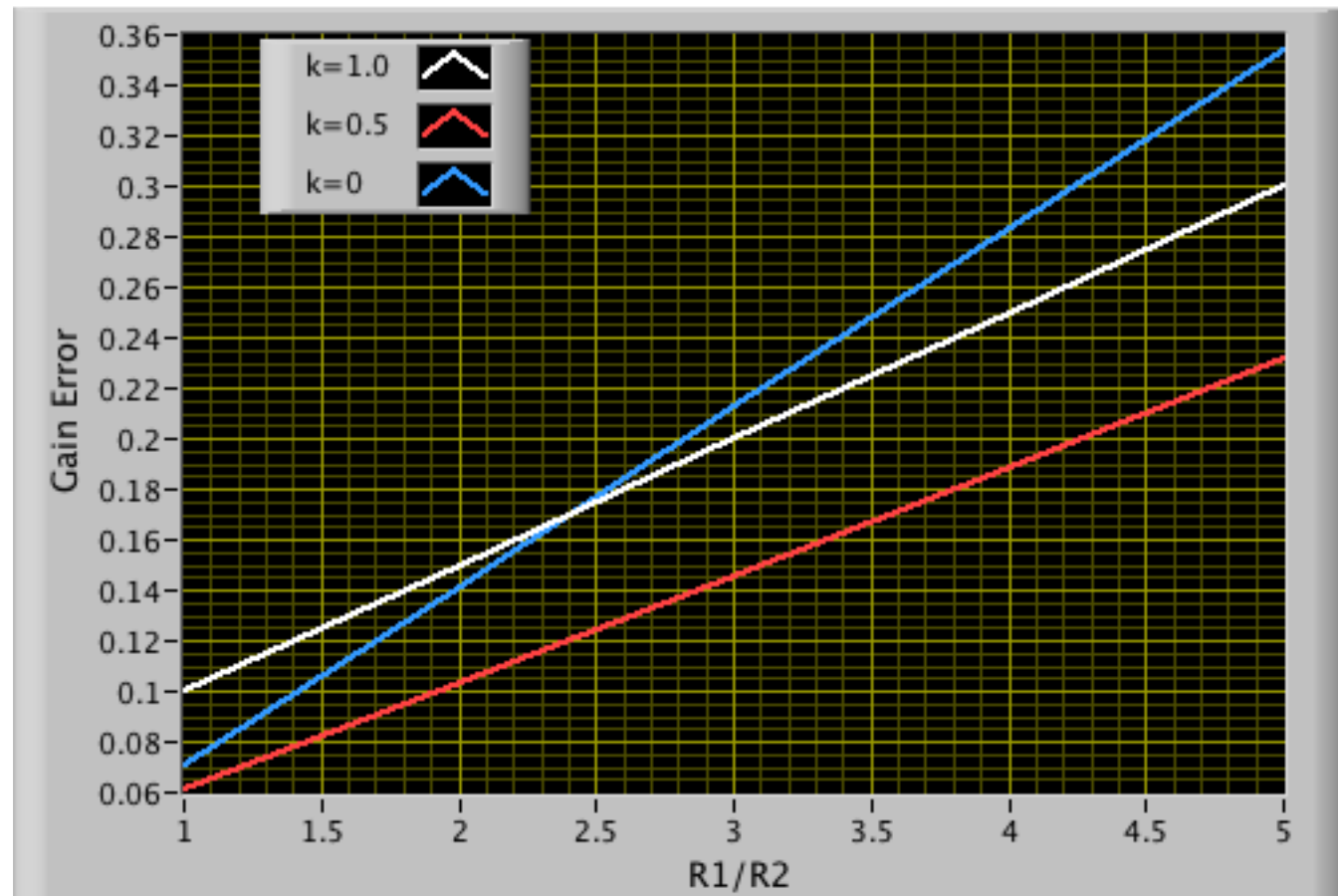Amplifier Gain Error with Potentiometer k as Function of as R1/R2



MENTATION SYSTEMS

Resistor Table

Resistor No.	Nom. Value k Ω	Tolerance, %	Measured Value, k Ω	% Deviation
1	1000 k Ω			
2	1000 k Ω			
3				
4				
5				
6				
7				
8				
9				
10				

Lab Procedure

- 1 Measure Resistance of Potentiometer *with $\{k=1, k=0\}$.*
 - a. Log Data.
- 2 Read Nominal Values/Tolerances for Test Resistors.
 - b) Log Data in Resistor Table.
- 3 Build and Test Circuit
 - c) Start with $R_1 = R_2 \sim 1000 \Omega$.
 - d) Power Up Circuit
 - e) Populate Voltage Tables for all R_i Resistors, Keep $R_2 \sim 1000 \Omega$.
 - f) Measure Voltages across nodes $\{a,c\}$ and $\{b,c\}$ Using MyDAQ Voltage Probes. See Figure on Slide 17.
 - g) Be sure to power down circuit when swapping out R_1
- 4 Repeat Part 3 for Potentiometer $k=\{0, \frac{1}{2}, 1\}$
- 5 Complete Error Analysis

Voltage Table I

R_1	Measured Value, $k\Omega$, R_1	V_{in}	$V_{\{b,c\}}$ “ V_{out} ”	V_{out}/V_{in} , Gain	$V_{\{a,c\}}$	k
1	1000 $k\Omega$					0
2						0
3						0
4						0
5						0
6						0
7						0
8						0
9						0

Voltage Table II


R_1	Measured Value, $k\Omega$, R_1	V_{in}	$V_{\{b,c\}}$ “ V_{out} ”	V_{out}/V_{in} , Gain	$V_{\{a,c\}}$	k
1	1000 $k\Omega$					$1/2$
2						$1/2$
3						$1/2$
4						$1/2$
5						$1/2$
6						$1/2$
7						$1/2$
8						$1/2$
9						$1/2$

Voltage Table III



R_1	Measured Value, $k\Omega$, R_1	V_{in}	$V_{\{b,c\}}$ “ V_{out} ”	V_{out}/V_{in} , Gain	$V_{\{a,c\}}$	k
1	1000 $k\Omega$					1
2						1
3						1
4						1
5						1
6						1
7						1
8						1
9						1

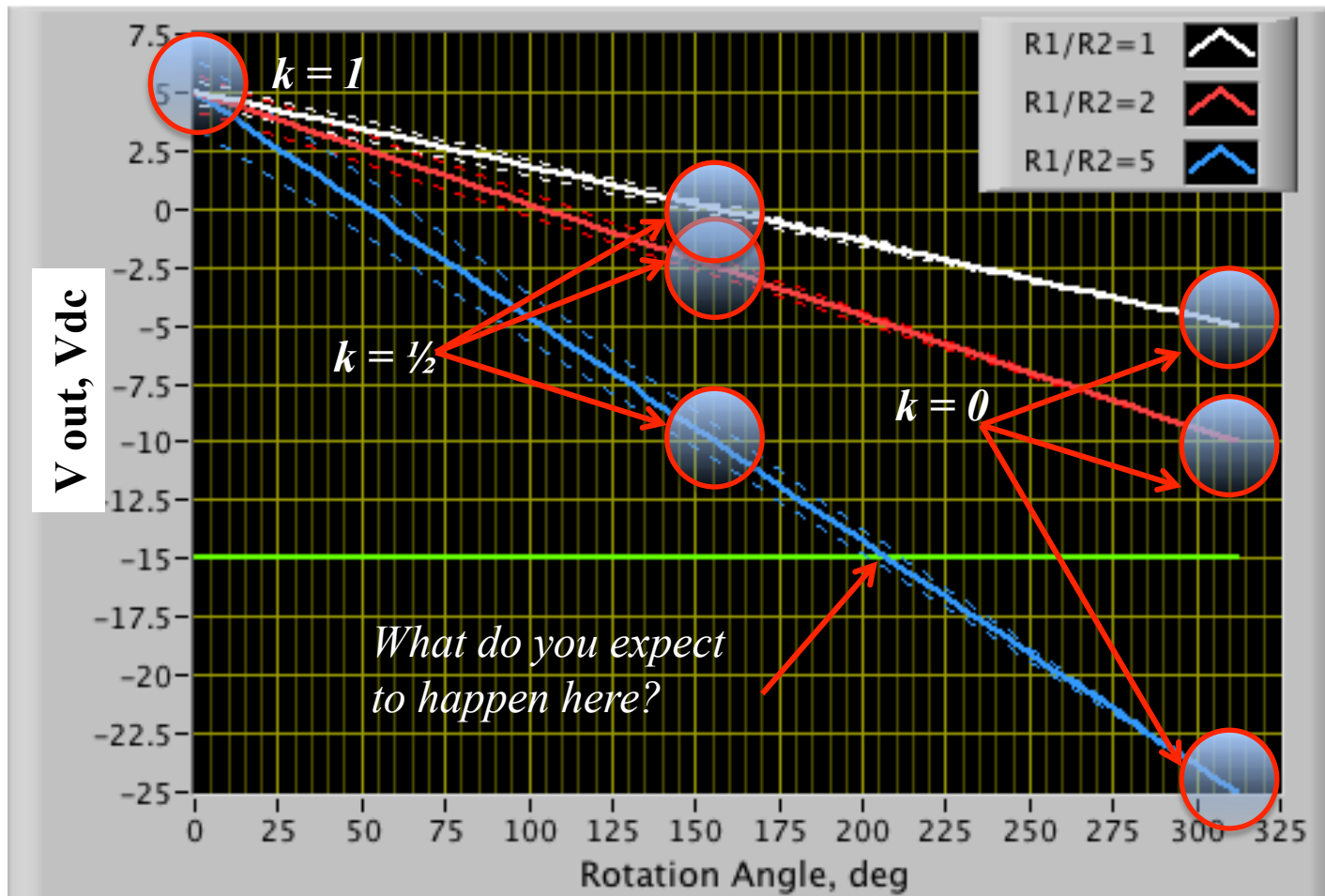Example of Expected Results


Vout For R1/R2 as Function of
Potentiometer Rotation Angle, deg.



OpAmp Saturation Voltage

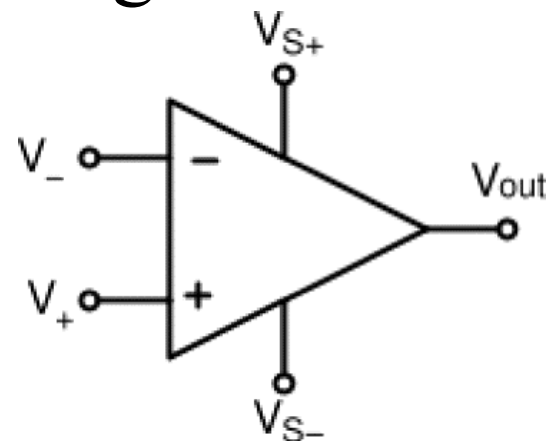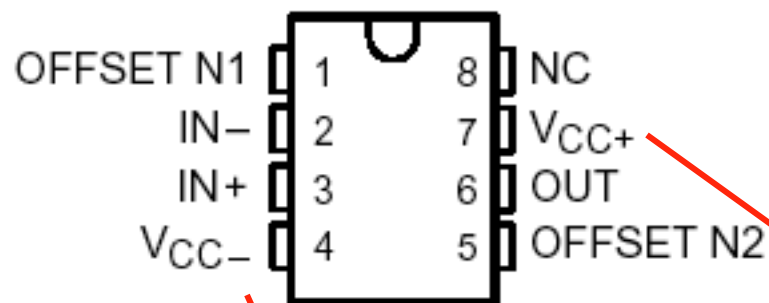


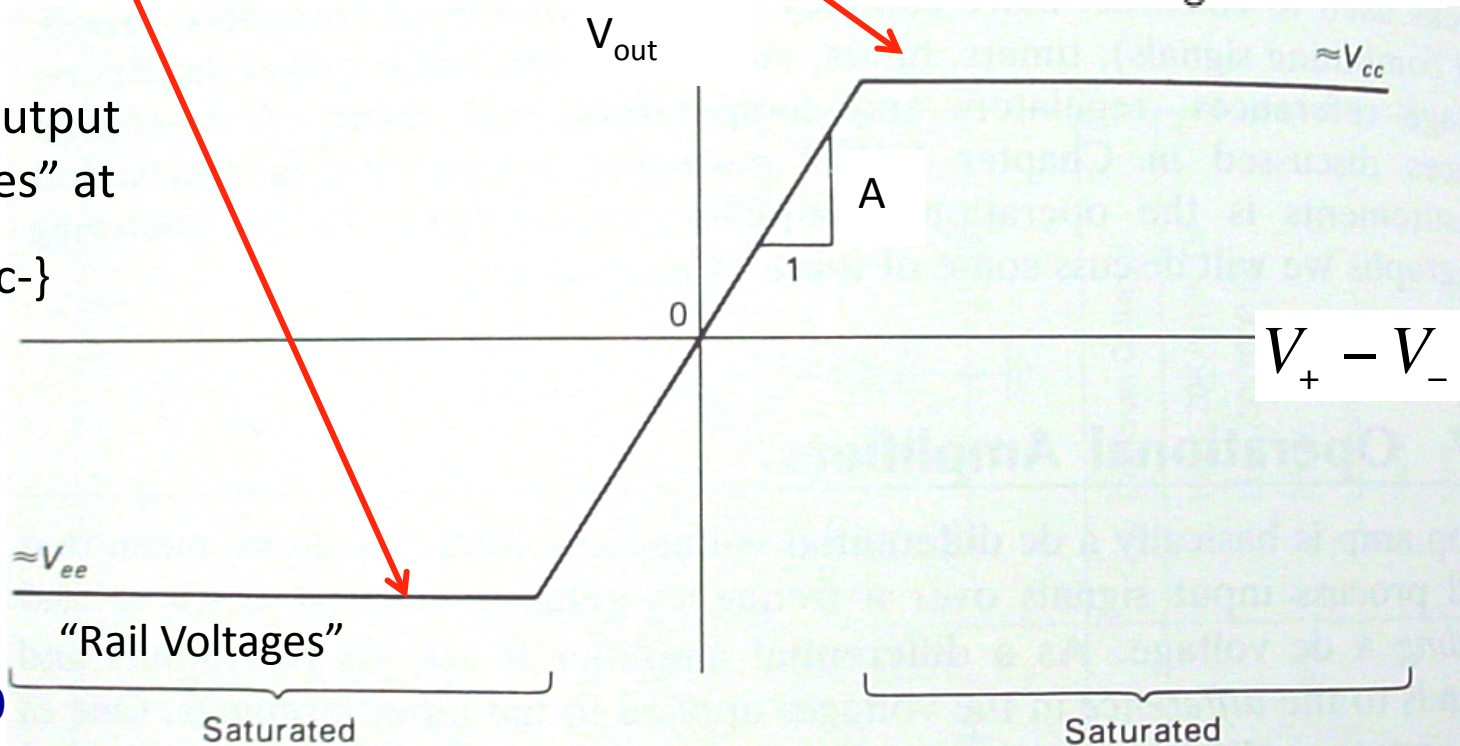- Chip Output “saturates” at $\{V_{cc+}, V_{cc-}\}$



Virtual Ground

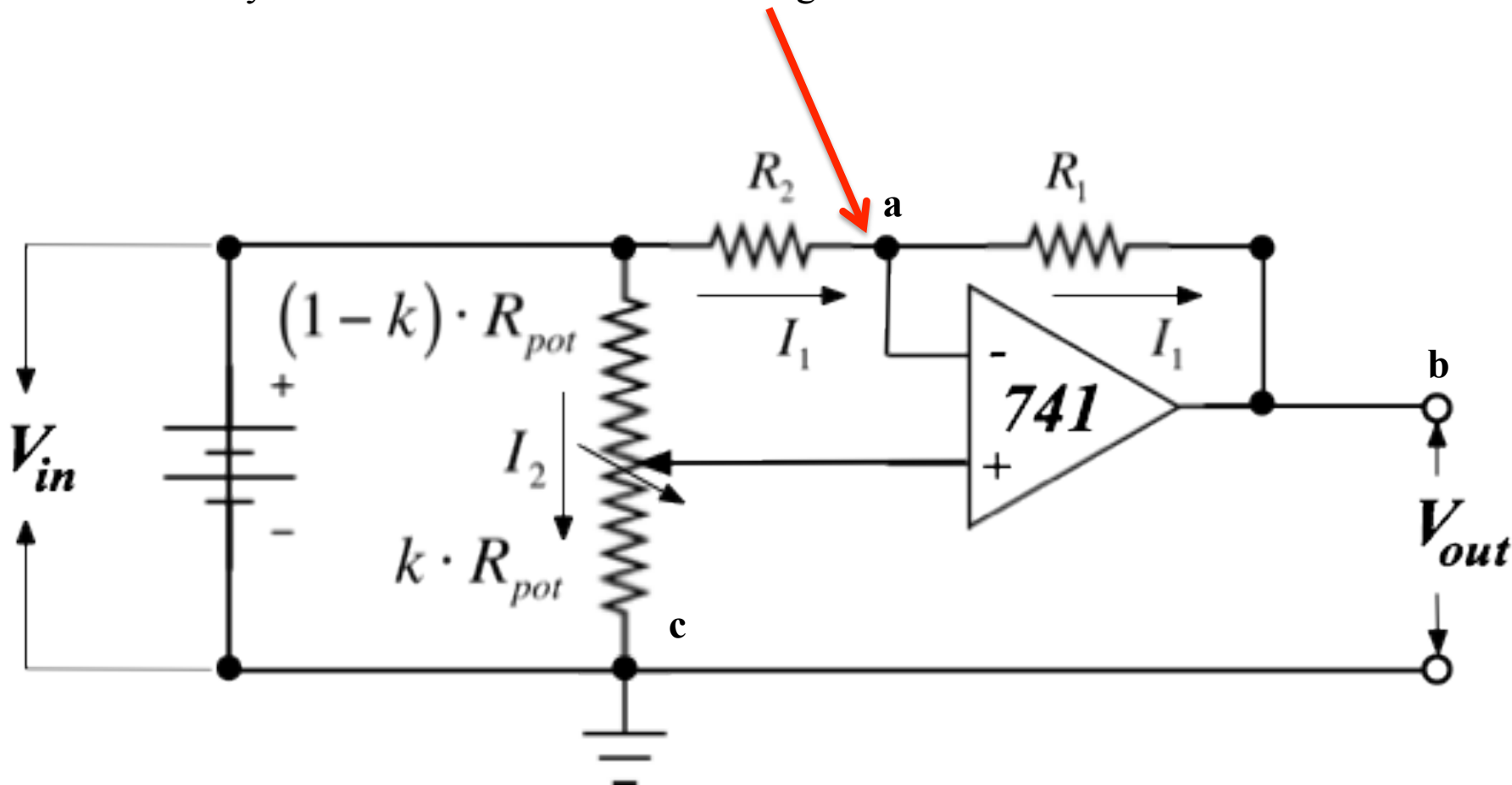Verify that Node “a” becomes Virtual ground as $k \rightarrow 0$



Error Analysis:

- For each Potentiometer setting $\rightarrow k=\{1, \frac{1}{2}, 0\}$ Calculate your mean Gain Value $\{V_{out}/V_{in}\}$ and the Corresponding Standard Deviation
- Assess the 95% confidence interval for this mean value
- Based on the Normal (Gaussian) Distribution
- Based on the Student-T Distribution with the appropriate degrees of freedom