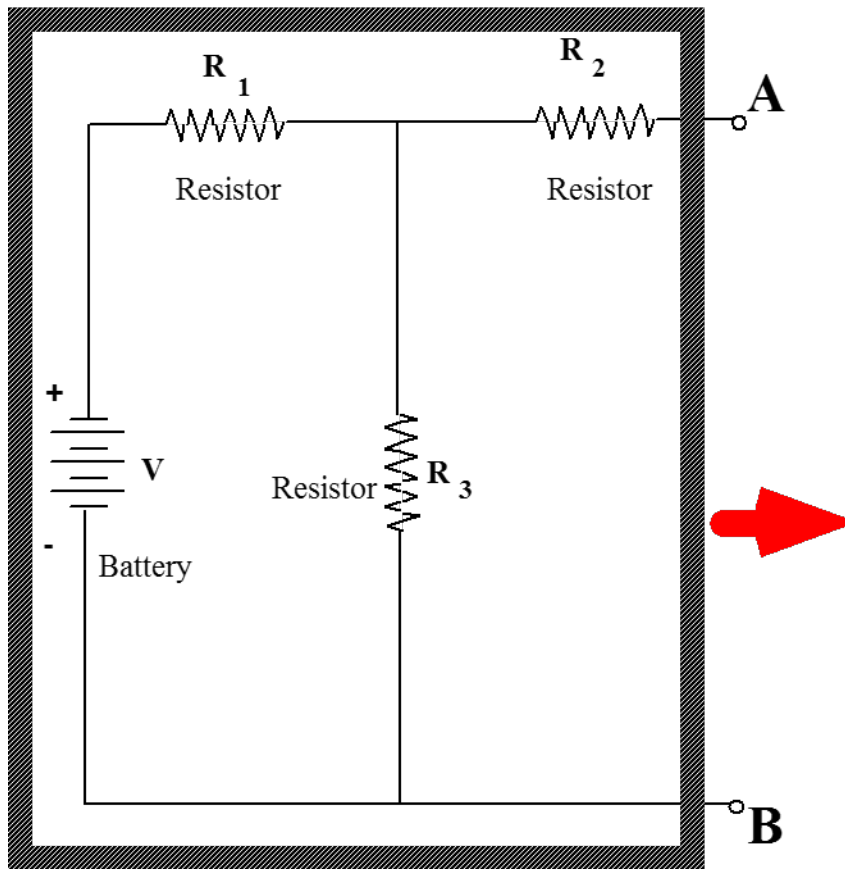


# Homework 2: Due in Lab Week of Jan. 19-22.

*Black Box*



For:

$$V = 12 \text{ Vdc}$$

$$R_1 = 120 \, \Omega$$

$$R_2 = 200 \, \Omega$$


Calculate  $R_3$  so that

$$V_{AB} = 4 \text{ Vdc}$$

How Much Current will be Drawn Through  $AB$  ( $R_2$ ) when circuit is closed across  $AB$  with no load (*Short circuit*)

A More Complex Example

## Thevenin's Equivalent Circuit (2)

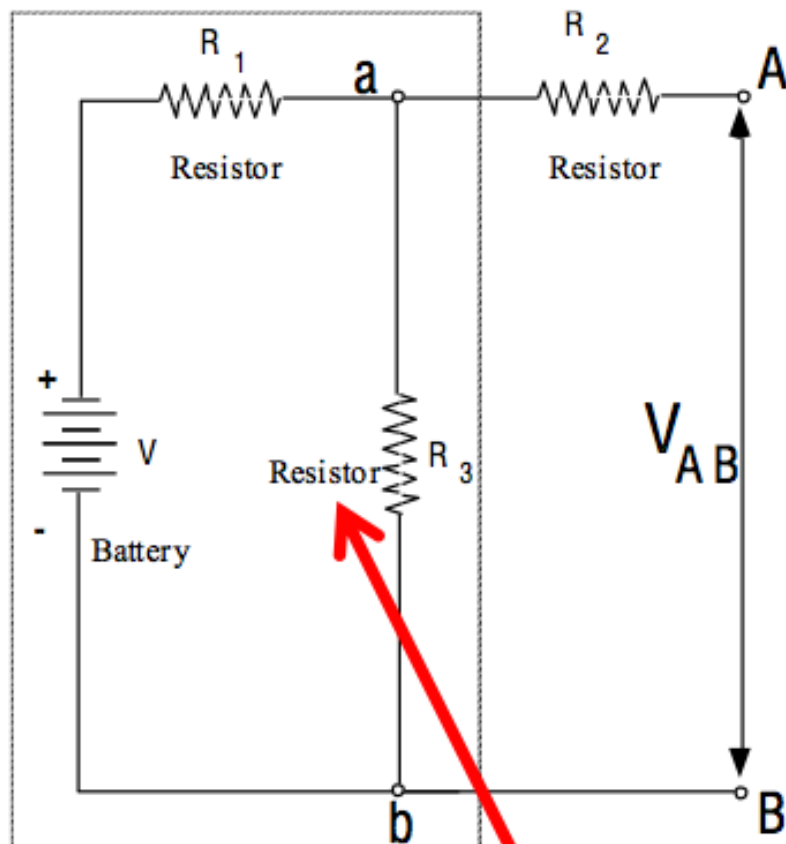

*Parallel resistances*


$$V_{ab} = I \cdot R_3$$

$$I = \frac{V}{(R_1 + R_3)}$$

$$V_{eq} = V_{ab} = V \cdot \frac{R_3}{(R_1 + R_3)}$$

- *Replace with Thevenin Equivalent Circuit*

## Thevenin's Equivalent Circuit (3)

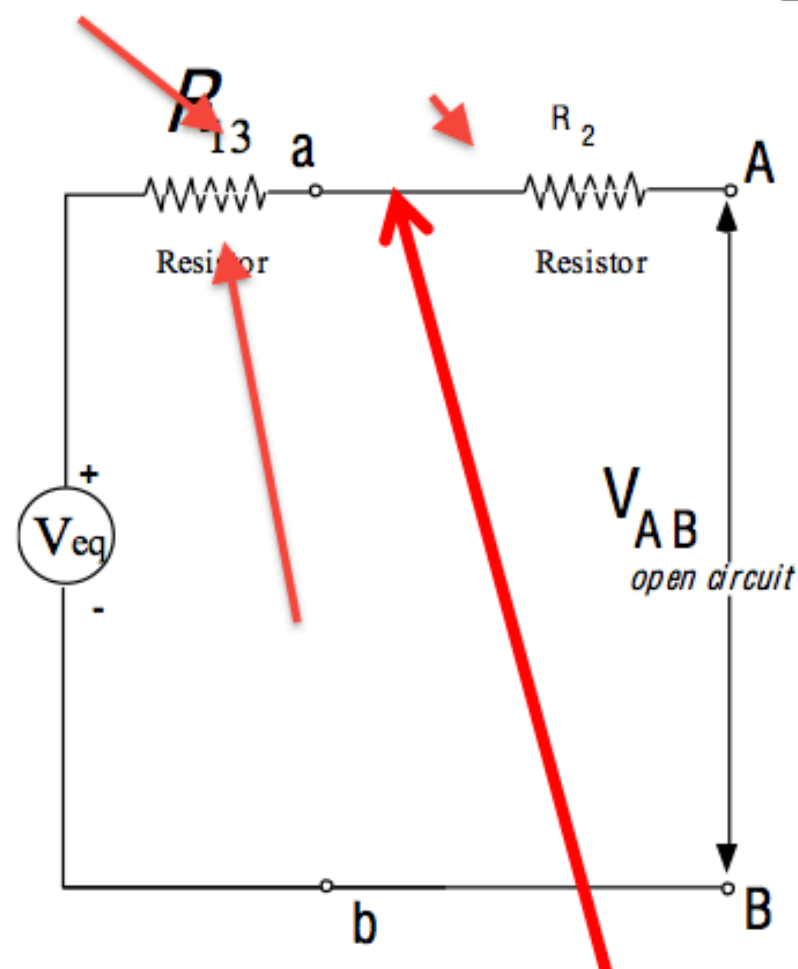

***Serial resistances***


$$V_{eq} = V \cdot \frac{R_3}{(R_1 + R_3)}$$

$$R_{13} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} = \frac{R_1 R_3}{(R_1 + R_3)}$$

- ***Replace again with Thevenin Equivalent Circuit***
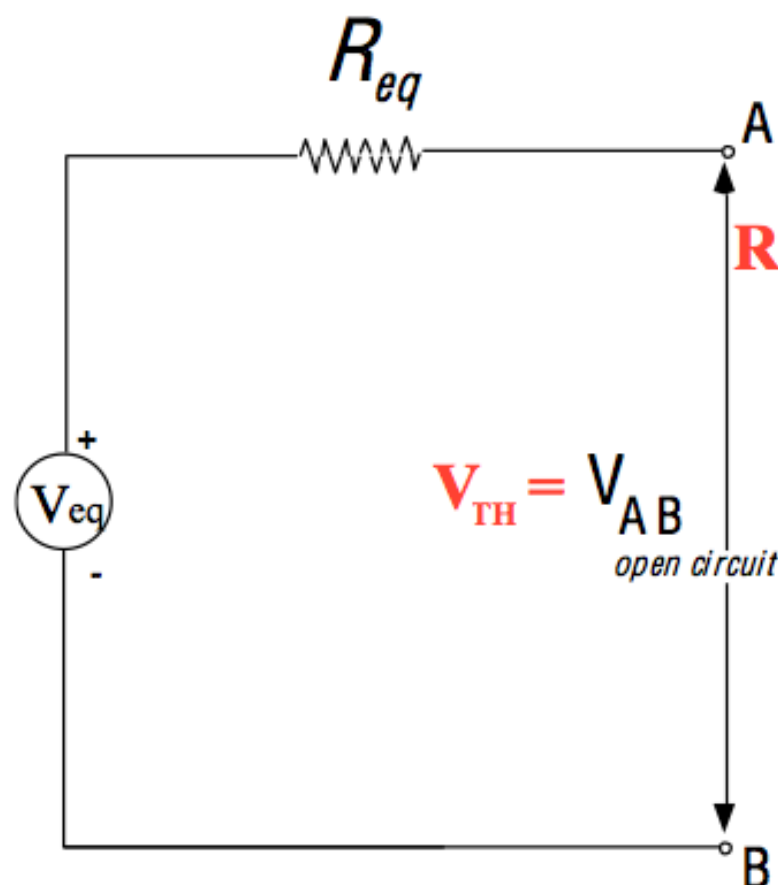
## Thevenin's Equivalent Circuit (4)

$$V_{eq} = V \cdot \frac{R_3}{(R_1 + R_3)}$$




$$R_{TH} = R_{eq} = R_2 + \frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} = R_2 + \frac{R_1 R_3}{(R_1 + R_3)}$$

$$= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 + R_3}$$

• ***Final Thevenin Equivalent Circuit***

# Thevenin's Equivalent Circuit

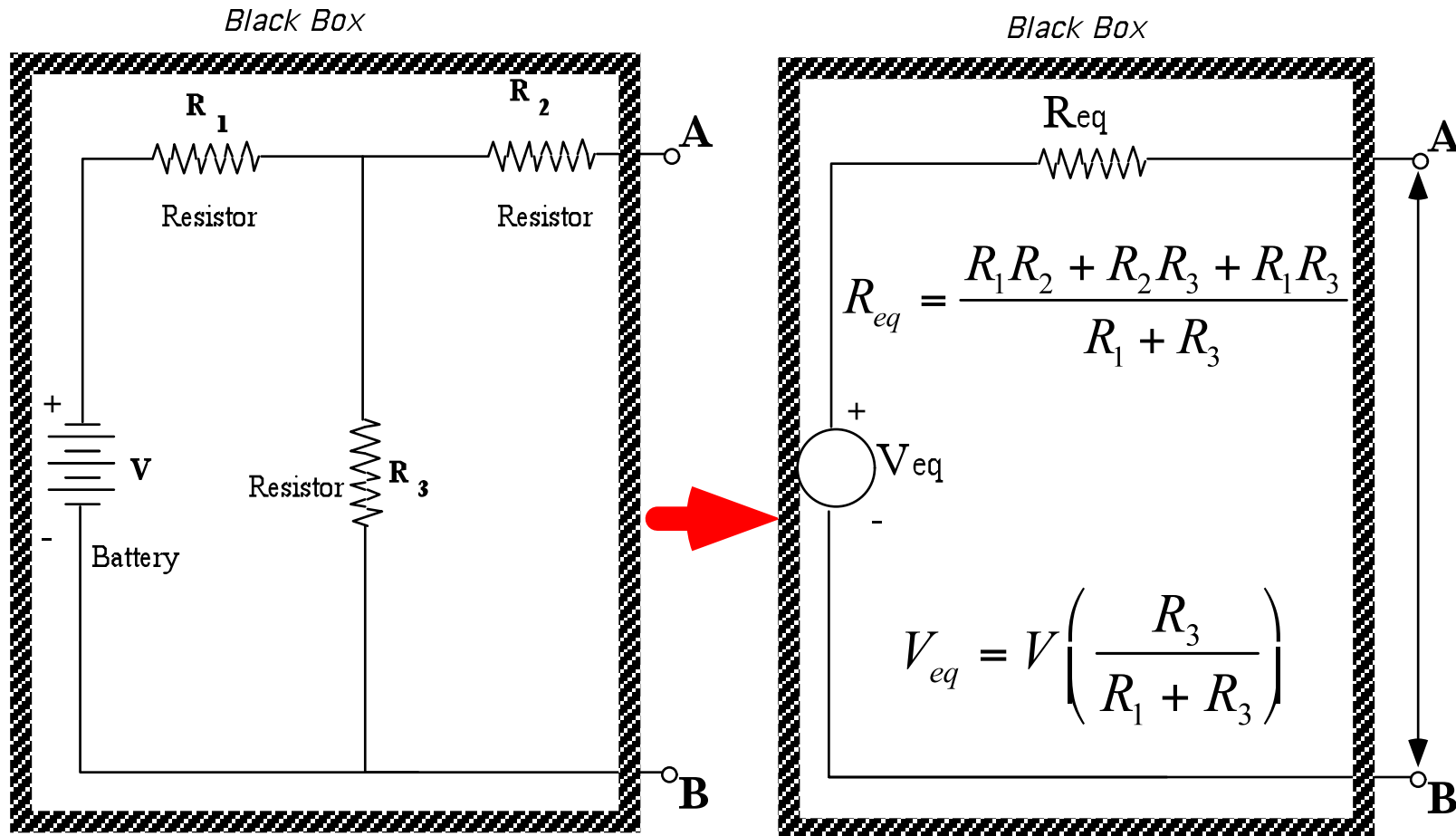

- *Allows Circuits of Components to be Simplified for Modeling and analysis*

*Second Circuit far  
More simple ...  
“but equivalent”*

## Thevenin's Equivalent Circuit ...



$$V_{eq} = V \cdot \left( \frac{R_3}{R_1 + R_3} \right) \rightarrow R_3 = R_1 \cdot \left( \frac{V_{eq}/V}{1 - V_{eq}/V} \right)$$

$$R_3 = 120\Omega \cdot \left( \frac{4/12}{1 - 4/12} \right) = 60\Omega$$

$$I_2 = I_{AB} = \frac{V_{eq}}{R_{eq}} = \frac{V_{eq}}{\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 + R_3}} = \frac{V \cdot \frac{R_3}{R_1 + R_3}}{\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 + R_3}} =$$

$$\frac{R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \cdot V = \left( \frac{60}{120 \cdot 200 + 200 \cdot 60 + 120 \cdot 60} \right)_{1/\Omega} \cdot 12_V = 0.01667 \text{ V}$$


## Lab 3 Circuit Solution

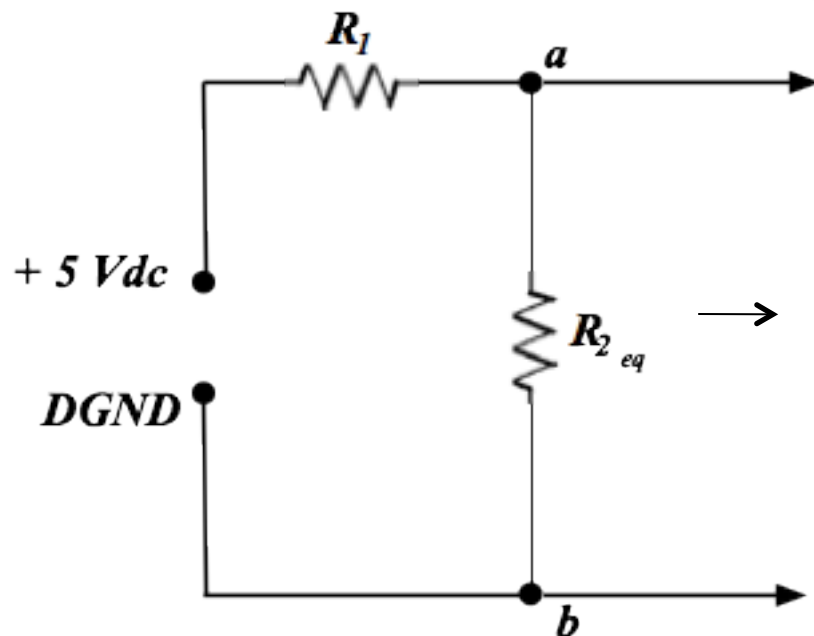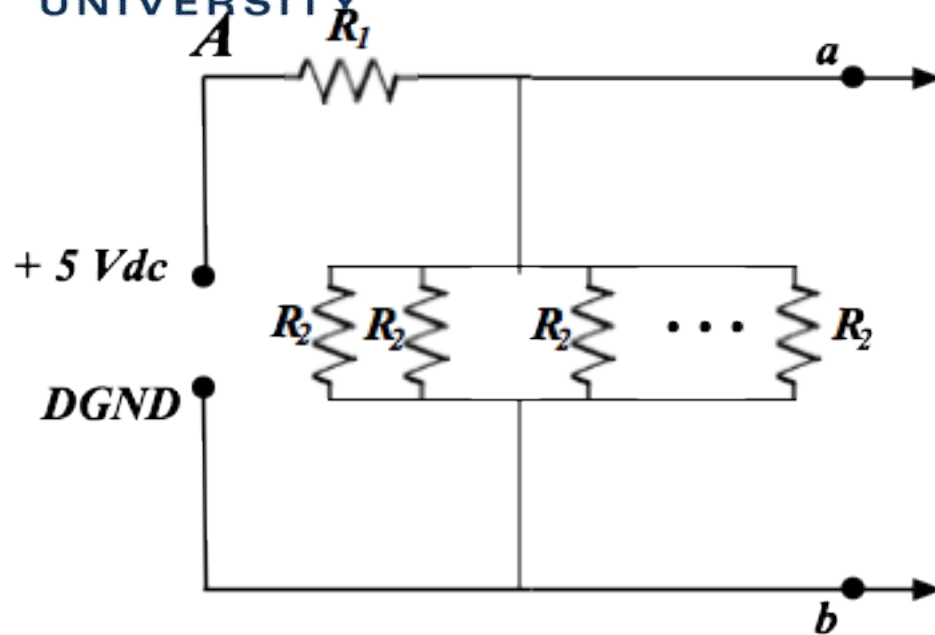

Equivalent Circuit (1)

$$R_{2eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_2} + \frac{1}{R_2} + \dots \frac{1}{R_2}} = \frac{1}{n} \cdot R_2$$

## Lab 3 Circuit Solution (2)

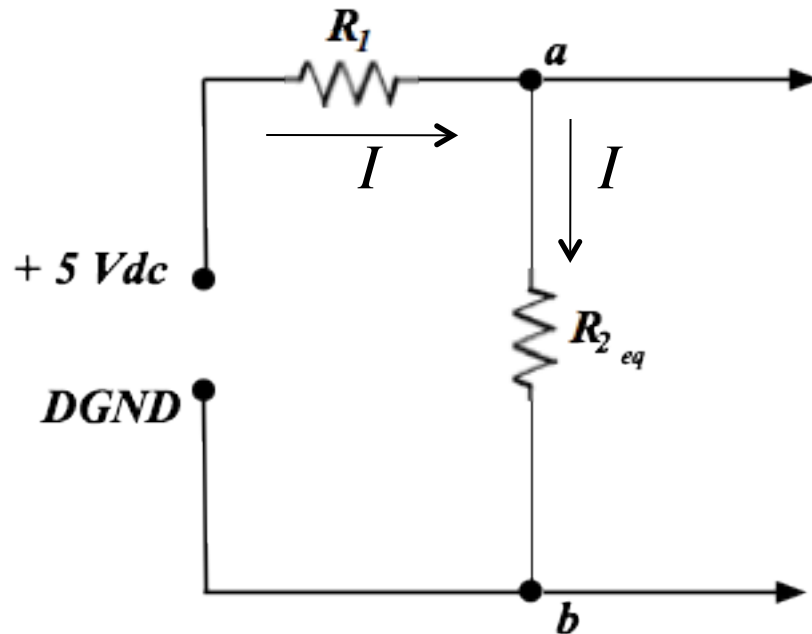

$$R_{2eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_2} + \frac{1}{R_2} + \dots \frac{1}{R_2}} = \frac{1}{n} \cdot R_2$$

$$V_{ab} = \frac{R_{2eq}}{R_1 + R_{2eq}} = \frac{\frac{1}{n} \cdot R_2}{R_1 + \frac{1}{n} \cdot R_2} = \frac{R_2}{n \cdot R_1 + R_2}$$

$$I = \frac{V}{R_1 + R_{2eq}} = \frac{V}{R_1 + \frac{1}{n} \cdot R_2} = \frac{n \cdot V}{n \cdot R_1 + R_2}$$

As  $n$  grows ...  $R_{2eq}$   
Approaches a short circuit