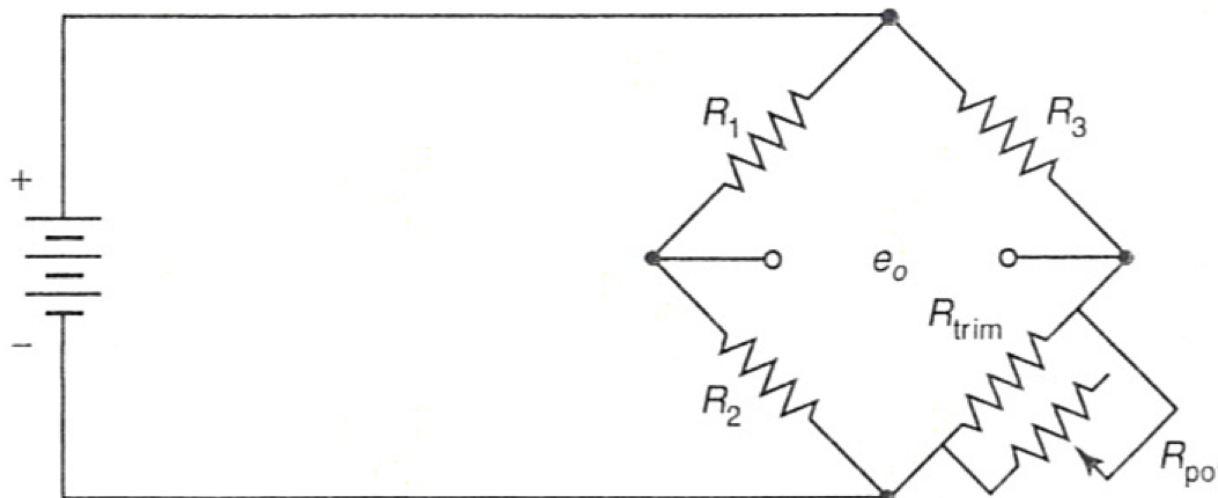


Homework ~~5~~ 6

- Figure below shows a shunt balance arrangement for nulling a Wheatstone bridge. Suppose
- 1) that $R_1 = R_3 = 120\ \Omega$, $R_{\text{trim}} = 127\ \Omega$, and $R_{\text{pot}} = 10\ \text{k}\Omega$. What is the maximum value of R_2 for which the bridge can be brought into balance by adjusting R_{pot} ? What would be the maximum value if $R_1 = 119\ \Omega$ and $R_3 = 121\ \Omega$?



- Assume Pot is fully variable from 0 to 10 k Ω

Circuit for Problem

Part 1 Solution

$$\text{Let } R_4 = R_{\text{trim}} \quad R_{\text{pot}} = \left(\frac{1}{R_{\text{trim}}} + \frac{1}{R_{\text{pot}}} \right)^{-1}$$

At balance (Eqn 7.14a)

$$\frac{R_1}{R_3} = \frac{R_2}{R_4} = R_2 \left(\frac{1}{R_{\text{trim}}} + \frac{1}{R_{\text{pot}}} \right) \quad R_1 = R_3$$

$$R_2 = \left(\frac{1}{R_{\text{trim}}} + \frac{1}{R_{\text{pot}}} \right)^{-1}$$

$$R_2 \leq \left(\frac{1}{127} + \frac{1}{10,000} \right)^{-1} = \underline{\underline{125.4 \, \Omega}}$$

If $R_1 = 119 \, \Omega$ and $R_3 = 121 \, \Omega$


$$R_2 \leq \frac{119}{121} \left(\frac{1}{127} + \frac{1}{10,000} \right)^{-1} = \underline{\underline{123.3 \, \Omega}}$$

Homework 5

- 2) . A mechanical engineering student wishes to determine the internal pressure existing in a diet soda can. She proceeds by carefully mounting a single-element strain gage aligned in circumferential direction on the center of the soda can, as shown in Figure Below. After wiring the gage properly to a commercial strain indicator, she “pops” the flip-top lid, which relieves the internal pressure. She notes that the strain indicator reads -400μ -strain. If the can body is made of aluminum with a thickness of 0.010 in. and a diameter of 2.25 in., what was the original internal pressure of the sealed can?

Assume $E = 10 \text{ ksi}$ (6.89 GPa)

assume $\nu = 0.5$

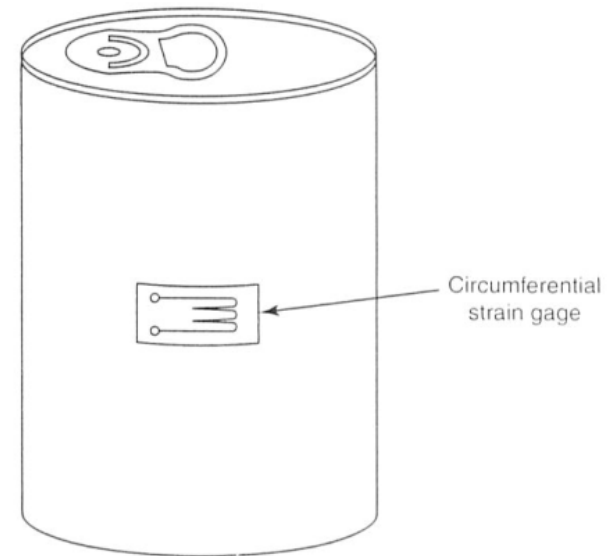

Part 2 Solution

σ_h = circumferential

σ_L = longitudinal

Assume $\sigma_h = 2\sigma_L$

$$\epsilon_h = \frac{1}{E} (\sigma_h - \nu \sigma_L) = \frac{\sigma_h}{E} (1 - 0.5\nu)$$

$$\sigma_h = \frac{E \epsilon_h}{1 - 0.5\nu} = \frac{10 \times 10^6 \times 400 \times 10^{-6}}{1 - 0.5(0.3)} = \underline{4706 \text{ psi}}$$


$$\sigma_h = \frac{PD}{2t} \quad P = \frac{2t\sigma_h}{D} = \frac{4706 \times 2 \times 0.01}{2.25}$$

$$\underline{P = 42 \text{ psi}} \quad (289 \text{ kPa})$$

Input Data		Microstrains
Gauge Pressure, kPa	288.21	400.001
Can Wall Thickness, cm	0.0254	Pressure, psig
Can Diameter, cm	5.715	41.8015
Can Modulus, Pascals	6.89E+10	
Poisson ratio	0.3	

Homework 5

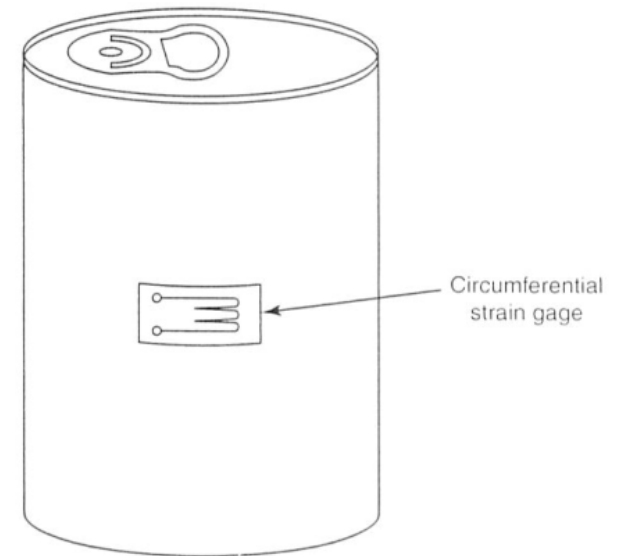- 3) Another student also performed the experiment described in [Previous problem](#). Unfortunately, he did not have access to the commercial strain indicator, and instead he had to construct his own Wheatstone bridge circuit. His strain gage had an initial resistance of $120\ \Omega$ and a gage factor of 2.05. He used the single gage as one leg of the bridge, which he powered with a 6-V battery. The bridge output was fed to an amplifier (gain = 1000), and the amp's output was read by a voltmeter. The student balanced the bridge circuit before he opened the can. After the can was opened, the voltmeter indicated a voltage of $-1.57\ \text{V}$. What was the measured strain for his can?



Part 3 Solution

$$V_{out} = G_{amplifier} \cdot \frac{V_{ex} \cdot G_F \cdot \varepsilon}{4 + 2 \cdot G_F \cdot \varepsilon}$$

$$\rightarrow (4 + 2 \cdot G_F \cdot \varepsilon) \cdot V_{out} = G_{amplifier} \cdot V_{ex} \cdot G_F \cdot \varepsilon$$

$$(G_{amplifier} \cdot V_{ex} \cdot G_F - 2 \cdot G_F \cdot V_{out}) \cdot \varepsilon = 4 \cdot V_{out}$$

$$\rightarrow \varepsilon = \frac{4 \cdot V_{out}}{(G_{amplifier} \cdot V_{ex} \cdot G_F - 2 \cdot G_F \cdot V_{out})}$$

$$\frac{4(-1.57)}{1000 \cdot 6 \cdot 2.05 - 2 \cdot 2.05(-1.57)} 10^6 = -510.302 \text{ Microstrains}$$