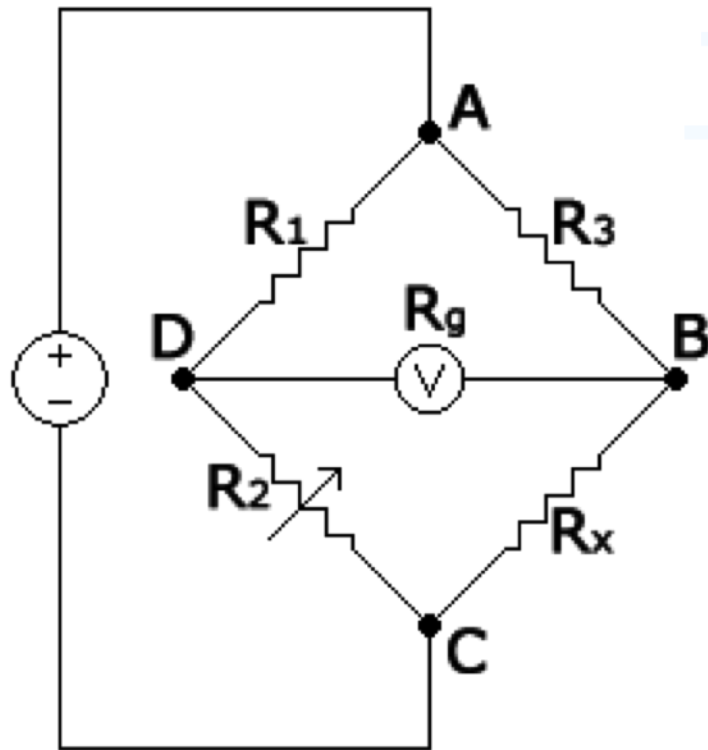


# Section 4.1 : Introduction to the Fundamental Tool of Modern Measurement, The Resistance Bridge



*Beckwith Chapter 7*  
*Sections 7.7-7.9*



Sir Charles Wheatstone

# Resistance and Resistivity (1)

- **Electrical resistivity** is a measure of how strongly a material opposes the flow of electric current.
- A low resistivity indicates a material that readily allows the movement of electrical charge.
- The SI unit of electrical resistivity is the ohm meter.
- The **Resistance** of Specimen is calculated by

$$R = \rho \cdot \frac{L}{A}$$


$\rho$  = resistivity of material ( $\Omega\text{-m}$ )

$L$  = length of specimen ( $m$ )


$A$  = cross sectional area of specimen ( $m^2$ )
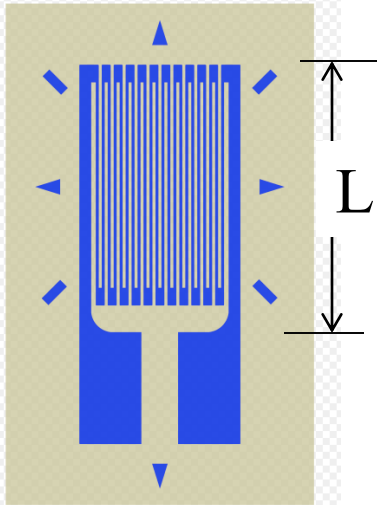
## Resistance and Resistivity (2)

• *Now consider a device made of a material with a known Resistivity .... And the design is far more sensitive to strain in the vertical direction than in the horizontal direction.*



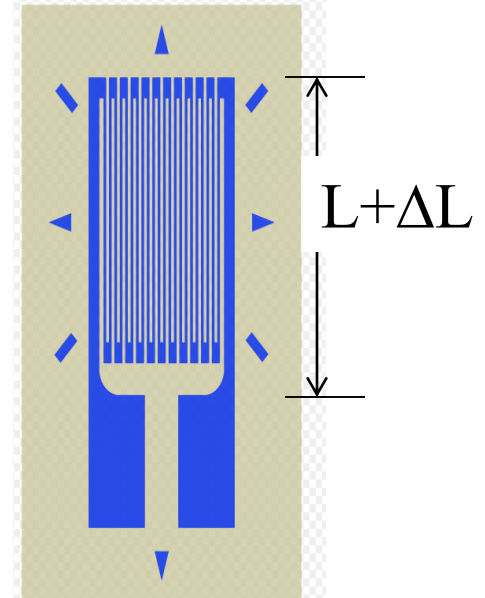- Now stretch the device ....
- Cross section does not change Much ... but length changes significantly



$$R = \rho \cdot \frac{L}{A}$$

$$R + \Delta R = \rho \cdot \left( \frac{L + \Delta L}{A - \Delta A} \right)$$

## Resistance and Resistivity (3)

- Normalize by R and collect terms

$$\frac{R + \Delta R}{R} = \left( \frac{L + \Delta L}{A - \Delta A} \right) \frac{A}{L} = \left( \frac{L + \Delta L}{L} \right) \frac{A}{A - \Delta A} \rightarrow$$

$$1 + \frac{\Delta R}{R} = \left( 1 + \frac{\Delta L}{L} \right) \left( \frac{A}{A - \Delta A} \right) \rightarrow$$

$$\frac{\Delta R}{R} = 1 - \left( \frac{A}{A - \Delta A} \right) + \left( \frac{\Delta L}{L} \right) \left( \frac{A}{A - \Delta A} \right)$$

$$1 - \left( \frac{A}{A - \Delta A} \right) = \left( \frac{\Delta A}{A - \Delta A} \right) \quad \text{For small deflections } \sim 0$$


# Resistance and Resistivity (4)

- Solving for area ratio


$$\frac{\Delta R}{R} = \left( \frac{\Delta L}{L} \right) \left( \frac{A}{A - \Delta A} \right) \rightarrow \left( \frac{A}{A - \Delta A} \right) \equiv G_F = \frac{\Delta R}{R} / \varepsilon$$

$G_F$  ---> Gauge factor

$\varepsilon$  ---> linear strain

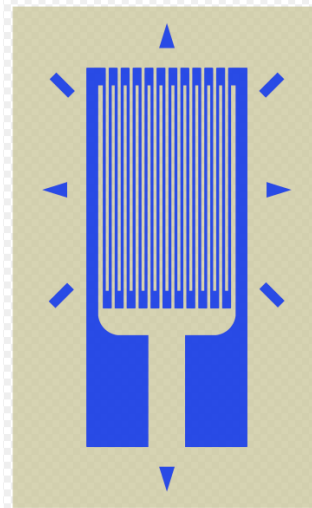

$$\Delta R = G_F \varepsilon R_g$$

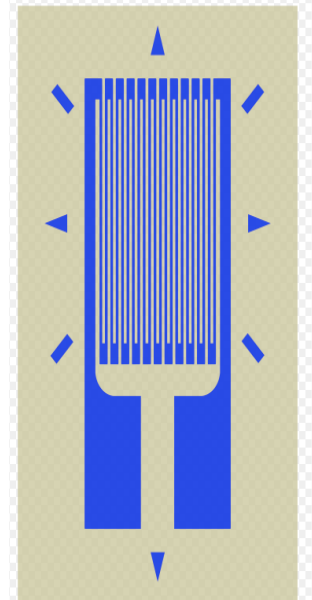


- *Strain Gauge ... change in resistance is proportional To the strain on the sensor*

## Strain Gauge (1)


- A **strain gauge** is a sensor used to measure deformation of an object.
- Most common type of strain gauge consists of an insulating flexible backing which supports a metallic foil pattern.
- Gauge is attached to the object by a suitable adhesive.
- As object being tested is deformed, the foil is deformed, causing its electrical resistance to change .... Which should be sensible  
As a change in current thru sensor ...

## Strain Gauge (2)

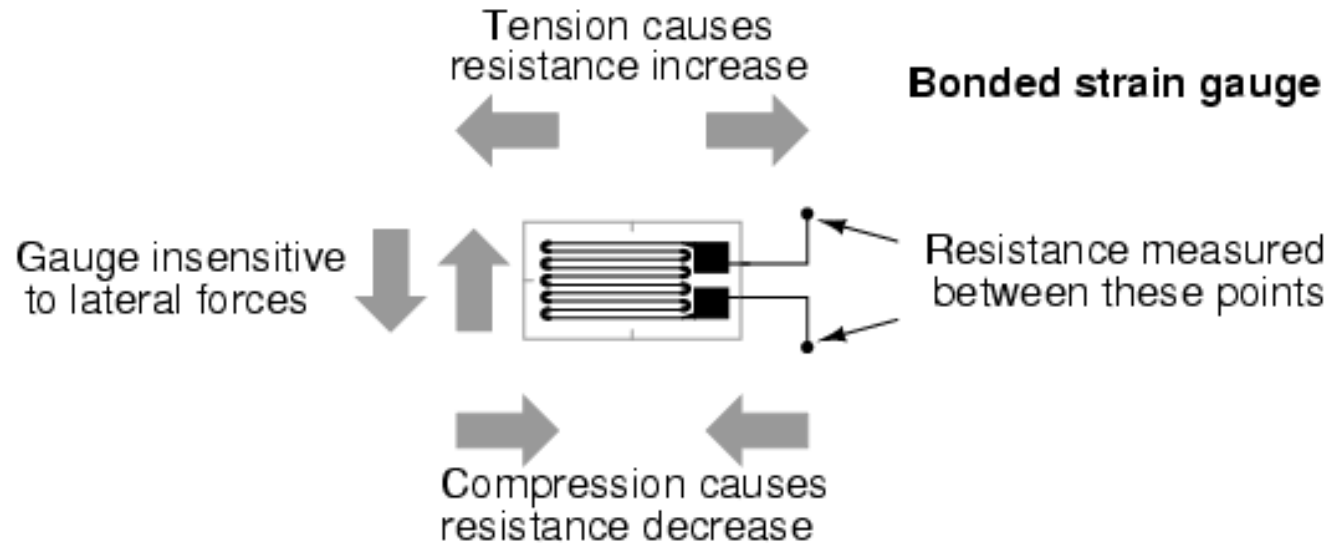

- After being strained, gauge is designed to “bounce-back” to original shape
- Given limits imposed by the elastic limits of the gauge material and test specimen, Resistance changes only a small fraction of a percent ( $\sim 0.1\%$ ) for full force range of the gauge.

# Strain Gauge (3)

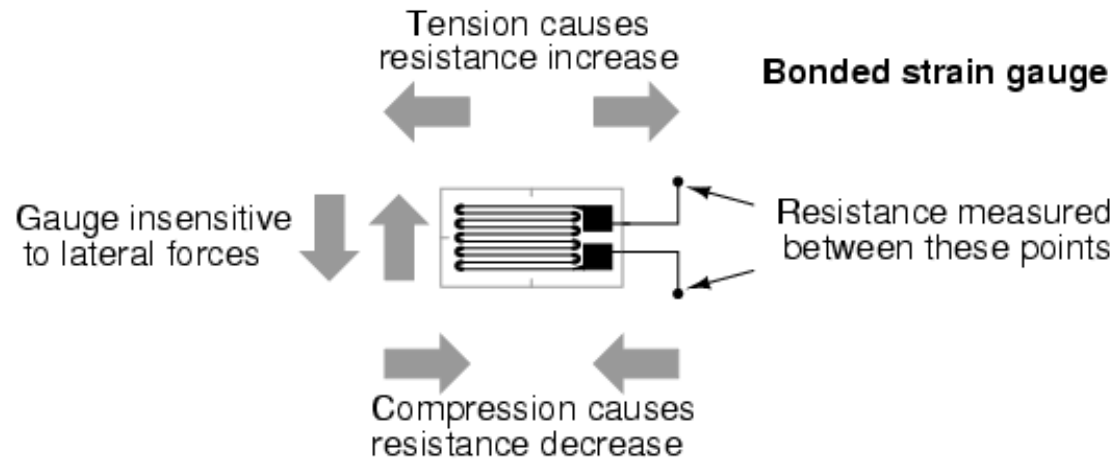


- Forces great enough to induce greater resistance changes permanently deform the test specimen and/or gauge.
- In order to use the strain gauge as a practical instrument, must measure very small changes in resistance with high accuracy.
- Typical strain gauge resistances range from 30  $\Omega$  to 100  $\Omega$  (unstressed).
- $\Delta R \sim 0.03 \text{ to } 0.1 \Omega \dots$  a very difficult task for a multimeter



# Wheatstone Bridge (1)

- Need a device that amplifies the changes in resistance

- Consider the circuit

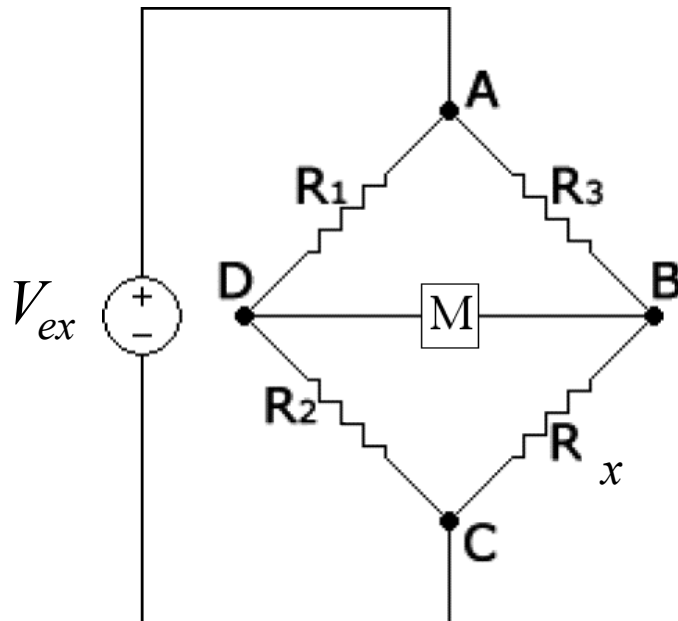


- What will voltage Across the volt Meter terminals  $\{D,B\}$  read?


... Oh Boy ...  
... this will be fun ...
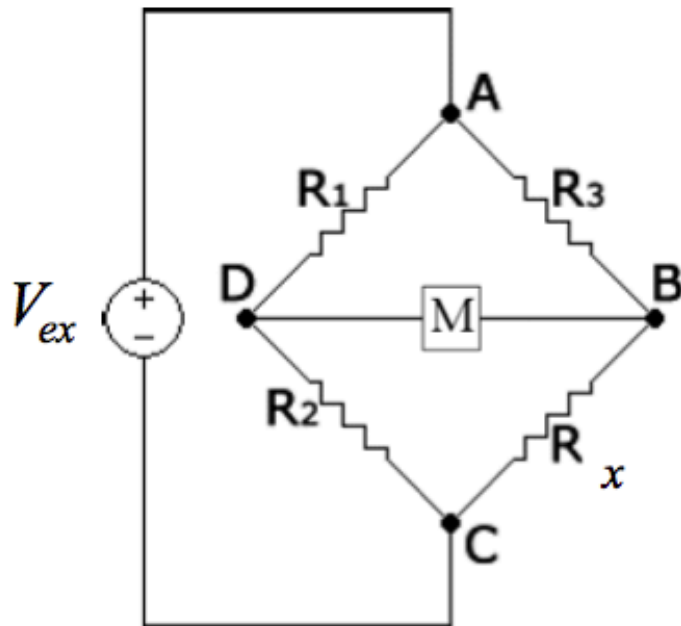
# Wheatstone Bridge (1)


- Need a device that amplifies the changes in resistance
- Consider the circuit



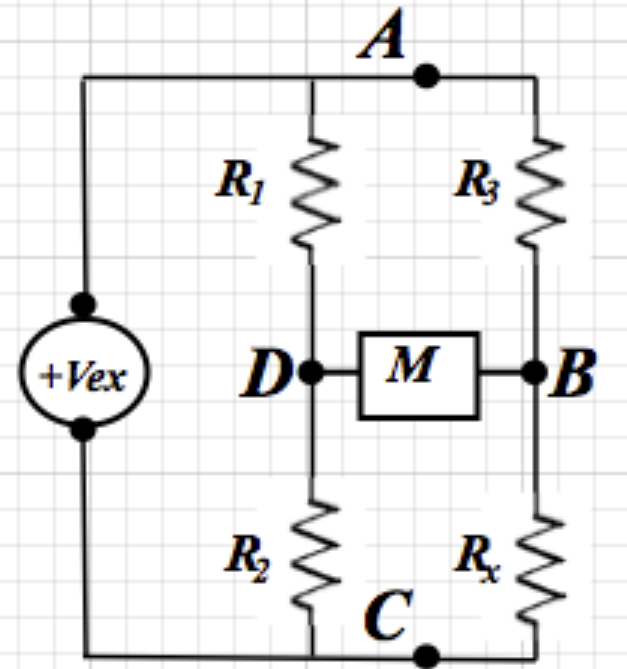REDRAW CIRCUIT AS PAIR OF  
VOLTAGE DIVIDERS




# Wheatstone Bridge (2)

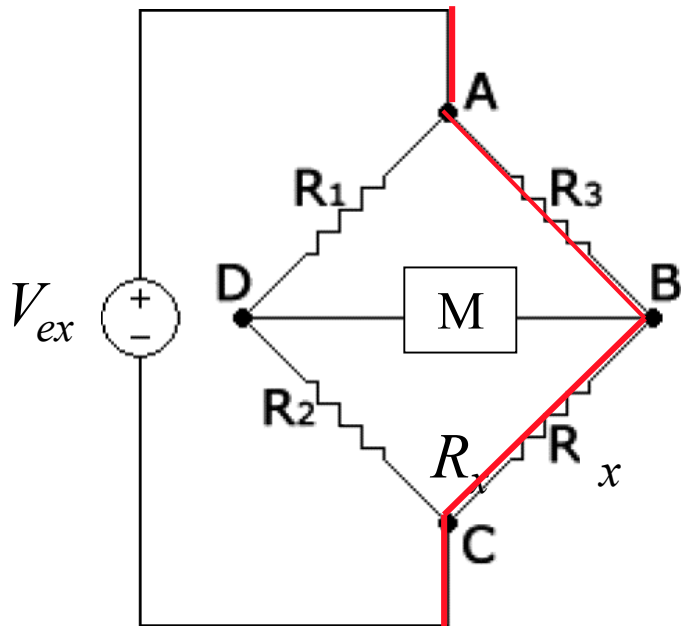

- What is Voltage Drop from *B* to *C*?



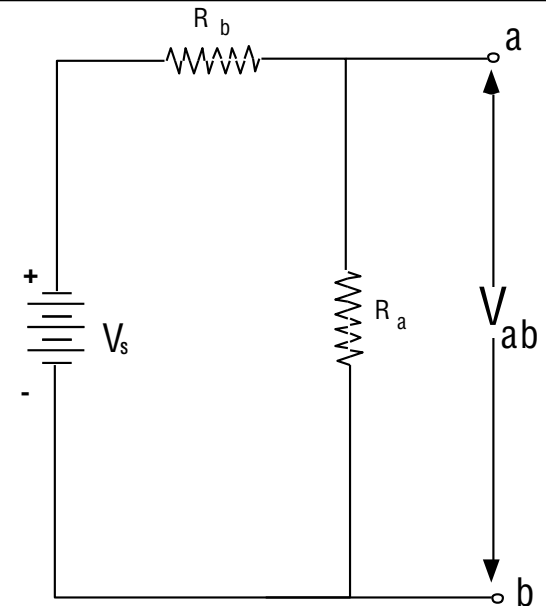
...  
*Looks like*  
*Voltage*  
*Divide Circuit*  
...



$$V_{ab} = V \cdot \frac{R_a}{(R_a + R_b)}$$


$$V_{BC} = V_{ex} \frac{R_x}{R_3 + R_x}$$

## Wheatstone Bridge (2)

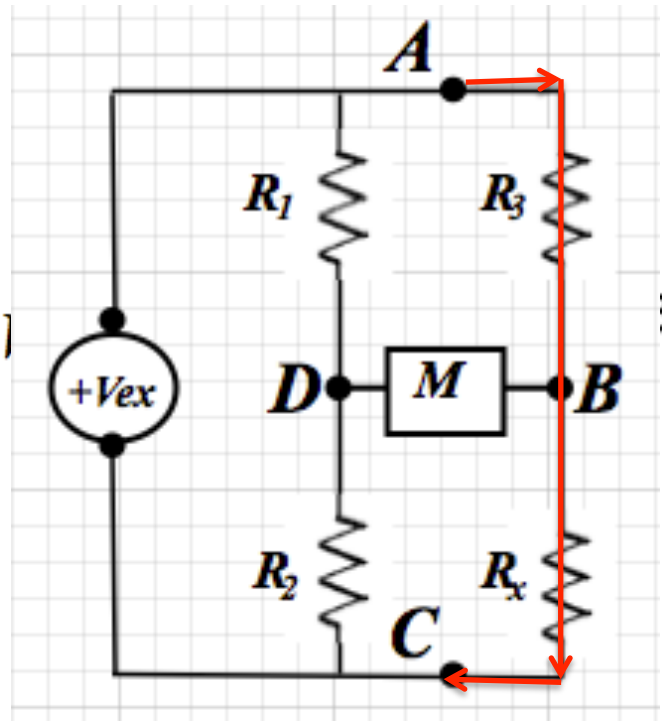

- What is Voltage Drop from *B* to *C*?

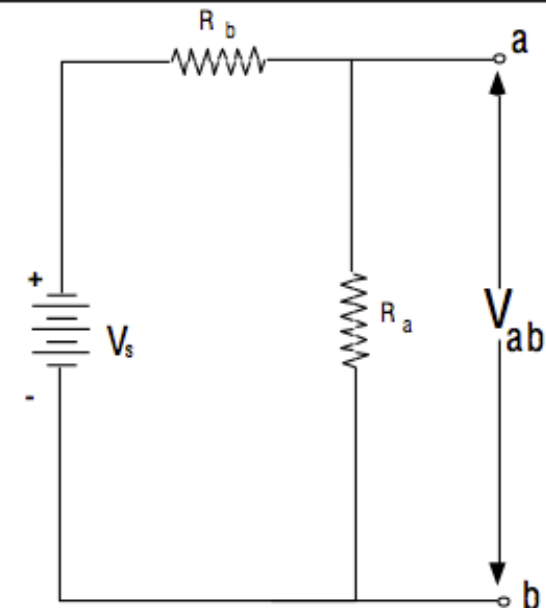...  
*Looks like*  
*Voltage*  
*Divide Circuit*  
...




$$V_{ab} = V \cdot \frac{R_a}{(R_a + R_b)}$$


$$V_{BC} = V_{ex} \frac{R_x}{R_3 + R_x}$$

# Wheatstone Bridge (3)

- What is Voltage Drop from *D* to *C*?

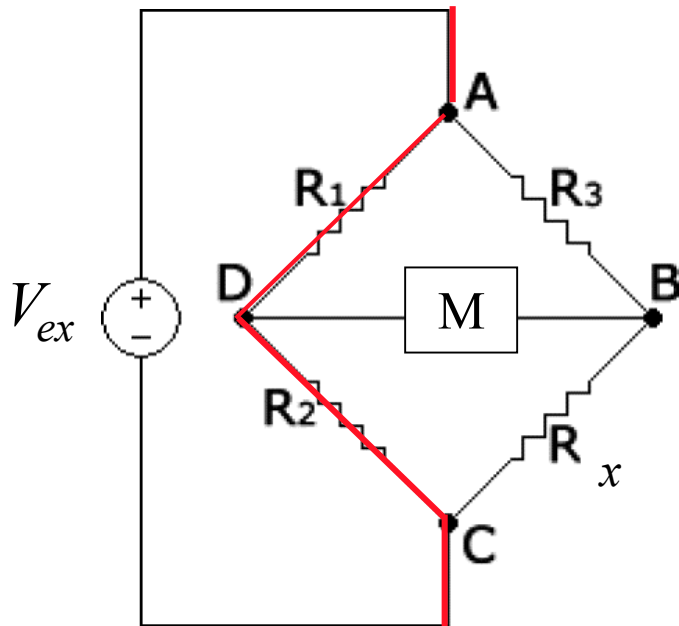

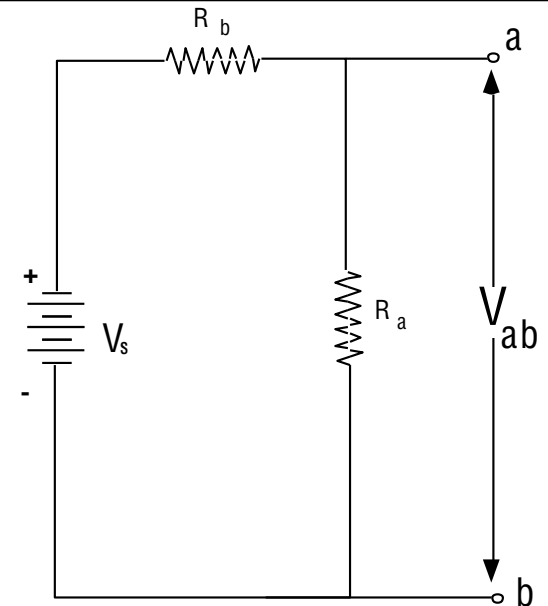
...  
*Looks like*  
*Voltage*  
*Divide Circuit*  
...



$$V_{ab} = V_s \cdot \frac{R_a}{(R_a + R_b)}$$


$$V_{DC} = V_{ex} \frac{R_2}{R_1 + R_2}$$

## Wheatstone Bridge (3)

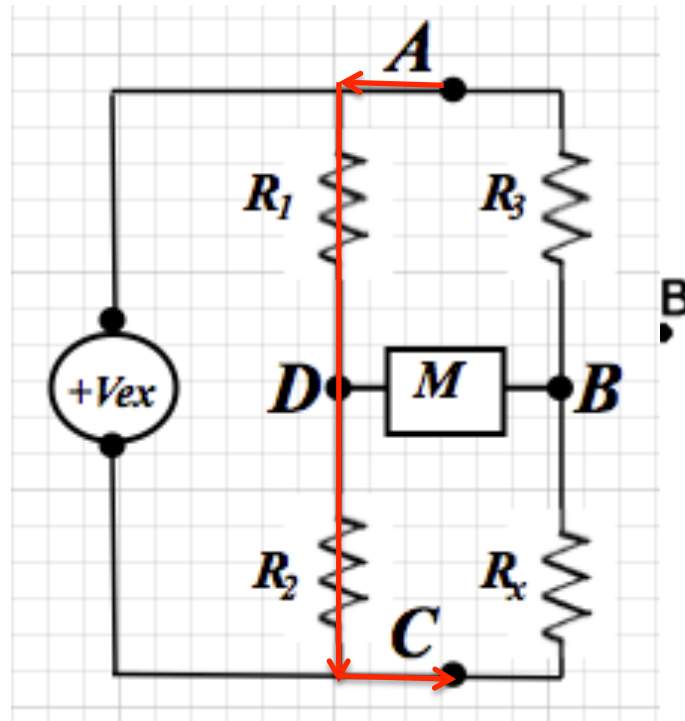


- What is Voltage Drop from *D* to *C*?

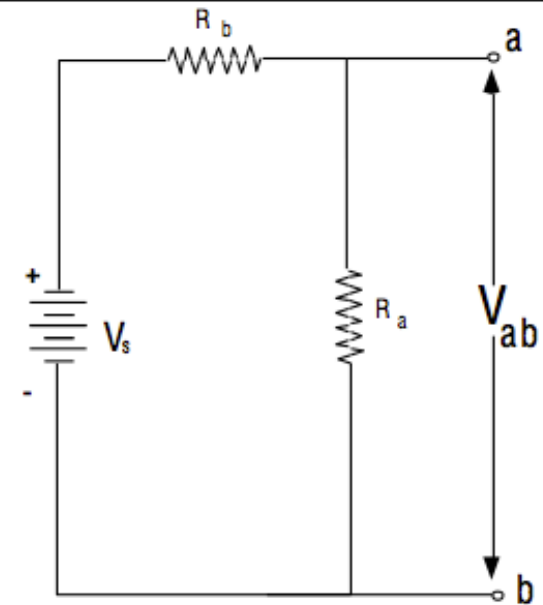...  
*Looks like*  
*Voltage*  
*Divide Circuit*  
...



$$V_{ab} = V \cdot \frac{R_a}{(R_a + R_b)}$$

# Wheatstone Bridge (4)

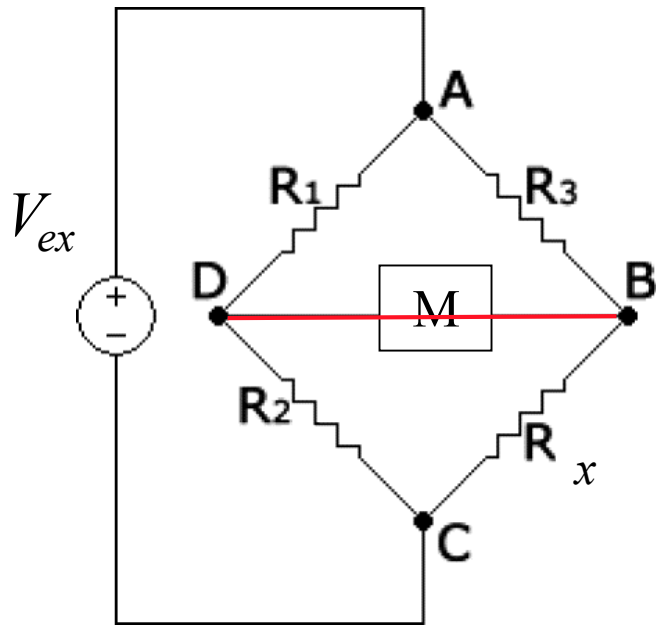


- What is Voltage Drop from  $B$  to  $D$ ? (across meter)
- Assume Impedance of  $M$  is Very Large  $> M\Omega$ , thus negligible current flows across meter

$$V_{BD} = V_{BC} + V_{CD} = V_{BC} - V_{DC} =$$

$$V_{ex} \left( \frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2} \right) = V_{ex} \left( \frac{R_x(R_1 + R_2) - R_2(R_3 + R_x)}{(R_1 + R_2)(R_3 + R_x)} \right) =$$

$$V_{ex} \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)}$$

## Wheatstone Bridge (4)

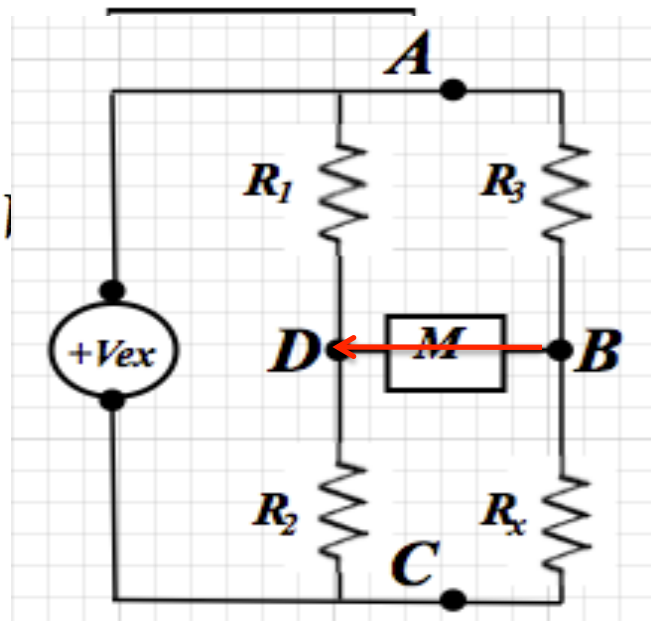

- What is Voltage Drop from  $B$  to  $D$ ? (across meter)
- Assume Impedance of  $M$  is Very Large  $> M\Omega$ , thus negligible current flows across meter

$$V_{BD} = V_{BC} + V_{CD} = V_{BC} - V_{DC} =$$


$$V_{ex} \left( \frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2} \right) = V_{ex} \left( \frac{R_x(R_1 + R_2) - R_2(R_3 + R_x)}{(R_1 + R_2)(R_3 + R_x)} \right) =$$

$$V_{ex} \frac{R_1 R_x - R_2 R_3}{(R_1 + R_2)(R_3 + R_x)}$$


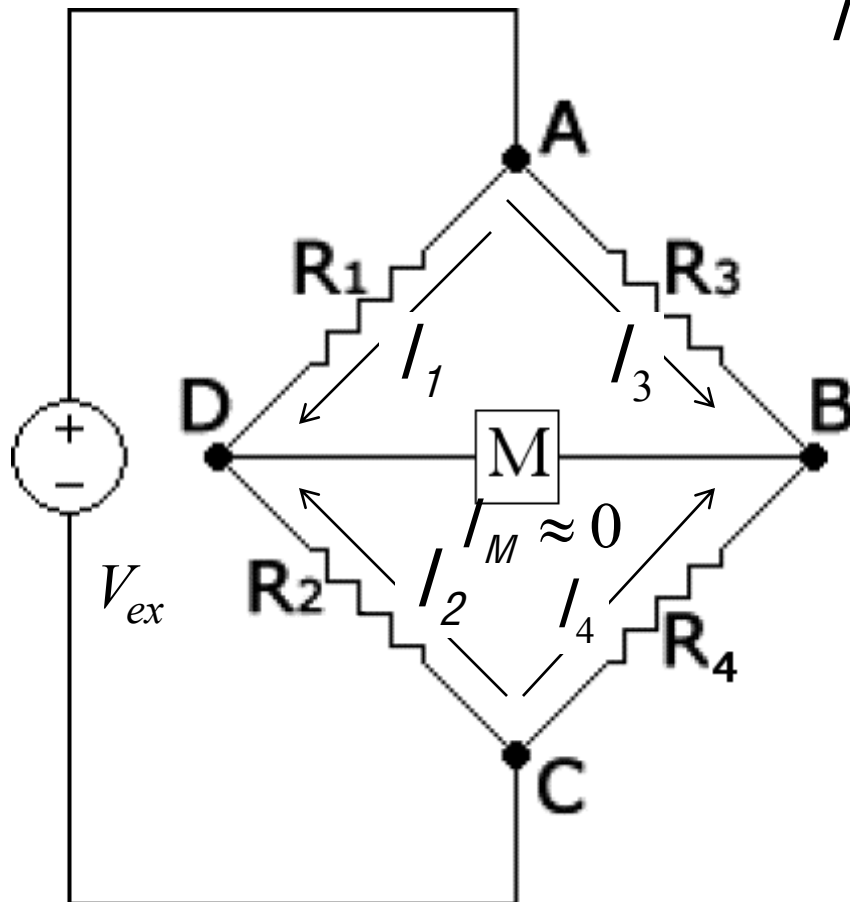
# “Balanced Bridge” (1)

*If the Voltage across the meter  $\{D,B\}=0$  • Currents at nodes  $\{D,B\}$   
... bridge is said to be “balanced.”*



$$I_M \approx 0$$

$$\begin{matrix} I_3 = I_4 \\ I_1 = I_2 \end{matrix}$$

• Voltage drops in Loops  $\{ABD\}$ ,  $\{BCD\}$

$$I_3 R_3 + I_M R_M - I_1 R_1 = 0$$

$$I_4 R_4 - I_2 R_2 - I_M R_M = 0$$


$$\frac{I_3 R_3}{I_4 R_4} = \frac{I_1 R_1}{I_2 R_2}$$

$$\begin{matrix} I_3 = I_4 \\ I_1 = I_2 \end{matrix} \rightarrow \boxed{\frac{R_3}{R_4} = \frac{R_1}{R_2}}$$
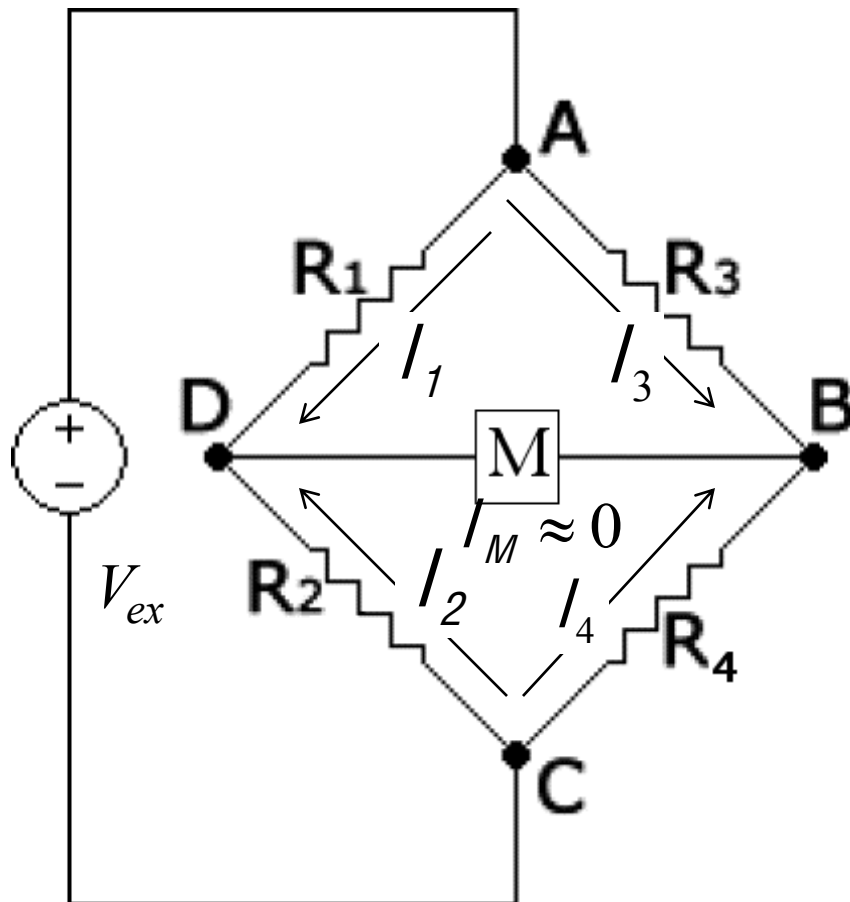
## Balanced Bridge (2)

*from previous....*  $\longrightarrow$

$$\left. \begin{aligned} I_3 R_3 &= I_1 R_1 \rightarrow \frac{R_1}{R_3} = \frac{I_3}{I_1} \\ I_4 R_4 &= I_2 R_2 \rightarrow \frac{R_2}{R_4} = \frac{I_4}{I_2} \end{aligned} \right\}$$



- Sum currents at Node A ...


$$I_1 = -I_3$$

- Sum currents at Node c ...

$$I_2 = -I_4$$

# Balanced Bridge (3)

*from previous....*

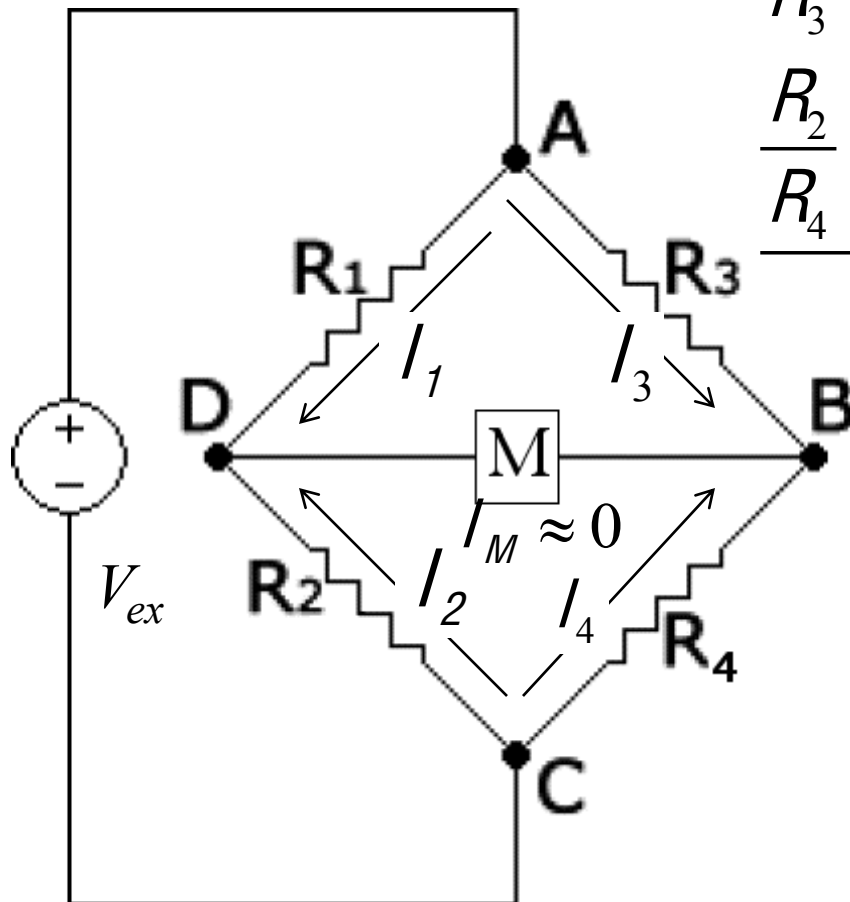


$$\left[ \begin{array}{l} \frac{R_1}{R_3} = \frac{I_3}{I_1} \\ \frac{R_2}{R_4} = \frac{I_4}{I_2} \end{array} \right]$$

$$\rightarrow \begin{array}{l} I_1 = -I_3 \\ I_2 = -I_4 \end{array} \rightarrow \frac{R_1}{R_3} = -1 = \frac{R_2}{R_4}$$

$$\boxed{\frac{R_1}{R_3} = \frac{R_2}{R_4}}$$

## Balanced Bridge (4)

*Conditions for Balanced Bridge ....*

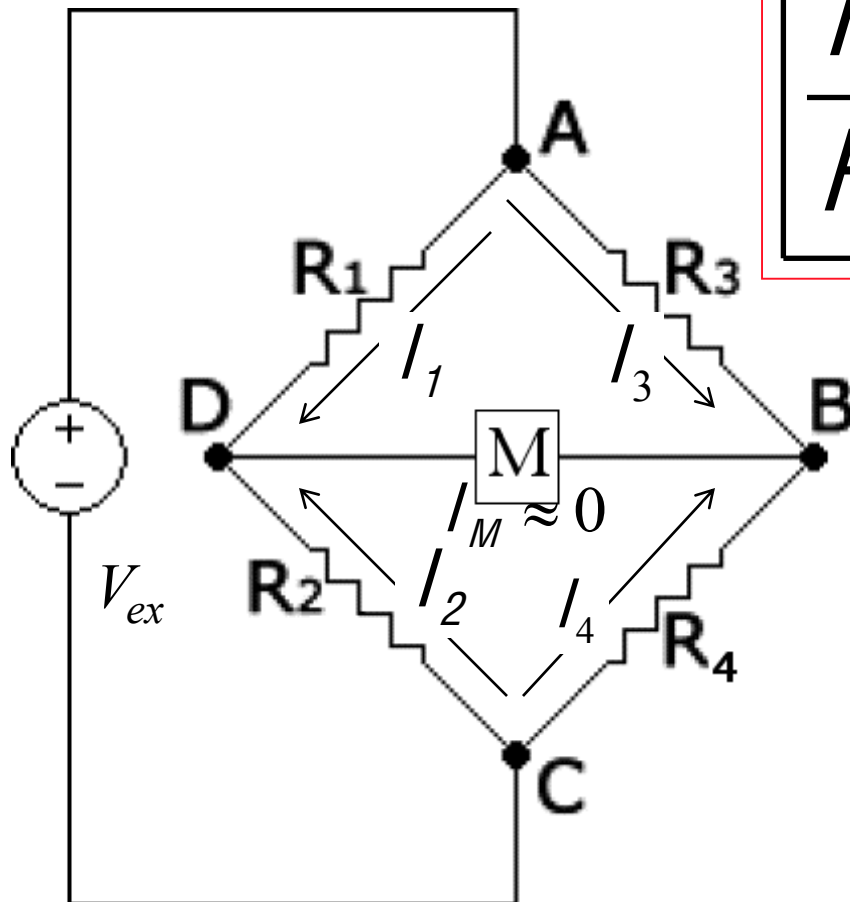


$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

• *Ratio of resistances of any two Adjacent arms must equal ratio Of resistance of remaining two Arms*

...

# Balancing Techniques (1)

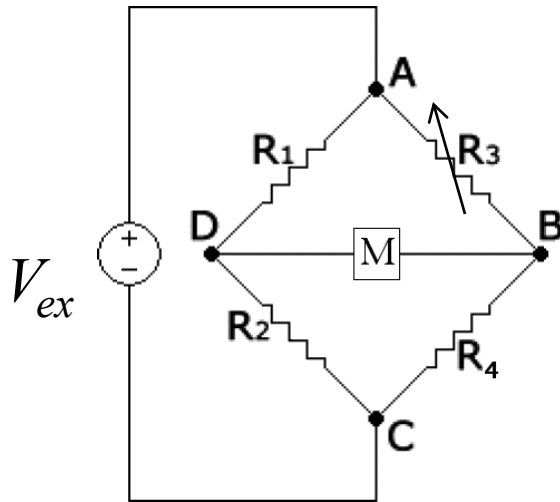

- Good way to sense  
*An unknown resistance*
- Solve for unknown resistance
- Adjust  $R_3$  until  $I_M = 0$

$$\begin{array}{l} I_3 R_3 = I_1 R_1 \\ I_x R_x = I_2 R_2 \end{array} \rightarrow R_x = \frac{(R_2 I_2)(R_3 I_3)}{(R_1 I_1) I_x} = \left( \frac{R_2 R_3}{R_1} \right) \left( \frac{I_2 I_3}{I_1 I_x} \right) \downarrow$$

$$\begin{array}{l} I_3 = I_x \\ I_1 = I_2 \end{array} \rightarrow R_x = \left( \frac{R_2 R_3}{R_1} \right)$$

**$R_3$  variable resistance  
“rheostat”**


## Balancing Techniques (2)

*If we make  $R_3$  a calibrated variable resistor, then we simply dial it until Meter current = 0.*

*If a change in the measured*


*condition causes a change in  $R_4$ , we determine the new value by re-nulling the bridge.*

• “Null Method”

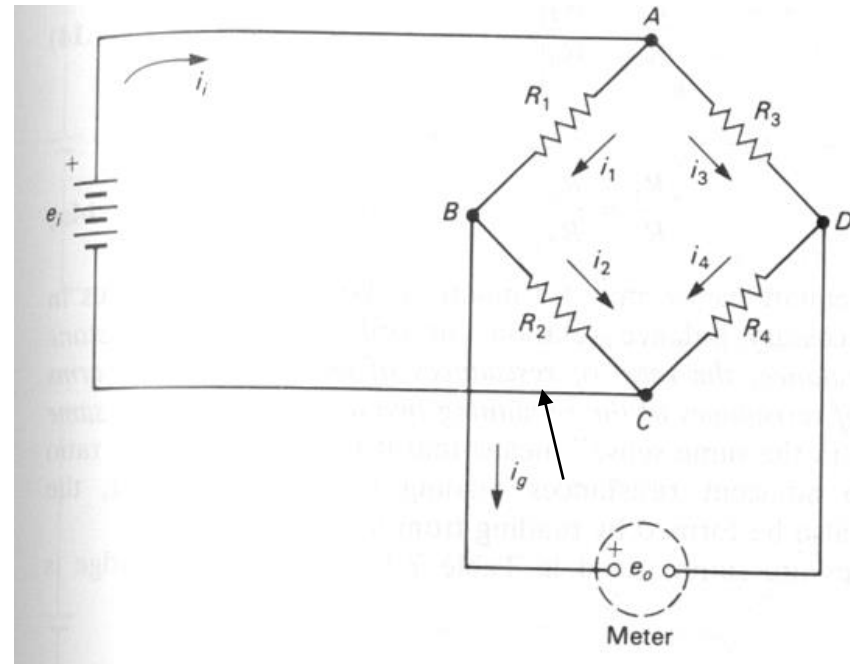

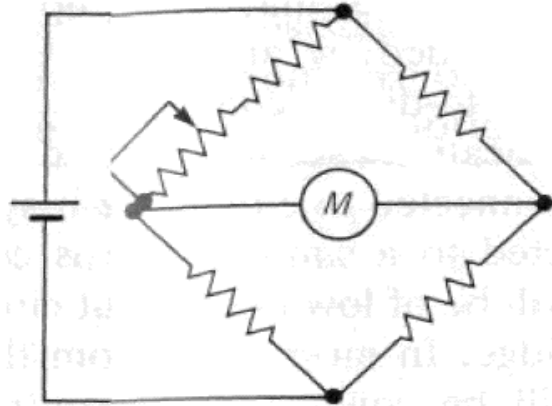
# Balancing Techniques (2)


Arrangements used to balance dc resistance bridges




(a) Series balance

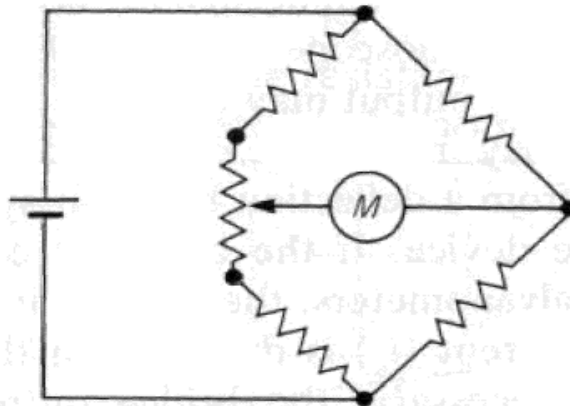

(b) Differential series balance

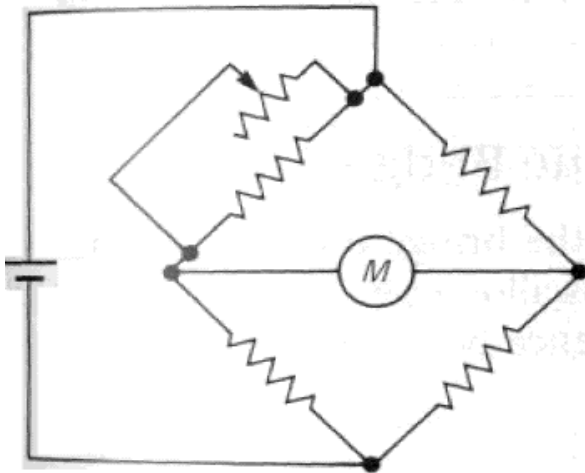


(c) Shunt balance

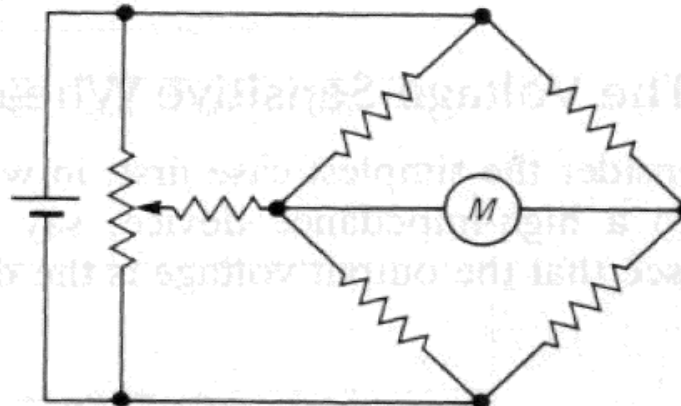

(d) Differential shunt balance

# Resistance Bridge Summary

- .. *Infinite Meter Impedance*

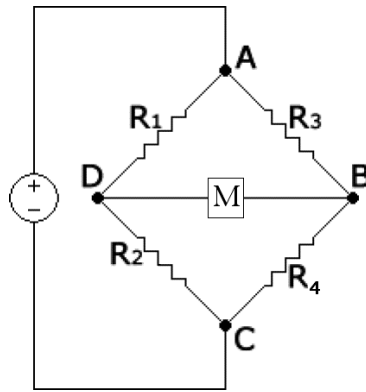

$$\begin{bmatrix} I_M = 0 \\ I_1 = \frac{V_{ex}}{(R_1 + R_2)} \\ I_2 = \frac{V_{ex}}{(R_1 + R_2)} \\ I_3 = \frac{V_{ex}}{(R_3 + R_4)} \\ I_4 = \frac{V_{ex}}{(R_3 + R_4)} \end{bmatrix} \rightarrow$$

*Current thru  
resistor*

$$\begin{bmatrix} V_M = V_{ex} \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} \\ V_1 = V_{ex} \frac{R_1}{(R_1 + R_2)} \\ V_2 = V_{ex} \frac{R_2}{(R_1 + R_2)} \\ V_3 = V_{ex} \frac{R_3}{(R_3 + R_4)} \\ V_4 = V_{ex} \frac{R_4}{(R_3 + R_4)} \end{bmatrix} \rightarrow$$

*Voltage drop  
cross resistor*

$$\begin{bmatrix} P_M = 0 \\ P_1 = R_1 \left[ \frac{V_{ex}}{(R_1 + R_2)} \right]^2 \\ P_2 = R_2 \left[ \frac{V_{ex}}{(R_1 + R_2)} \right]^2 \\ P_3 = R_3 \left[ \frac{V_{ex}}{(R_3 + R_4)} \right]^2 \\ P_4 = R_4 \left[ \frac{V_{ex}}{(R_3 + R_4)} \right]^2 \end{bmatrix}$$

*Power dissipated  
by resistor*